



Analog Electronics - XLVI

Lakshya GATE 2023: Course on Analog Electronics for ECE EE IN




**THE BEST WAY
TO PREDICT THE
FUTURE IS TO
CREATE IT. ✨**

Peter Drucker

Q
QUES 8.2.14

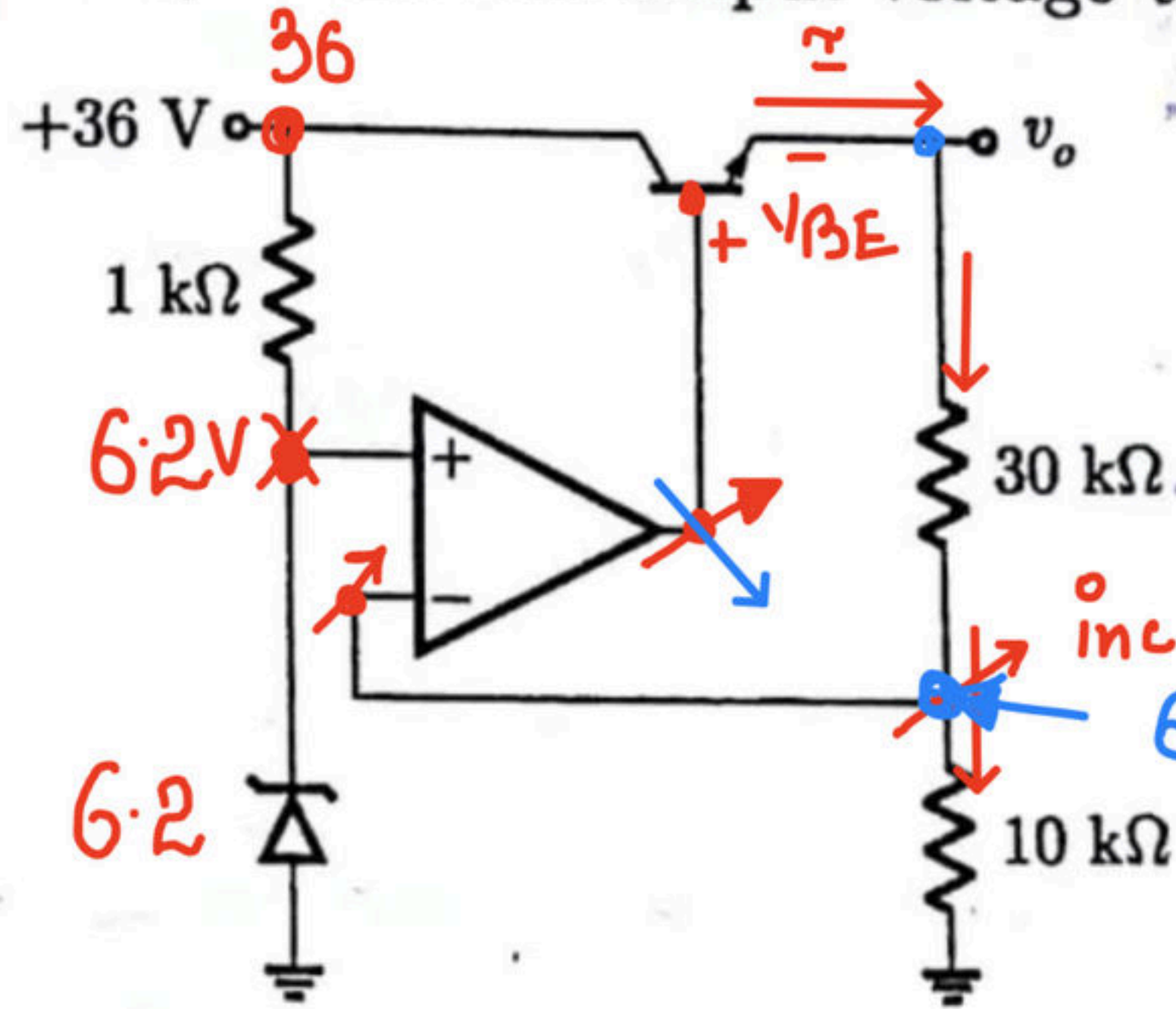In the op-amp series regulator circuit shown below, $v_z = \underline{6.2\text{ V}}$, $V_{BE} = 0.7\text{ V}$ and $\beta = 60$. The output voltage v_o is _____ volts.



a) neg. f/d

b) +ve f/d


• Zener will go in B.D

$$V_o \times \frac{10}{10+30} = 6.2$$

$$V_o = 4 \times 6.2 = 24.8\text{ V.}$$

QUES 8.2.13

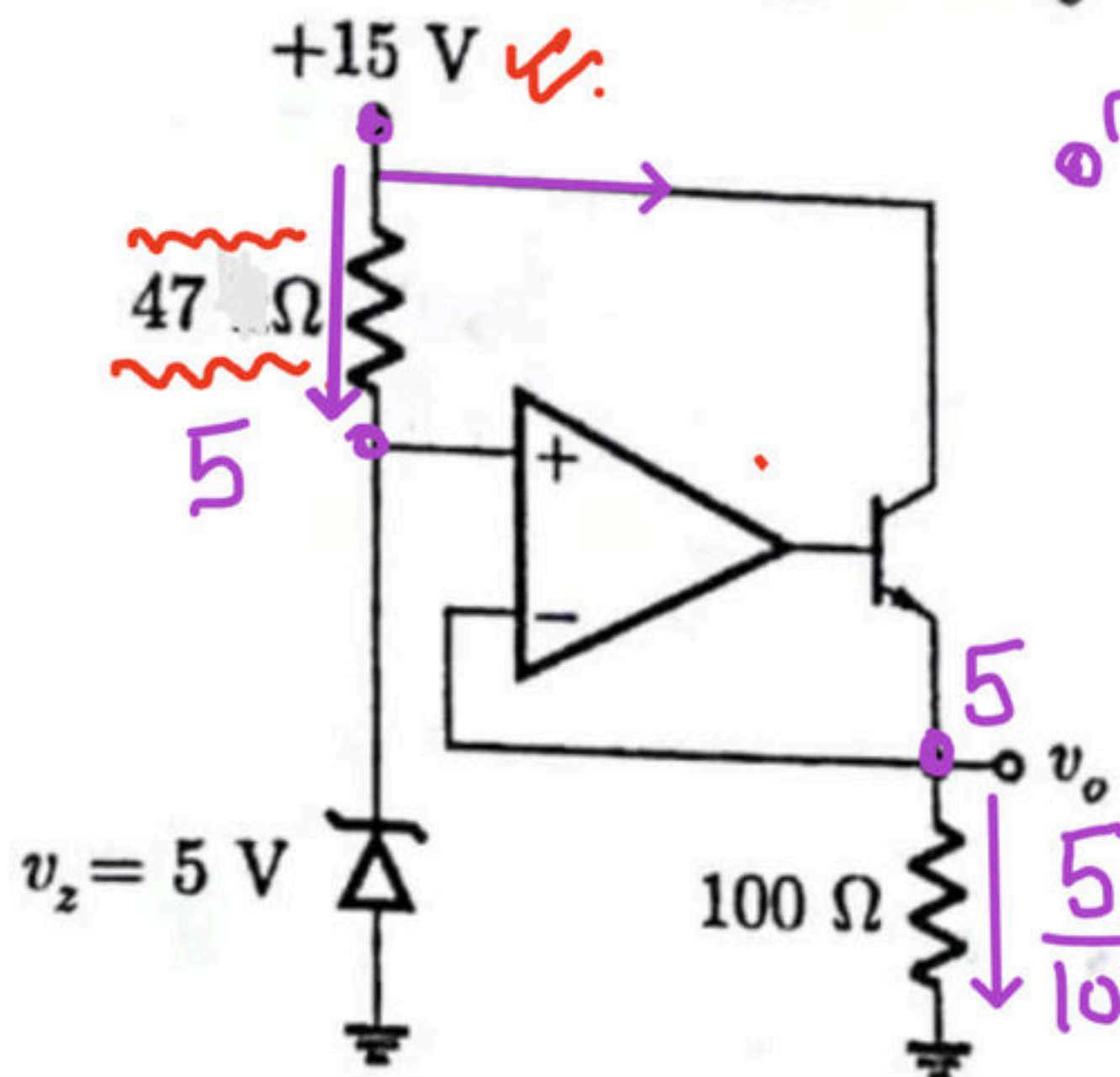In the following circuit, the op-amp is ideal. If $\beta_F = 60$, then the total current (in mA) supplied by the 15-V source is _____



• The v_{k+} is in neg feed back

• Zener in BD

$$\frac{5}{100} = 50\text{ mA}$$

a) 49

b) 152

~~c) 261~~

d) 342

BD


$$I_{\text{supplied by 15V source}} = \frac{15-5}{47} + \frac{5}{100} \times \frac{60}{61}$$

$$= \frac{10}{47} + \frac{5}{100} \times \frac{60}{61}$$

$$= 0.261 \text{ Amp}$$


$$= \underline{\underline{261 \text{ mA}}}$$

11

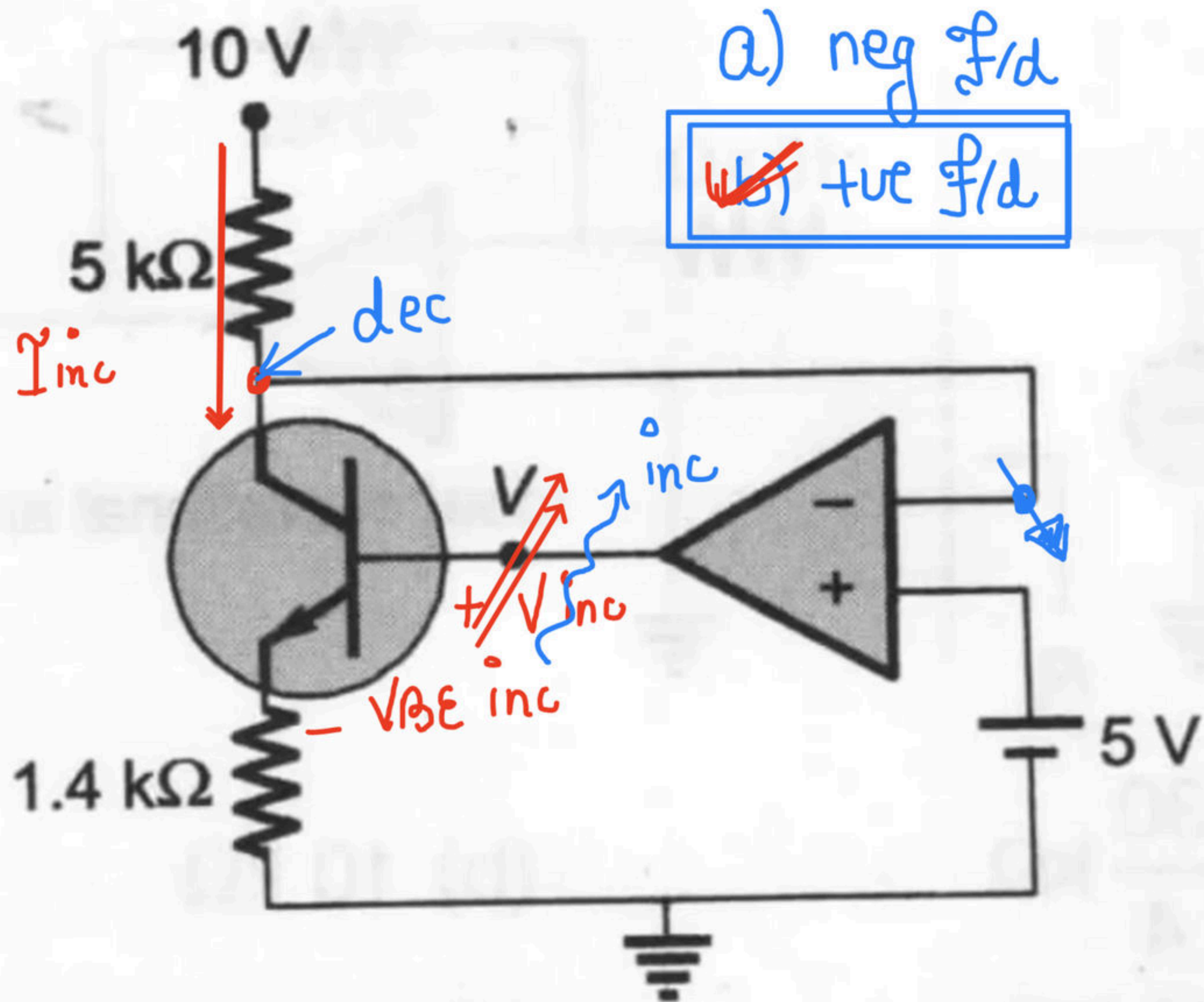

Common Data For Q. 8 and 9 :

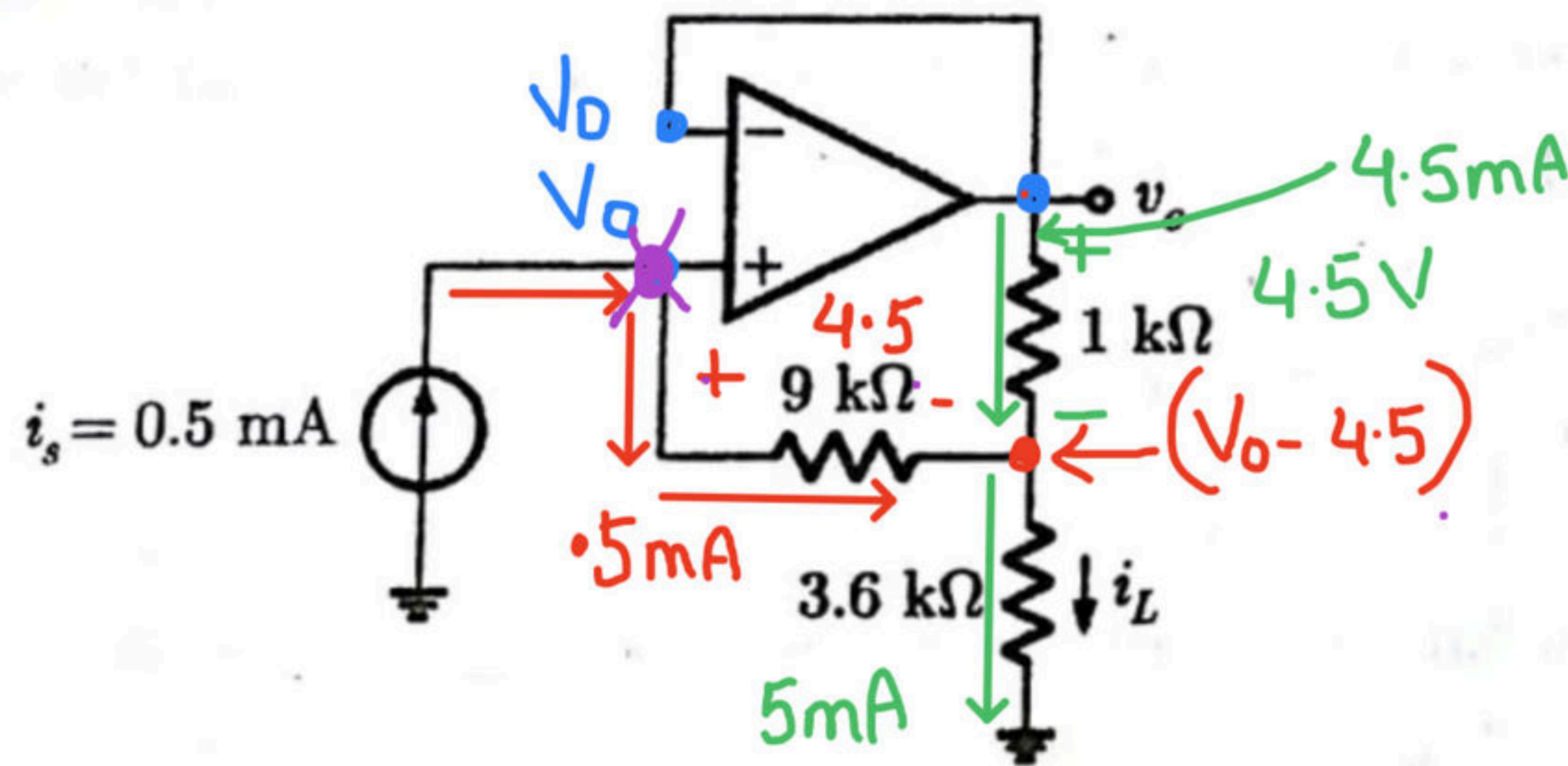An ideal op-amp circuit is shown in figure



$$V_o = 4.5 + 18$$

$$V_o = 22.5V \quad Z = V_o/i_o$$

- a) 22.5 ~~b) 45~~
- c) 67.5 d) 90

QUES 8.2.8

Current i_L is 5mA mA.



QUES 8.2.9

In above circuit, input impedance (Z_{in}) seen by the current source is _____ kΩ

Q

Common Data For Q. 6 and 7 :

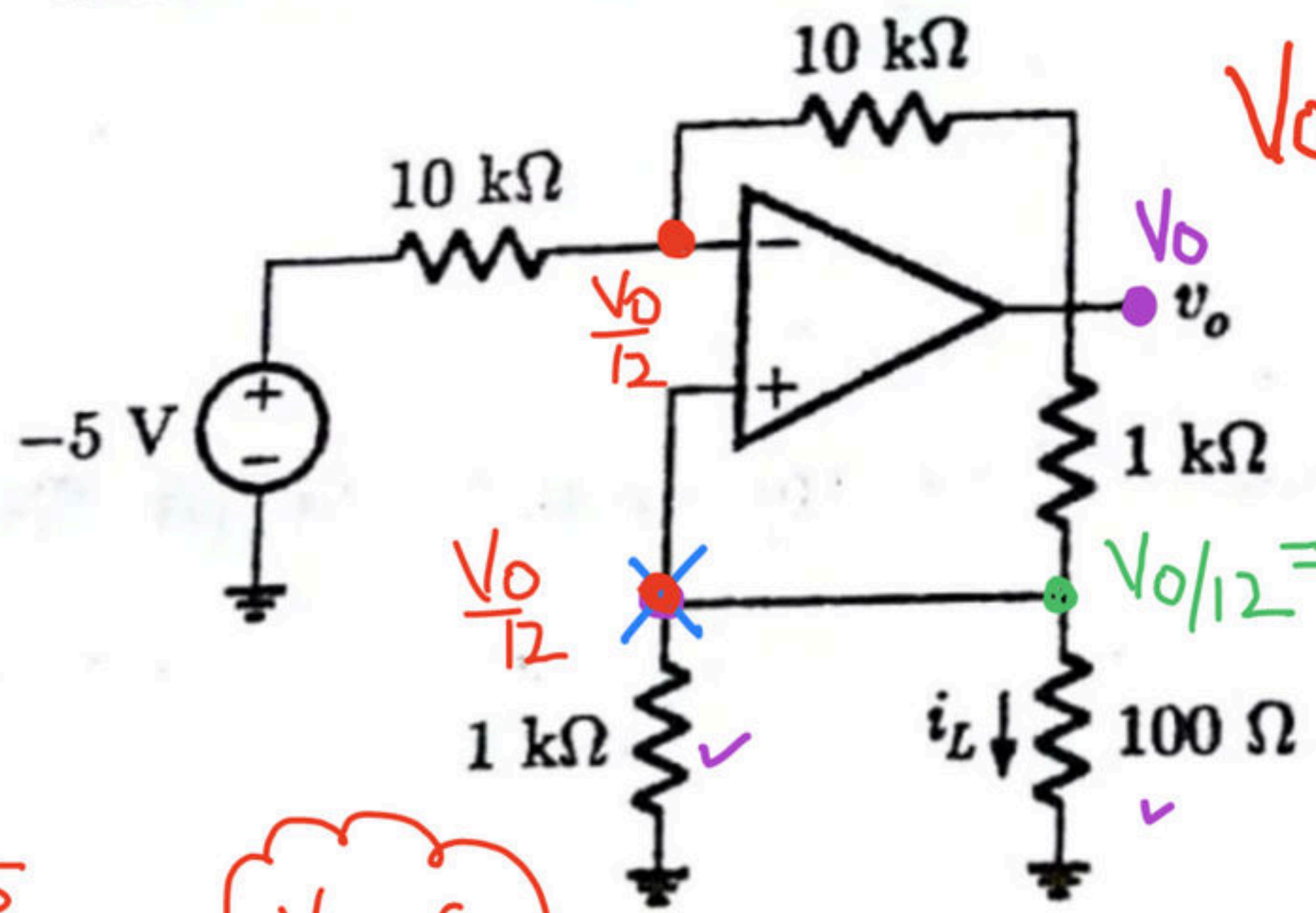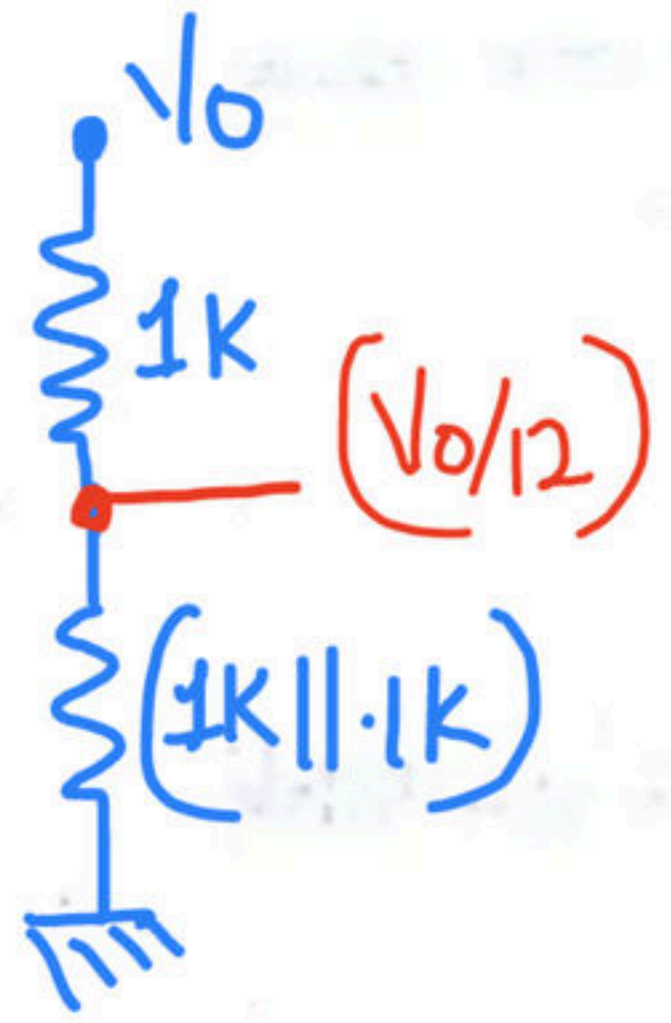Consider ideal op-amp circuit shown below.



- $v_o \Rightarrow$ ~~a) 6~~
b) 12
c) 8
d) 4

$$\frac{v_o - \frac{v_o}{12}}{10k} = \frac{\frac{v_o}{12} + 5}{10k}$$


$v_o = 6V$

$$i_L = \frac{5}{100} = \frac{5}{1000} = \underline{\underline{5mA}}$$

QUES 8.2.6 Load current i_L is _____ mA.

QUES 8.2.7 Output voltage v_o is _____ volts.


#

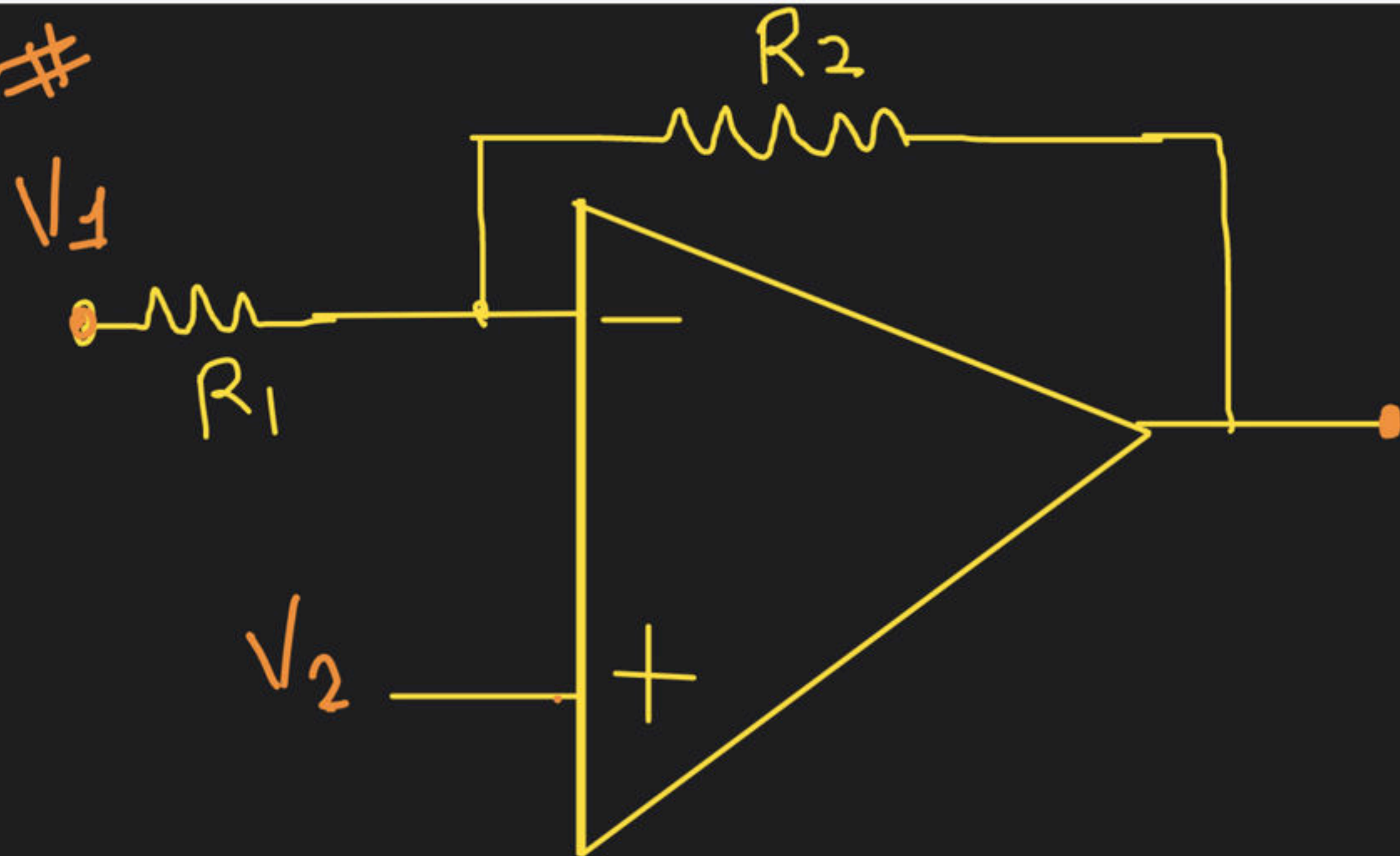

$$V_2 \left(1 + \frac{R_2}{R_1} \right) + \left(-V_1 \frac{R_2}{R_1} \right)$$

Q
QUES 8.2.19

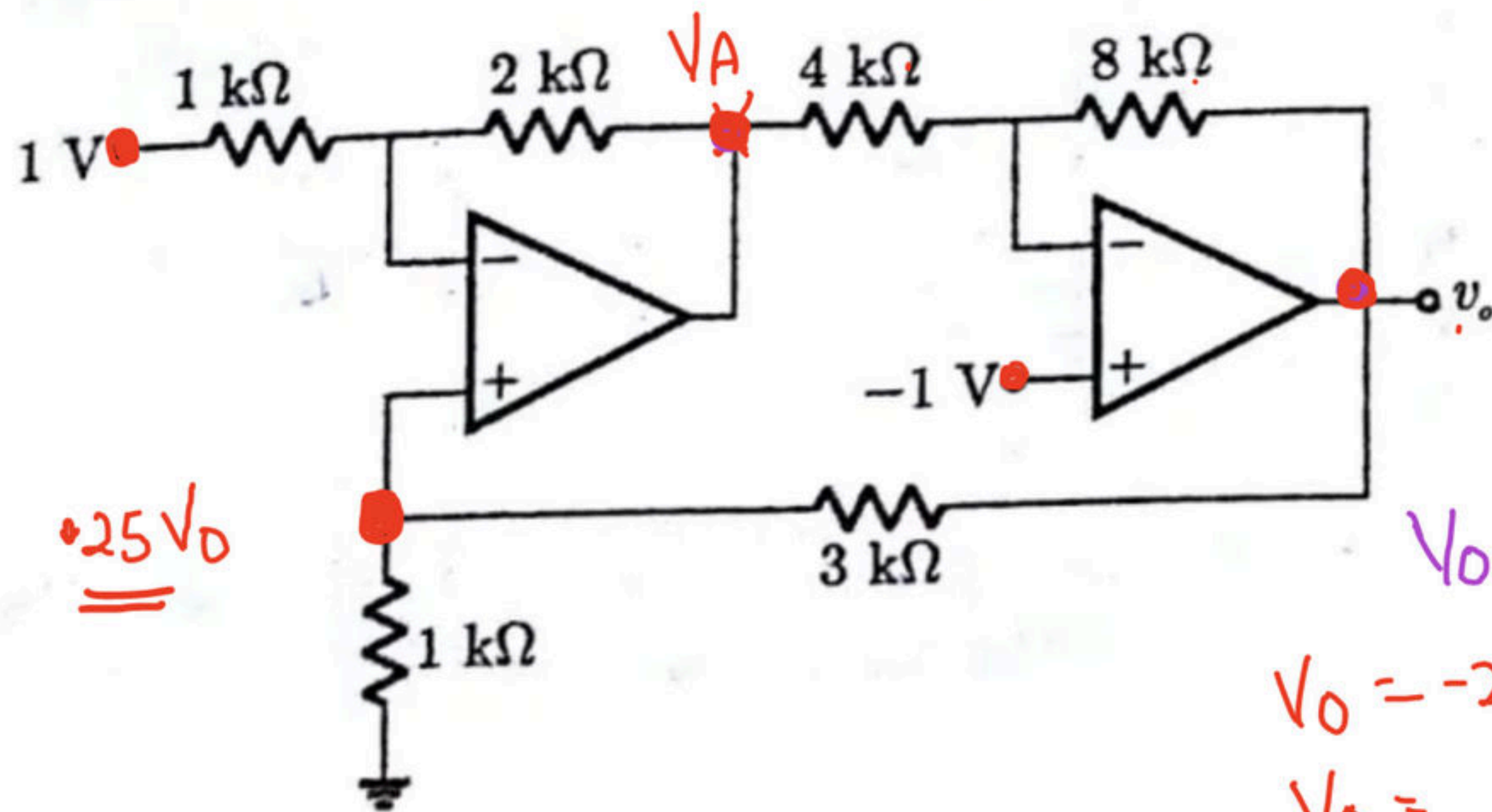For the op-amp circuit shown in figure. Assume that the op-amps are ideal.
The output voltage v_o is _____ volt.



$$V_A = -2 + \frac{V_o}{4}(1+2)$$

$$V_A = -2 + 0.75V_o$$

$$0.25V_o$$

$$V_o = -2V_A - 1(3)$$


$$V_o = -2(-2 + 0.75V_o) - 3$$

$$V_o = 4 - 1.5V_o - 3$$

$$V_o = \frac{1}{2.5} = 0.4$$

QUES 8.2.19

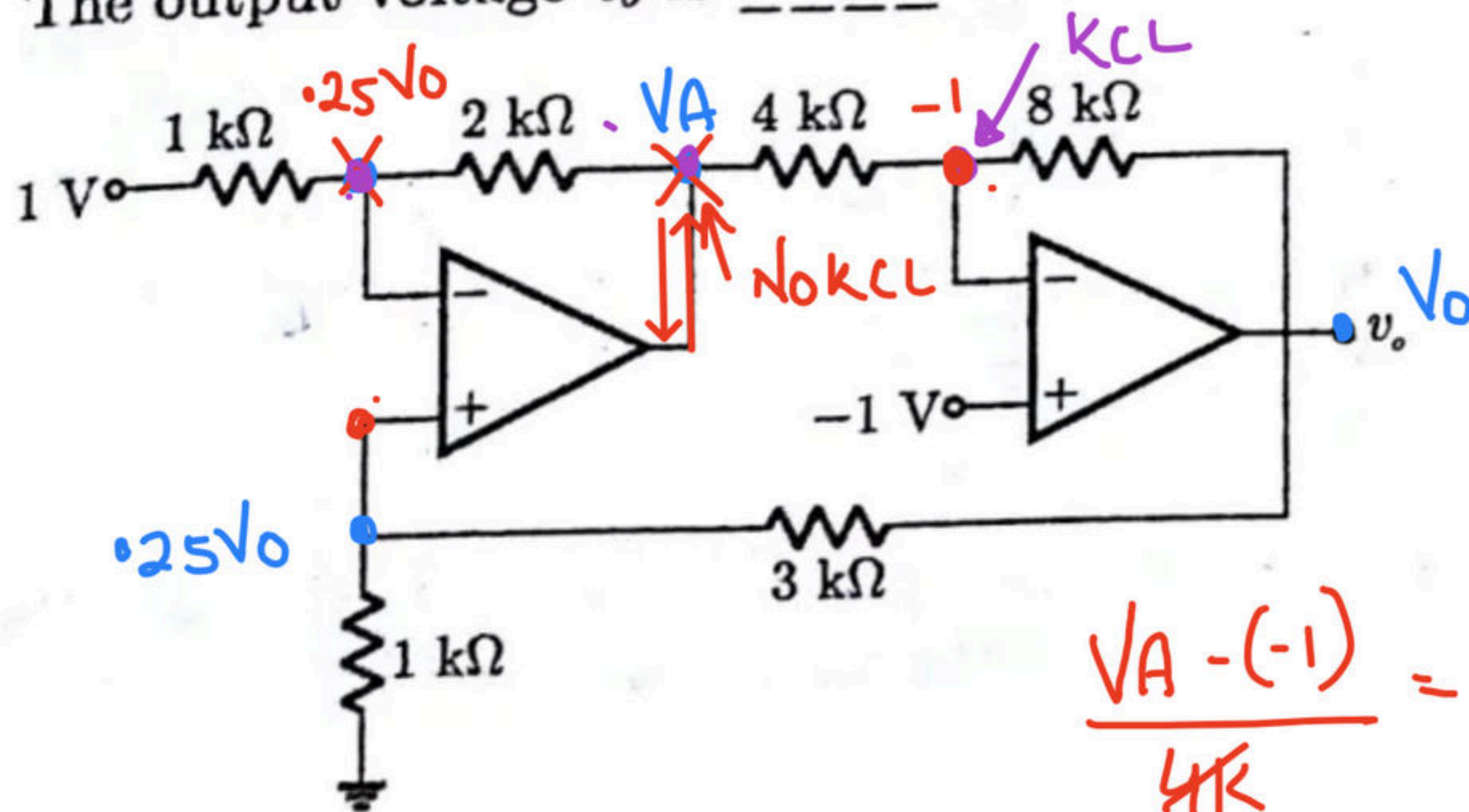For the op-amp circuit shown in figure. Assume that the op-amps are ideal.
The output voltage v_o is _____ volt.



$$\frac{V_A - 0.25V_o}{2k} = \frac{0.25V_o - (-1)}{1k}$$

$$V_A - 0.25V_o = 0.5V_o - 2$$

$$V_A = 0.75V_o - 2$$

$$\frac{V_A - (-1)}{4k} = \frac{(-1) - V_o}{8k}$$

$$2V_A + 2 = -1 - V_o$$

$$1.5\sqrt{0-4} + 2 = -1 - \sqrt{0}$$


$$2.5\sqrt{0} = -1 - 2 + 4$$

$$\boxed{\boxed{\sqrt{0} = \frac{1}{2.5}}}$$

QUES 8.2.24

Q.

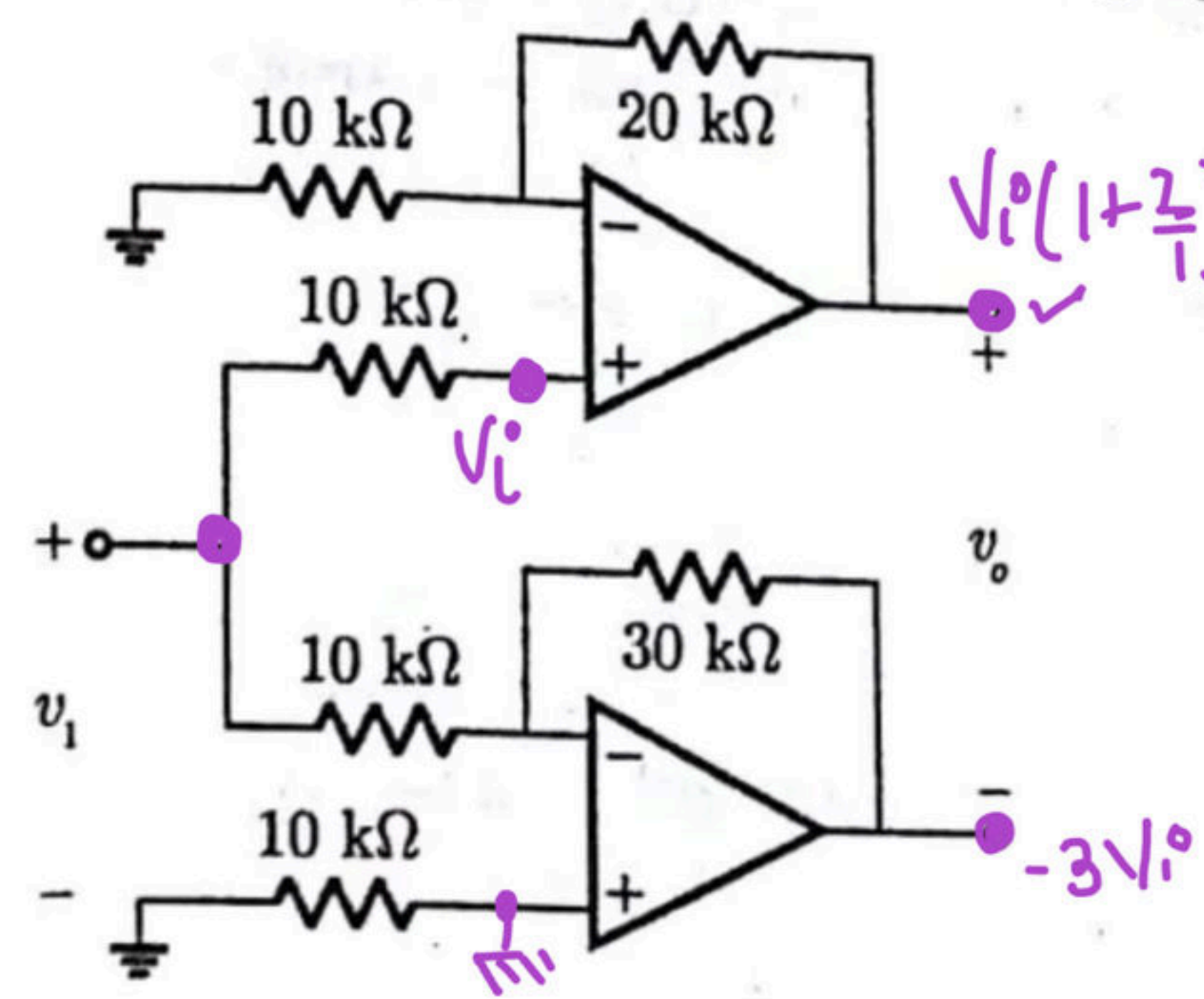Consider the amplifier circuit shown in figure below. Assume op-amp is ideal. What is the value of voltage gain $A_v = \frac{v_o}{v_i}$?



$V_i(1 + \frac{2}{1}) = 3V_i$

a) 5

~~b) 6~~

c) -5



d) -6

$$V_o = 3V_i - (-3V_i)$$





$$= 6V_i$$


MCQ 8.1.45

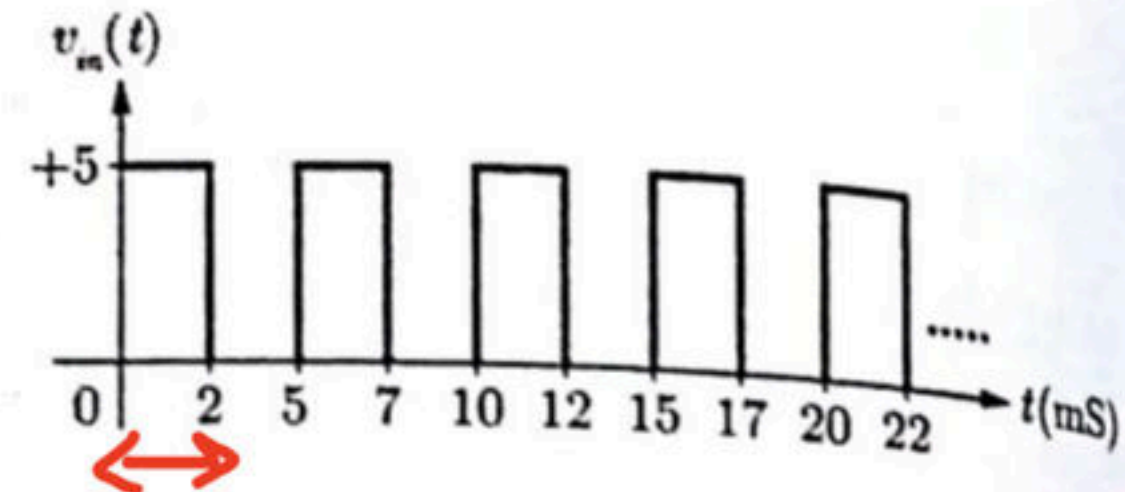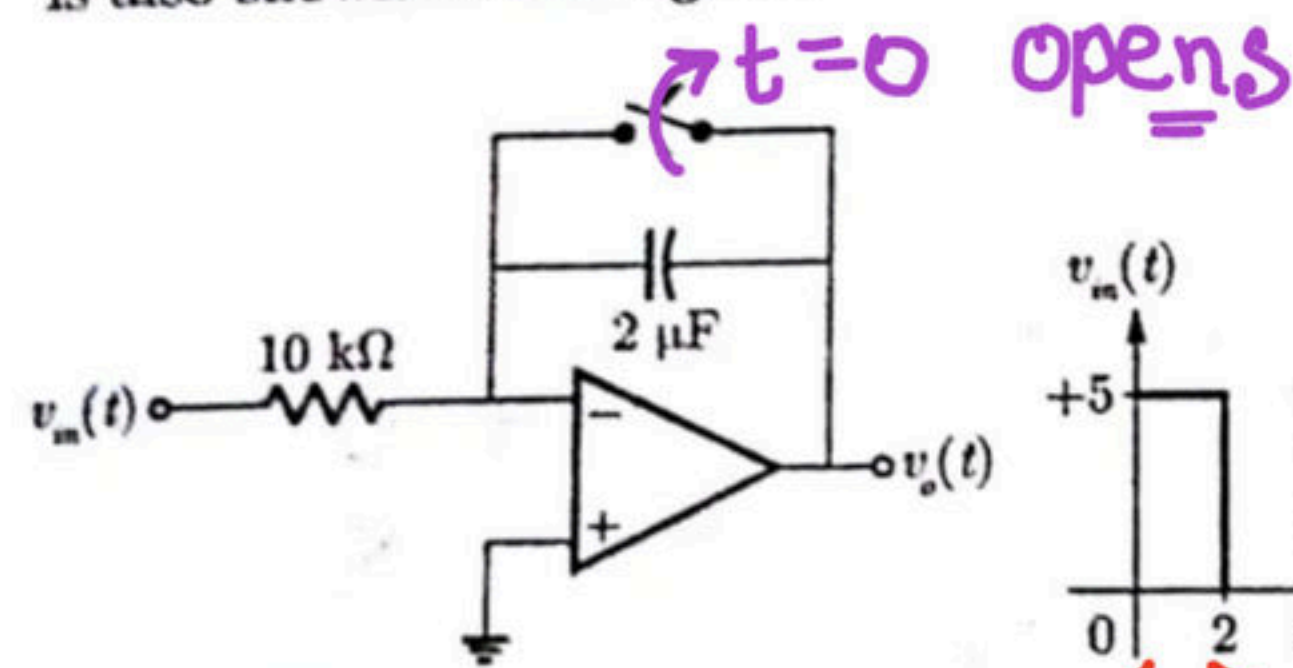Consider the circuit shown in below. Assume op-amp is ideal. Input waveform is also shown in this figure.



The output waveform will be

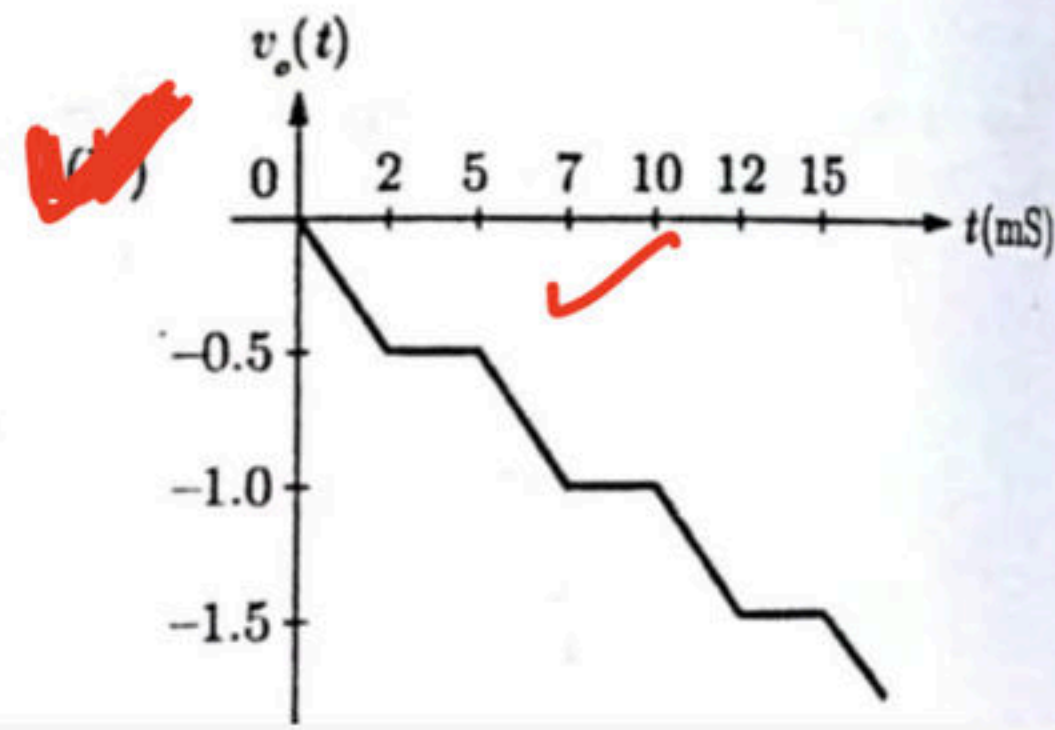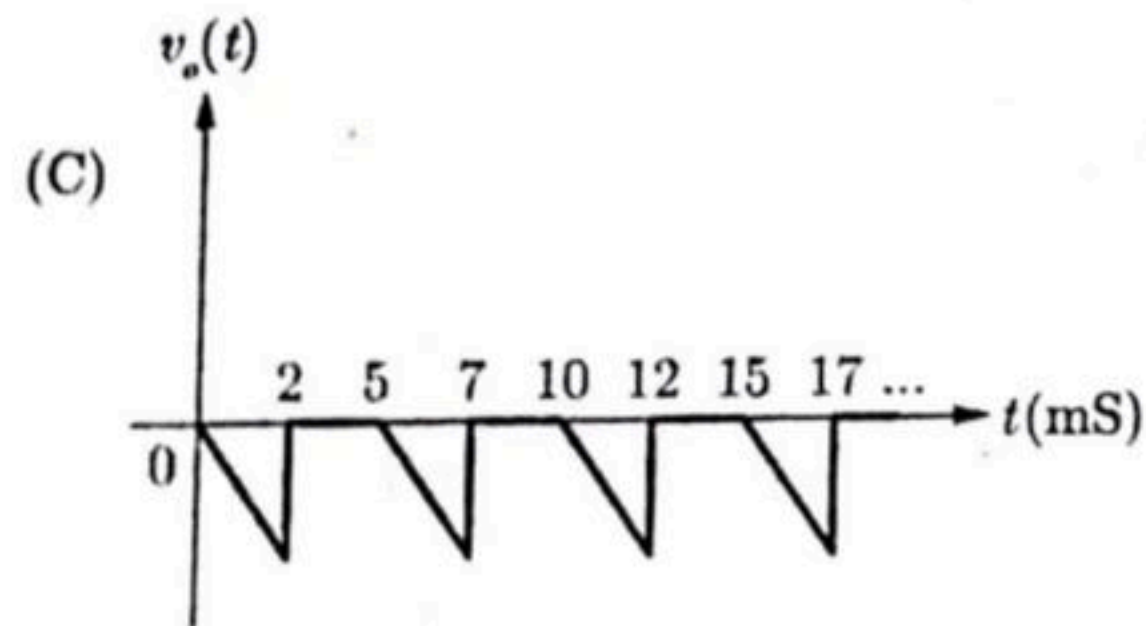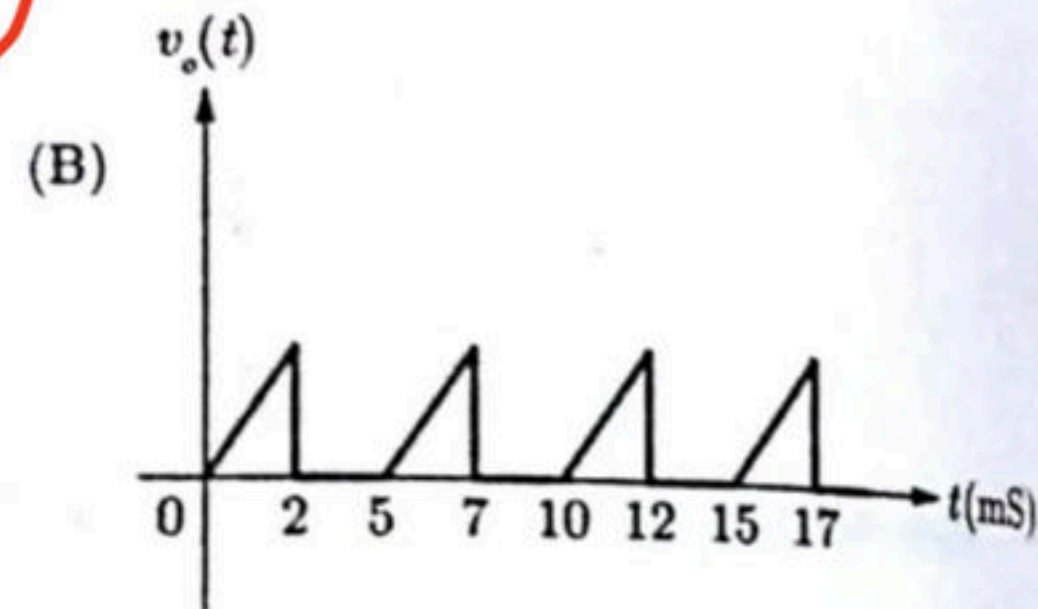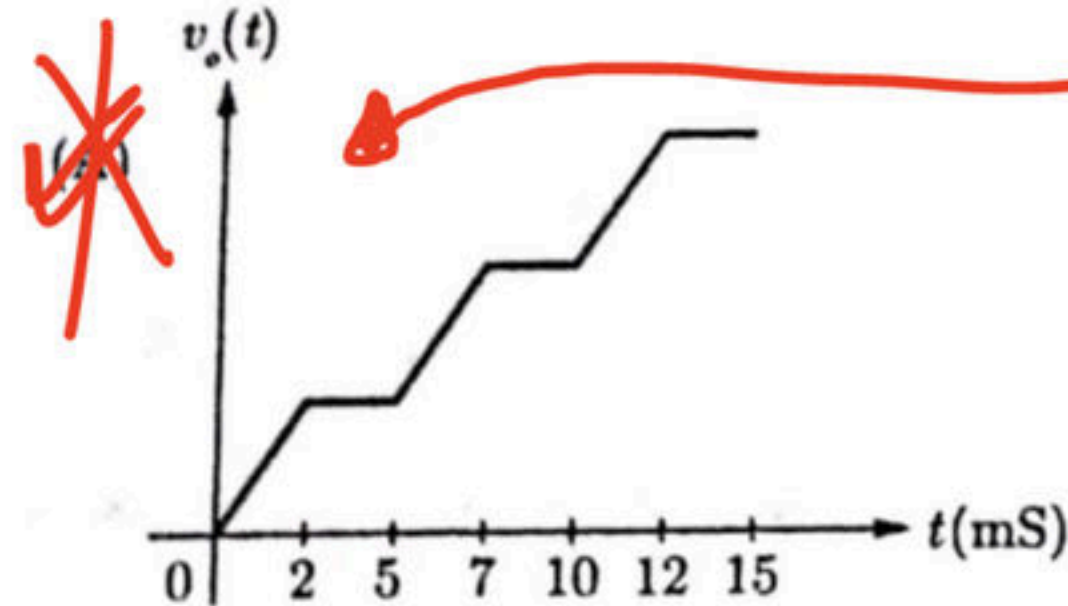

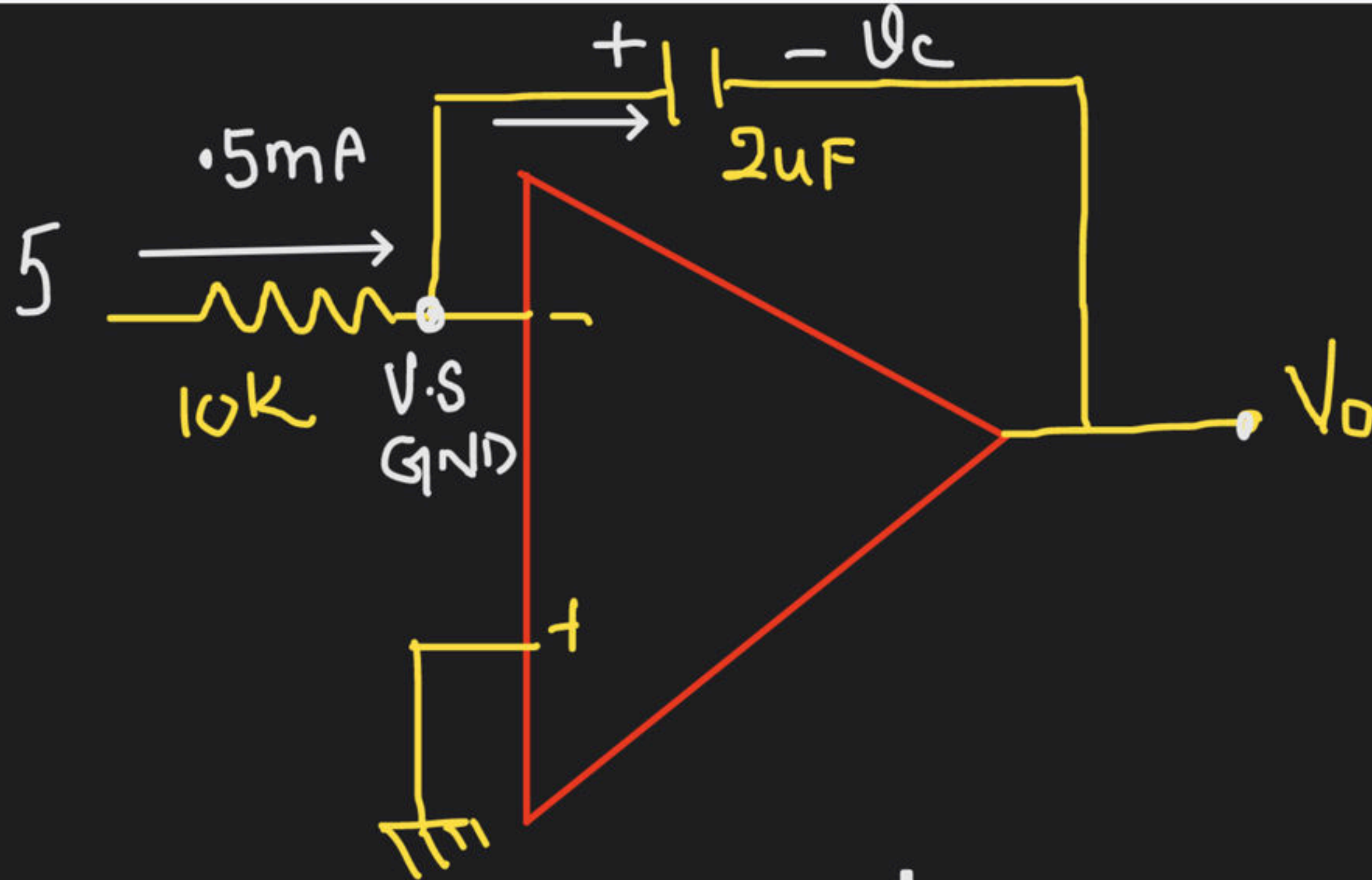


$$V_c = \frac{1}{C} \int i dt$$

$$V_c = \frac{1}{2 \times 10^{-6}} \cdot 5 \text{mF} \cdot t$$

$$V_c = \frac{t}{4} \times 10^3$$


$$V_o = -V_c = -\frac{t}{4} \times 10^3$$



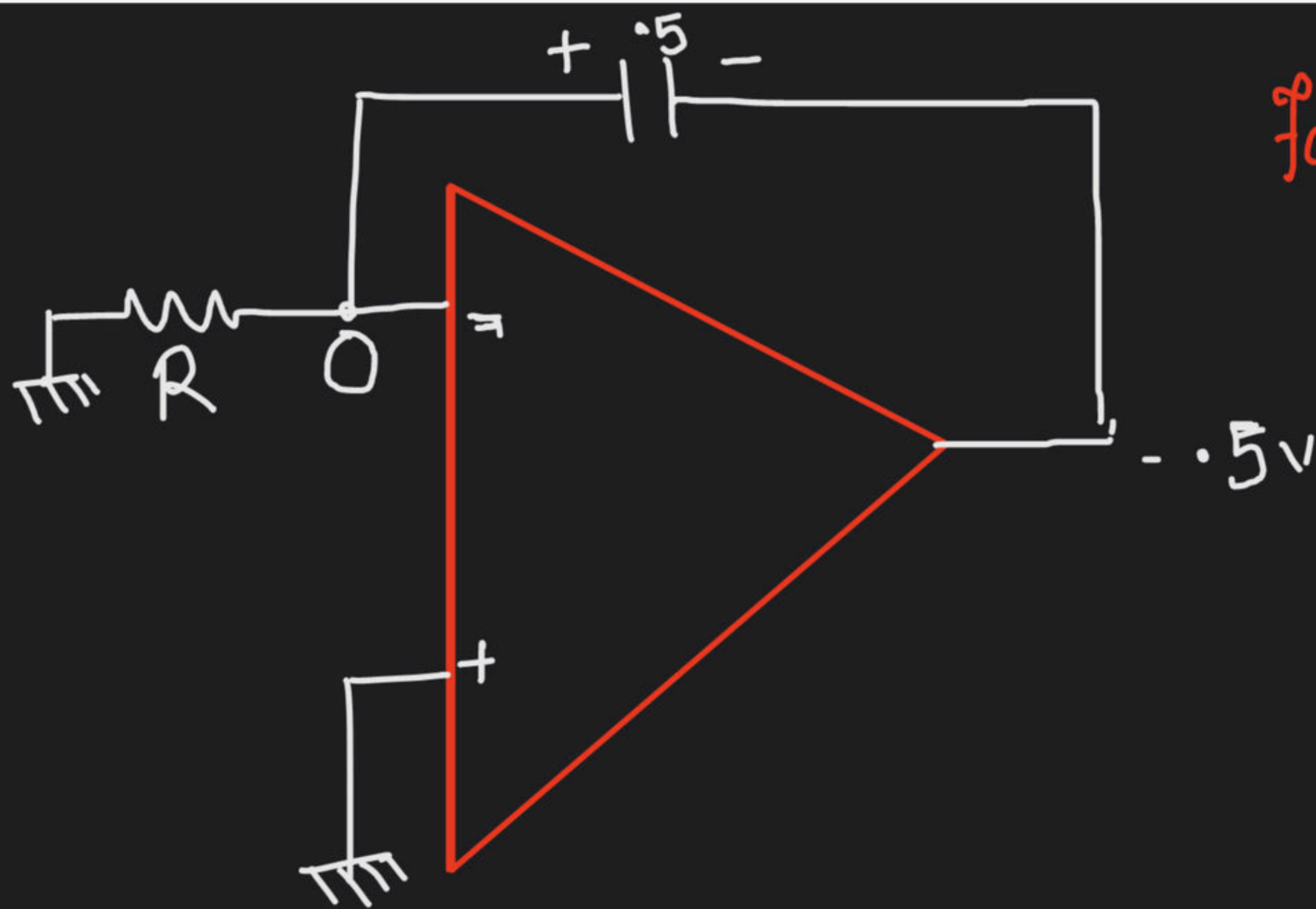


from 2 - 4ms
Cap. has no path to
discharge
C

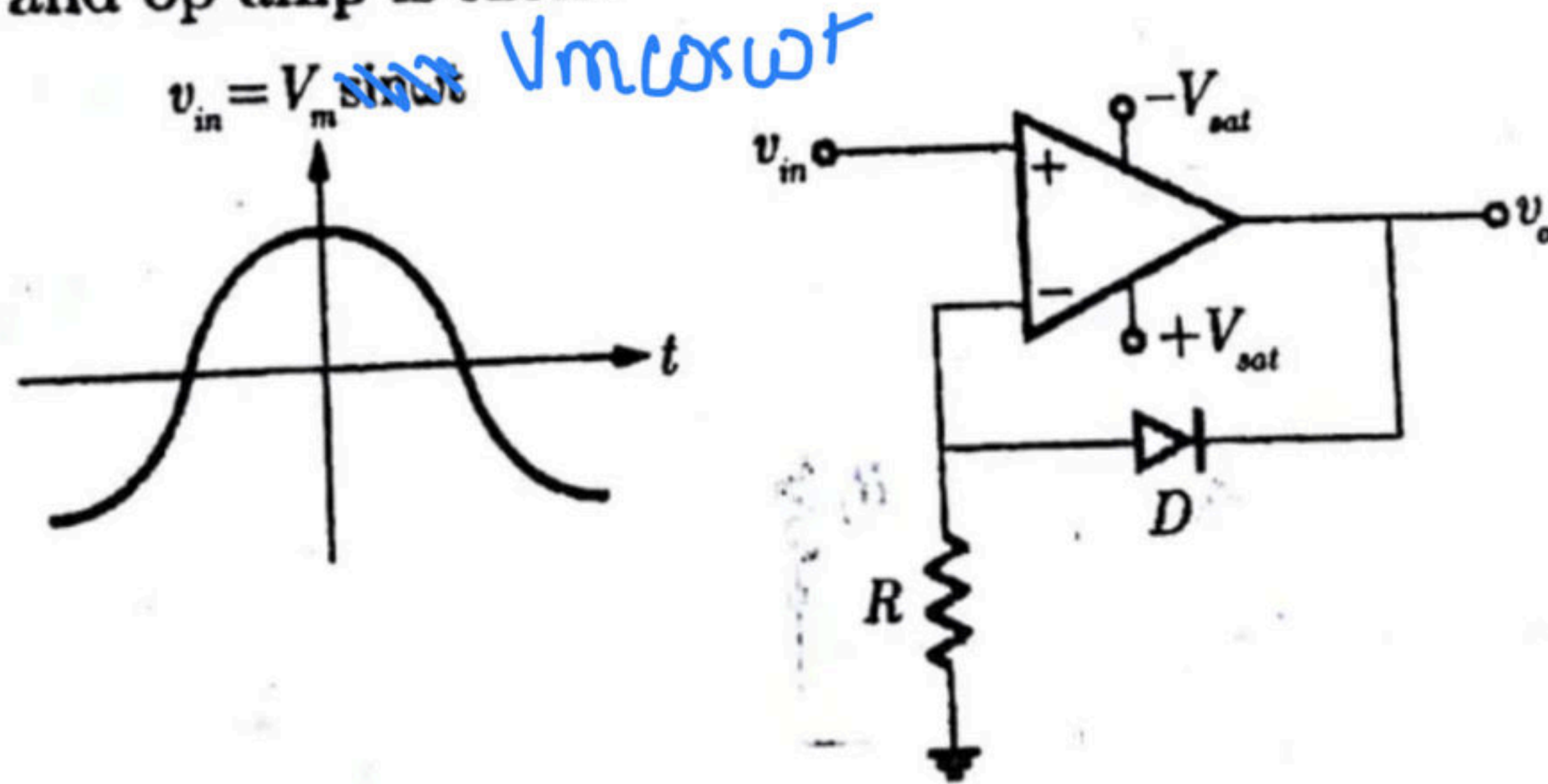MCQ 8.1.50 Consider the circuit shown in figure below. Cut in voltage of diode is 0.7 V and op-amp is ideal.



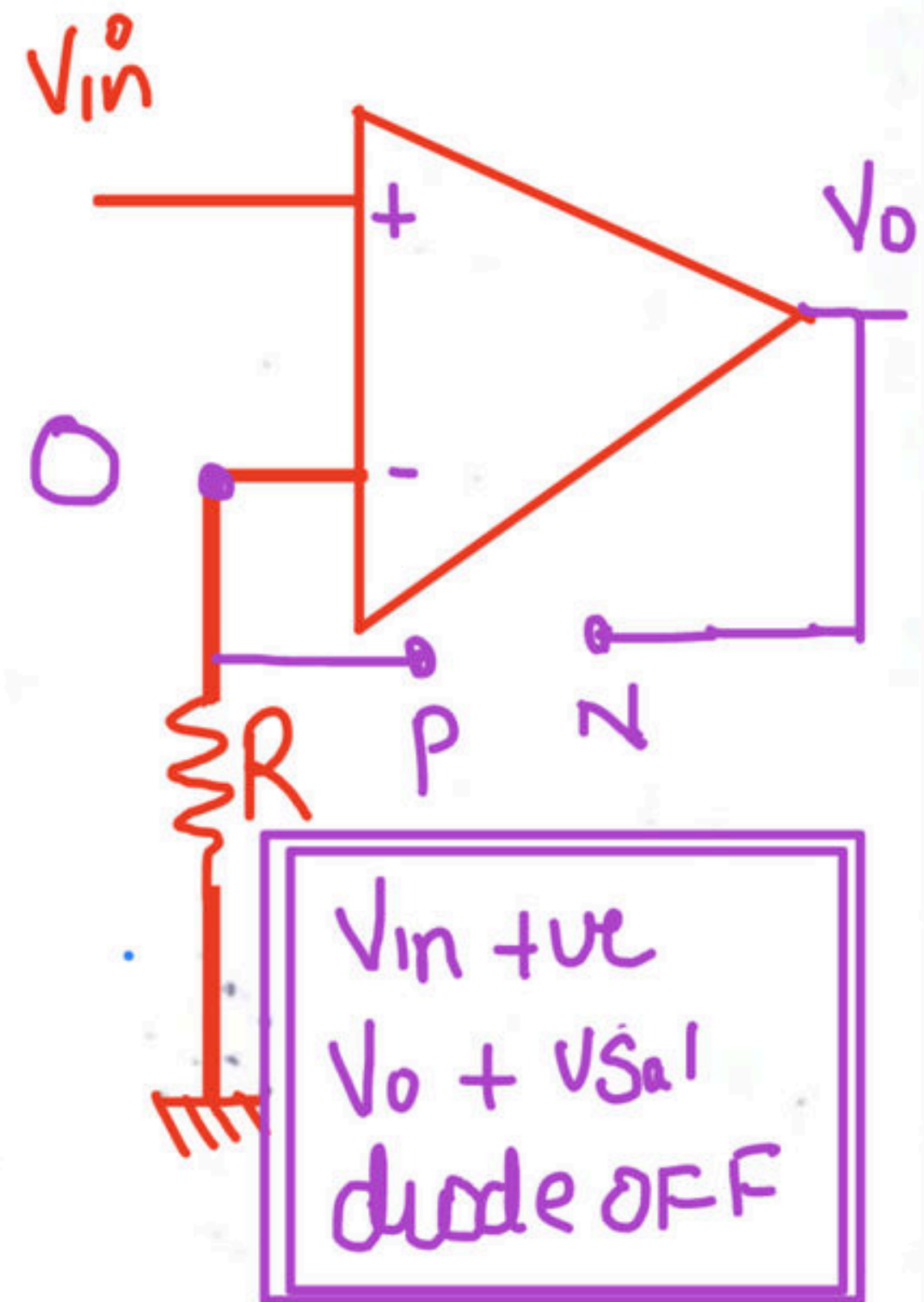If $V_{in} = V_m \cos \omega t$, then the output waveform V_{out} is




$V_{in} > 0 \quad V_o = +V_{sat}$


"diode OFF"

and simply when $V_{in} = -ve$ diode on.

$V_{in} = -ve$

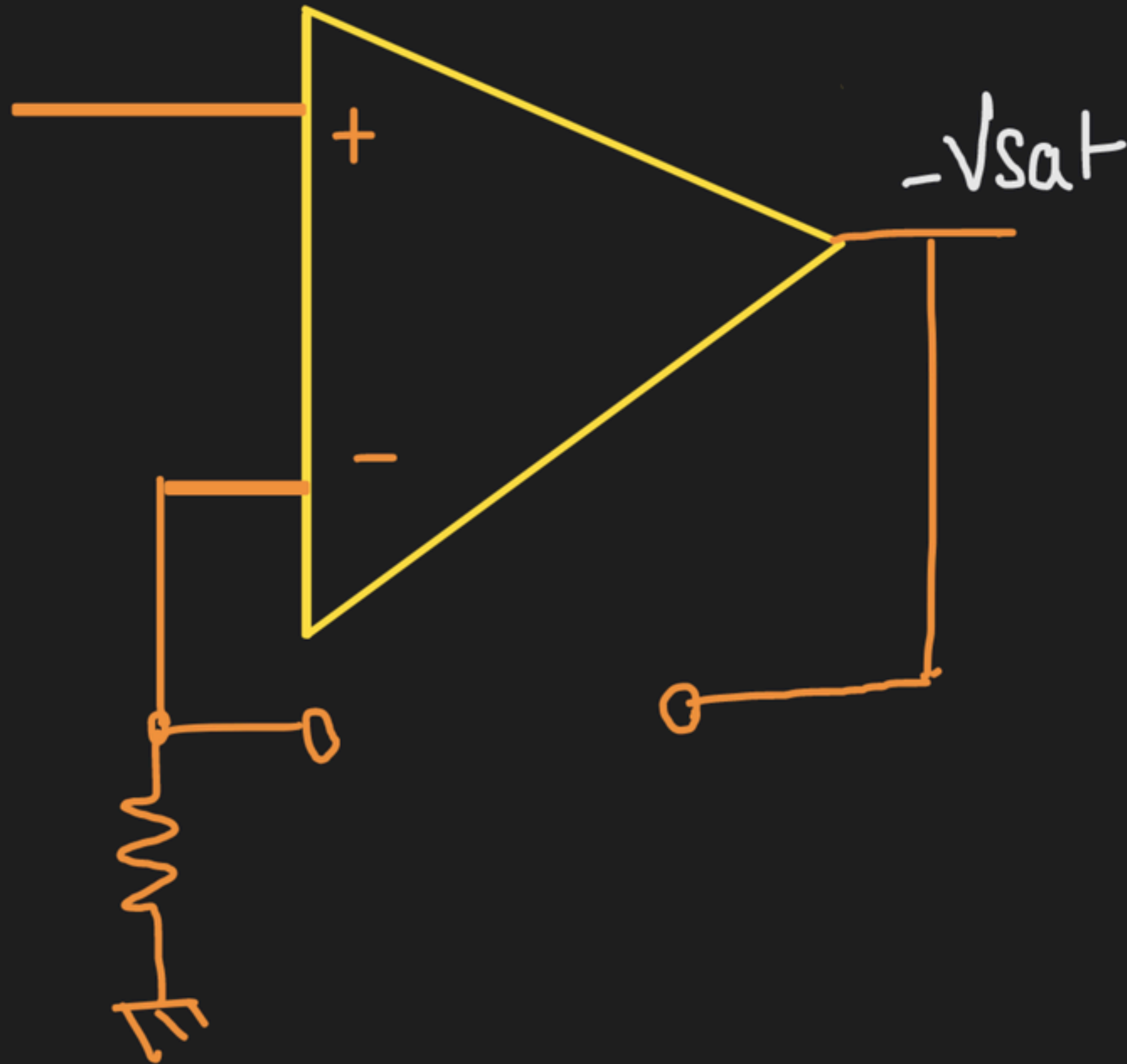


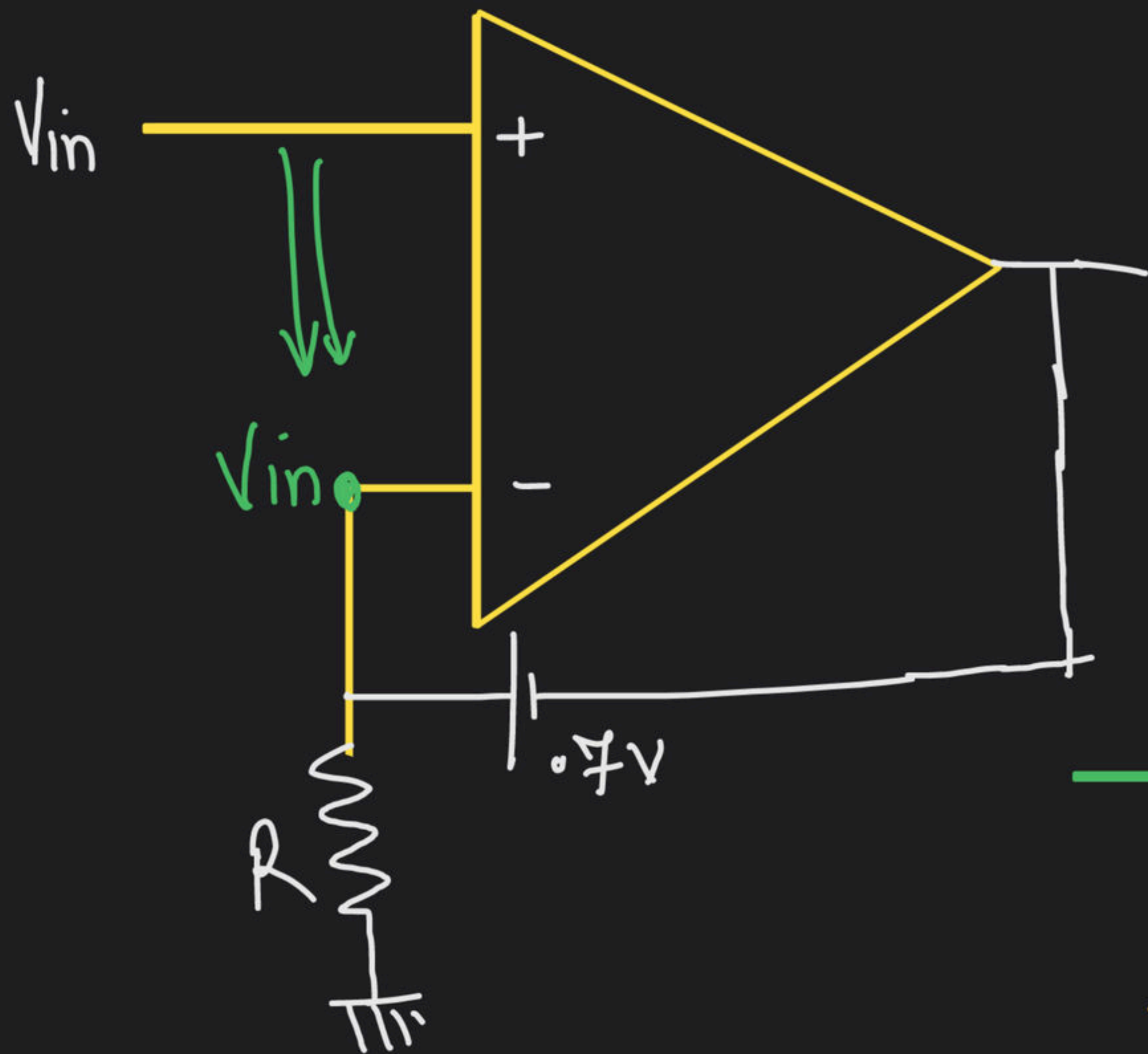
no effect of diode
cut in, diode
on $V_{in} < 0$




So $V_{in} < 0$ diode on


$$V_o = \underline{V_{in} - 0.7}$$

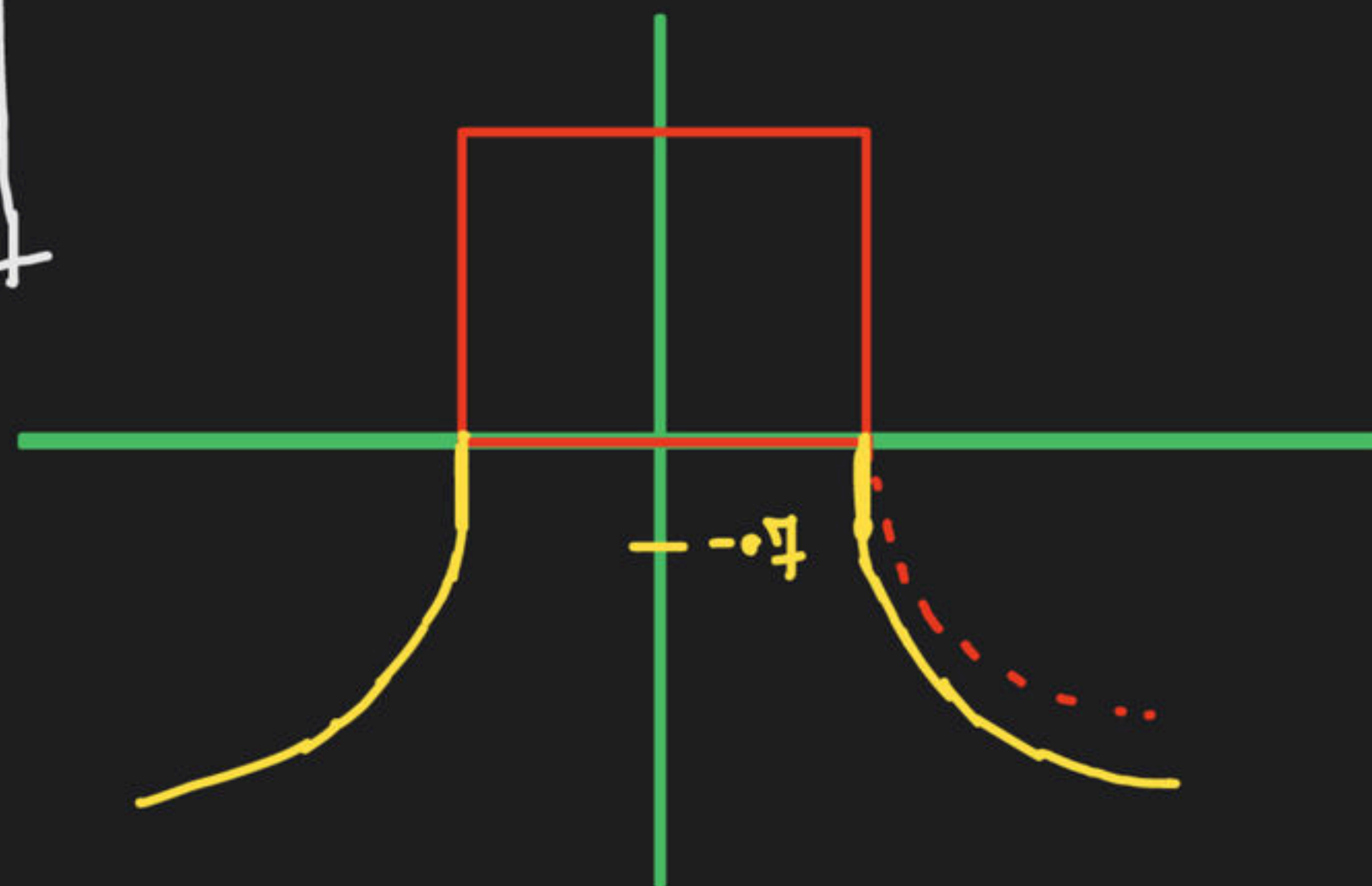

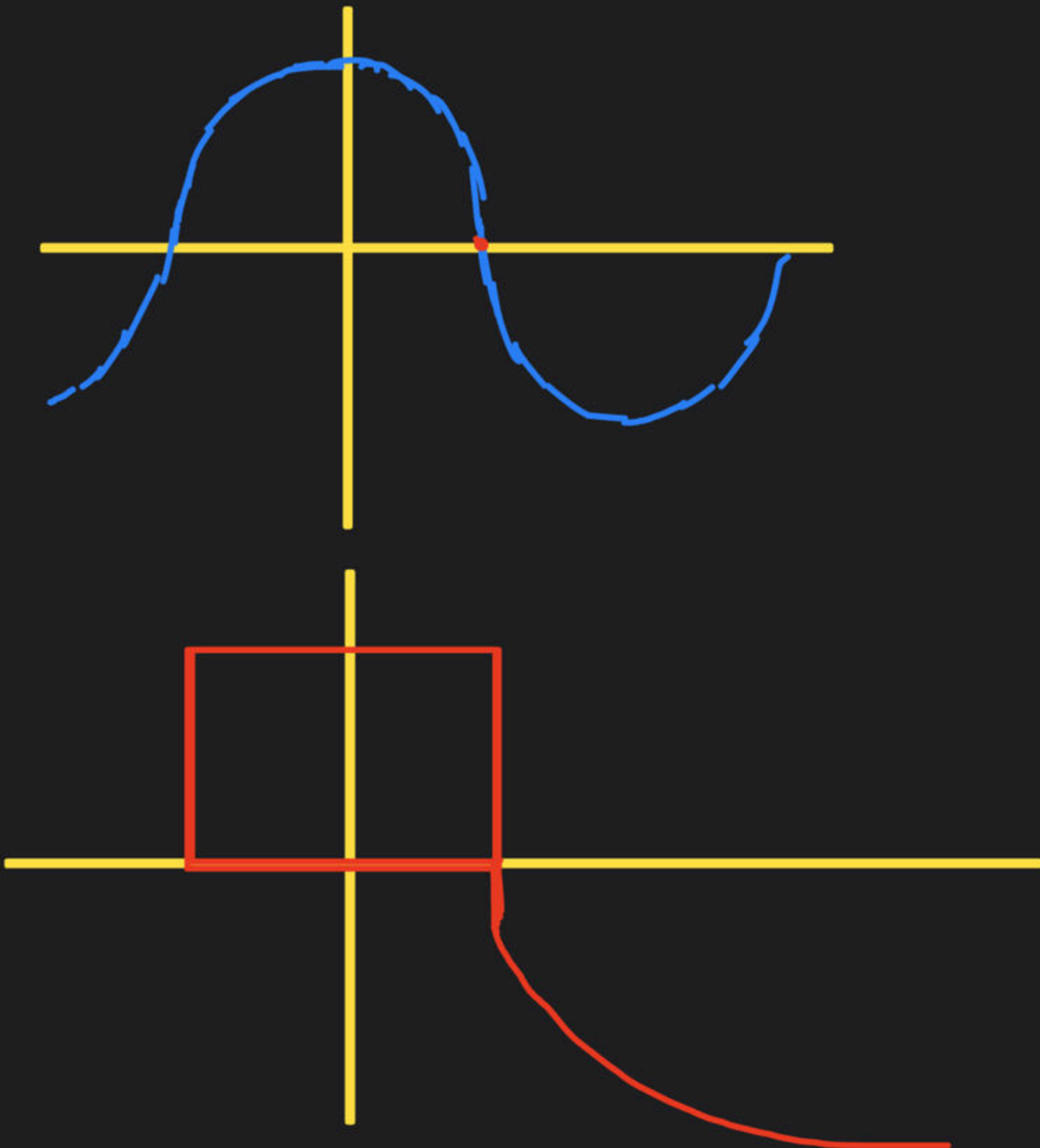


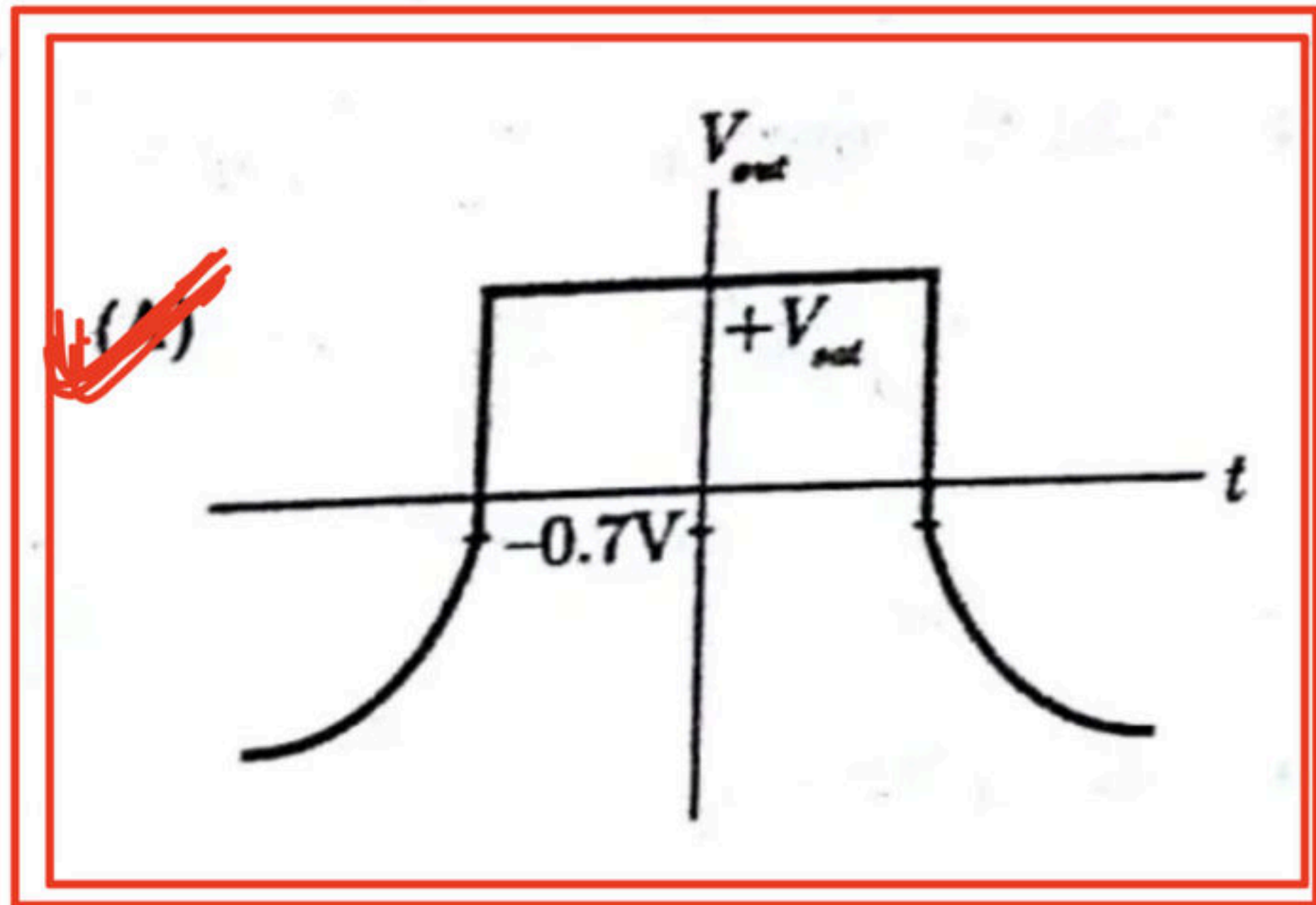


(B)

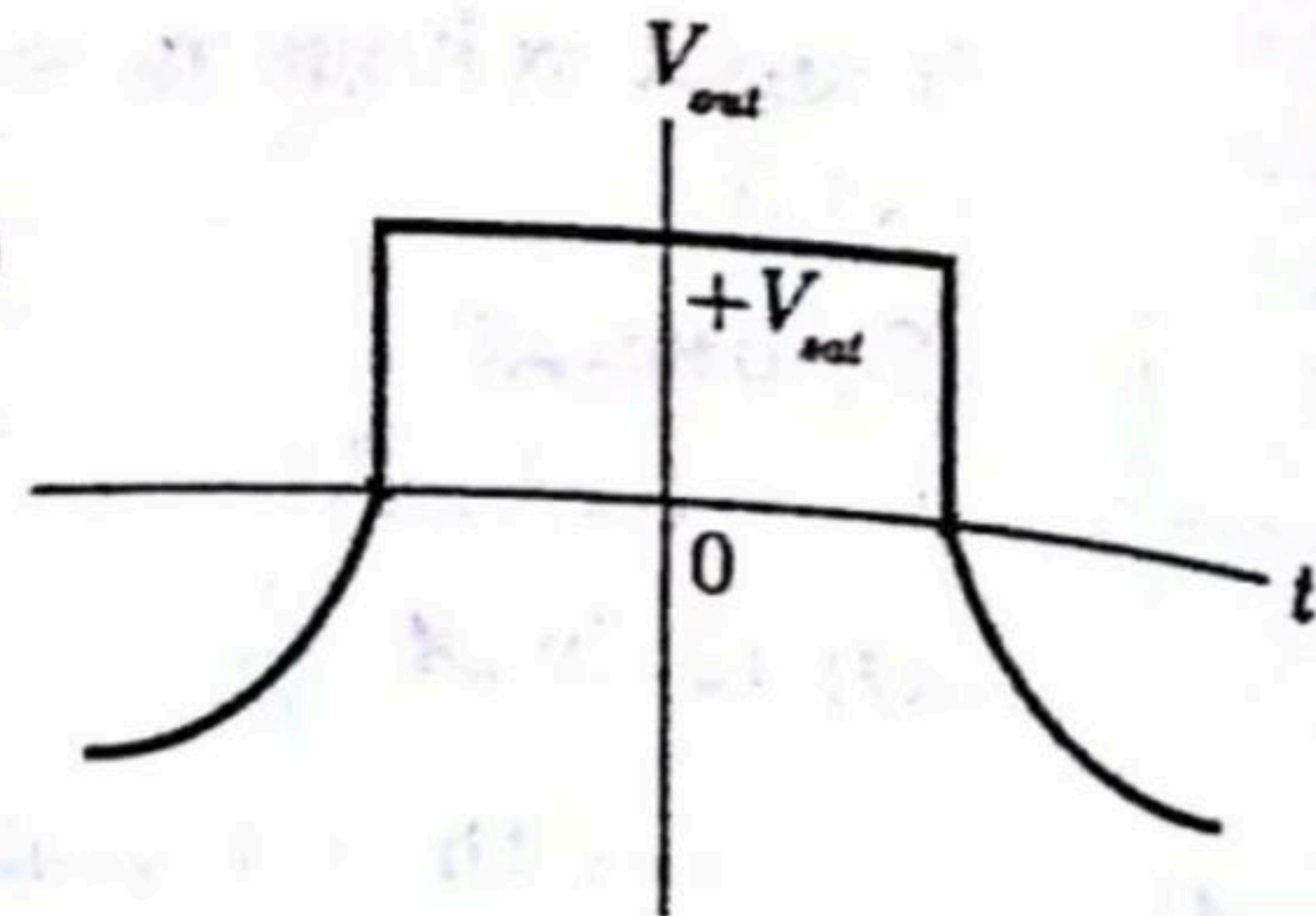

(C)

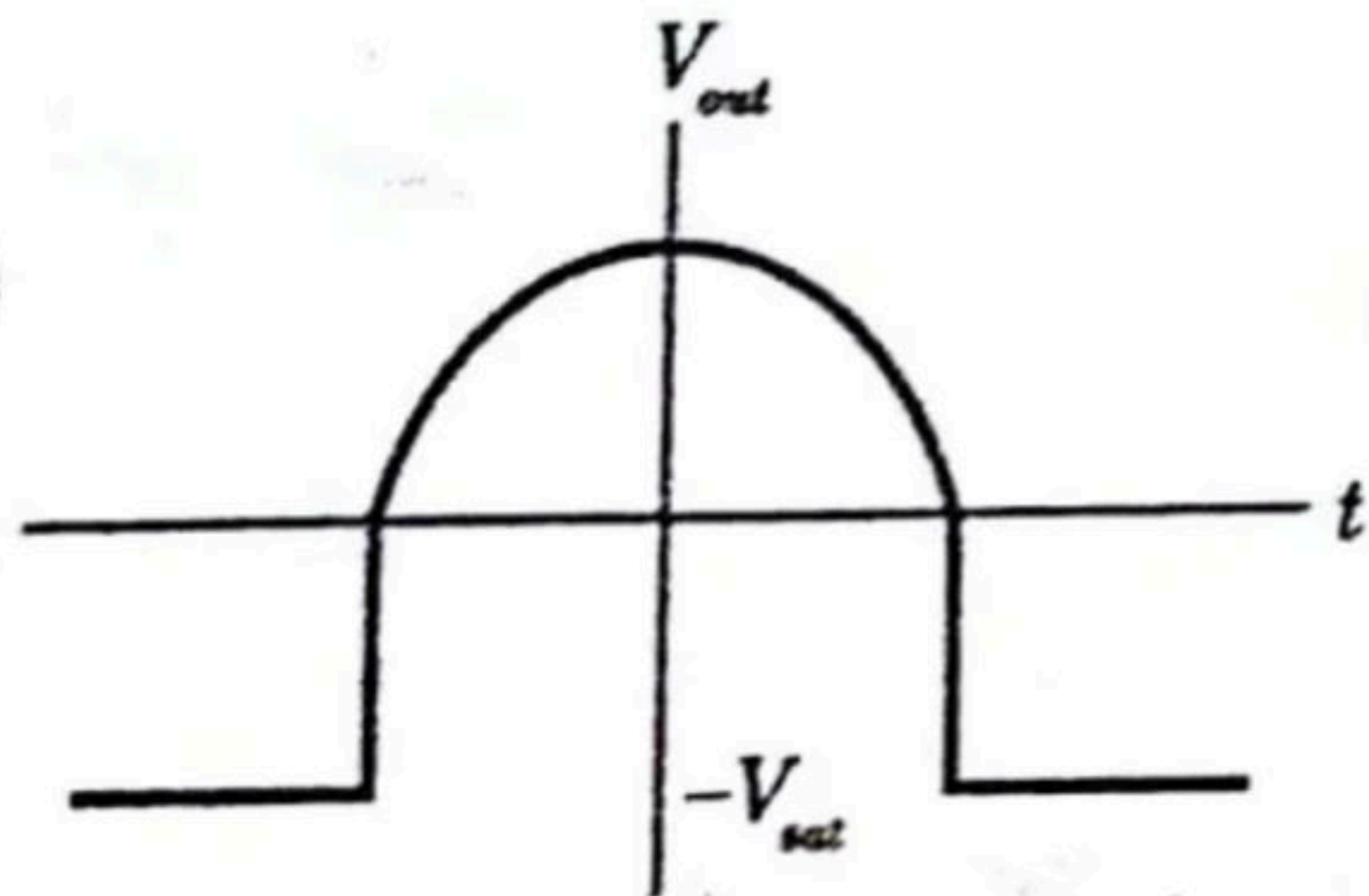


(D)

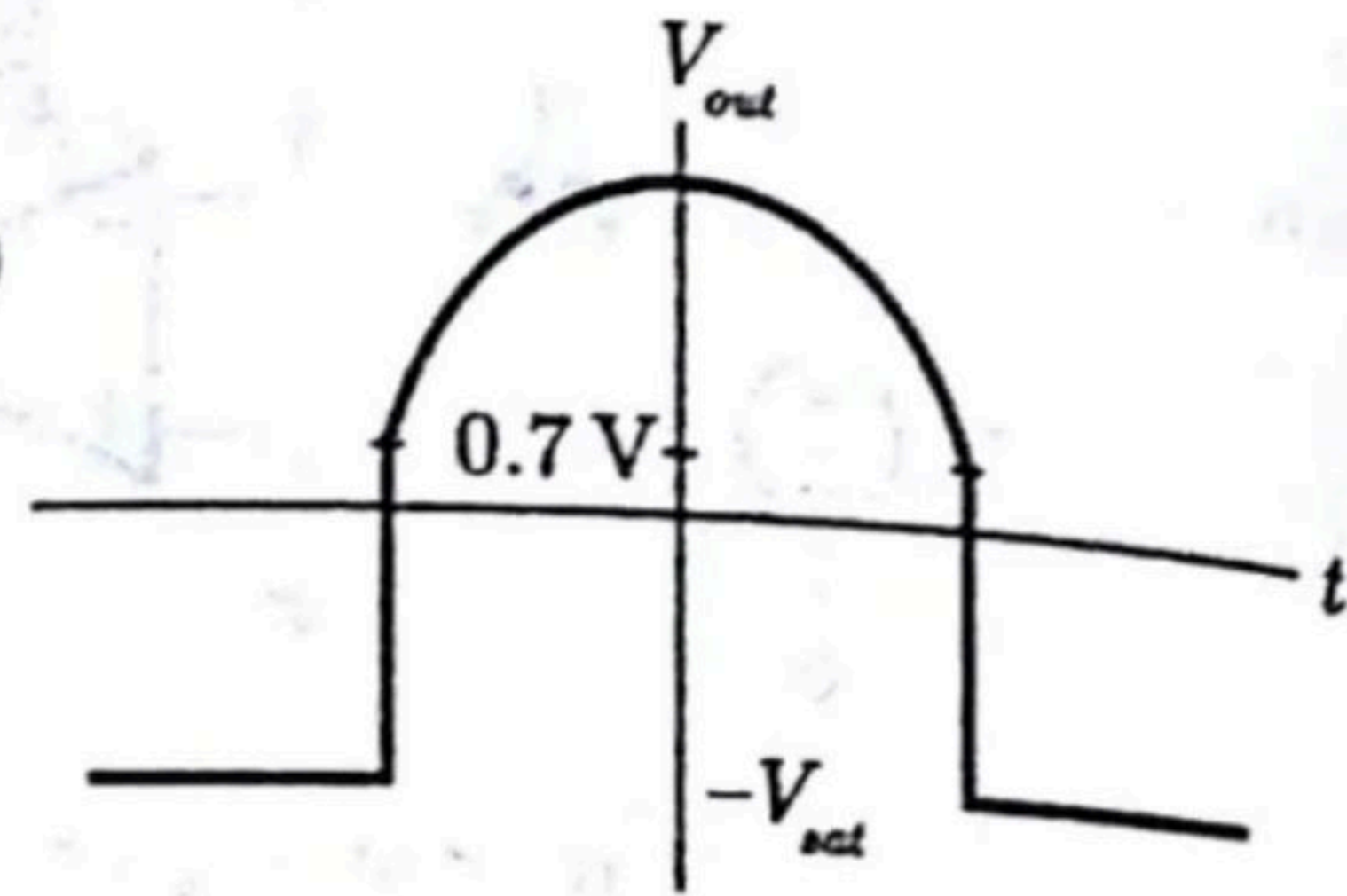





MCQ 8.1.51

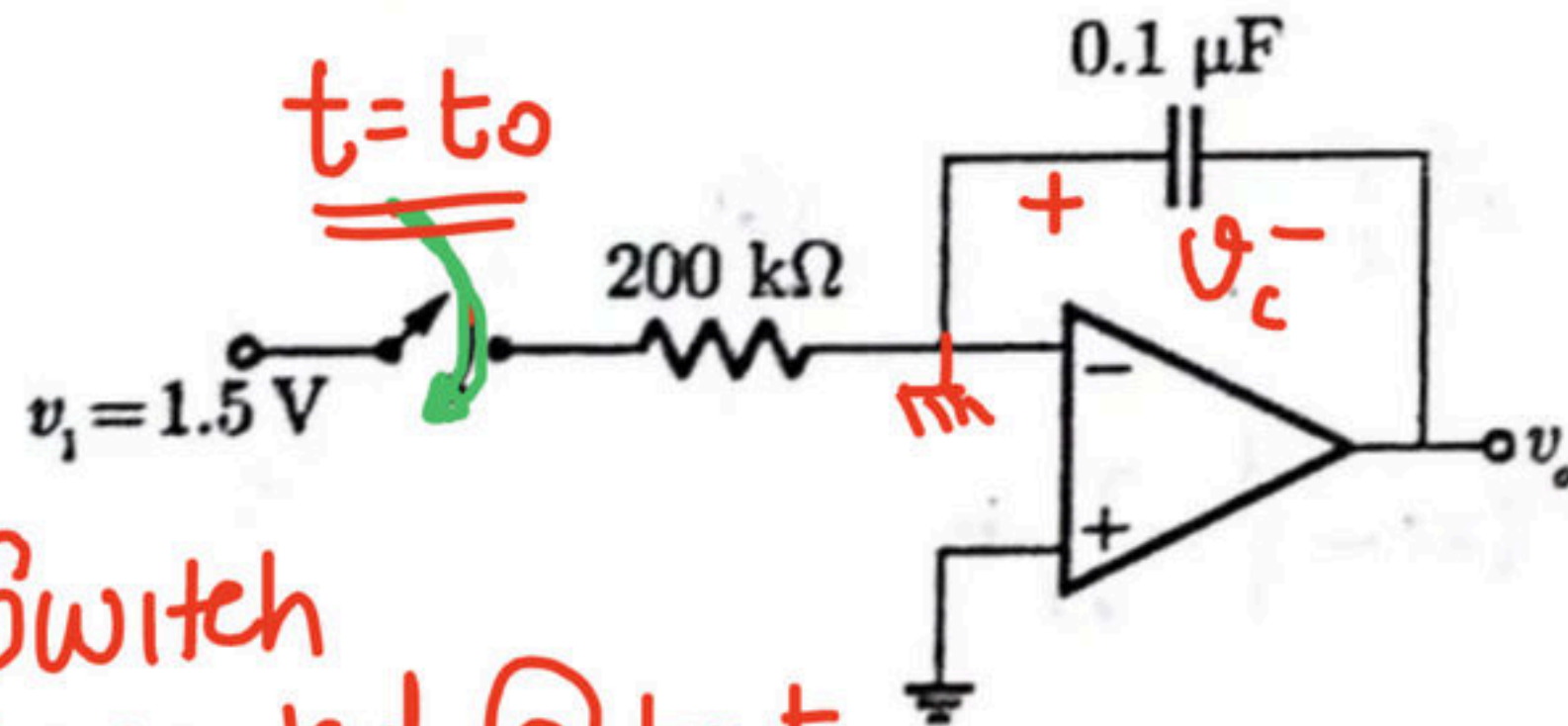Consider the circuit shown in figure below. Assume op-amp is ideal.



Switch
Connected @ $t = t_0$

The output wave form is

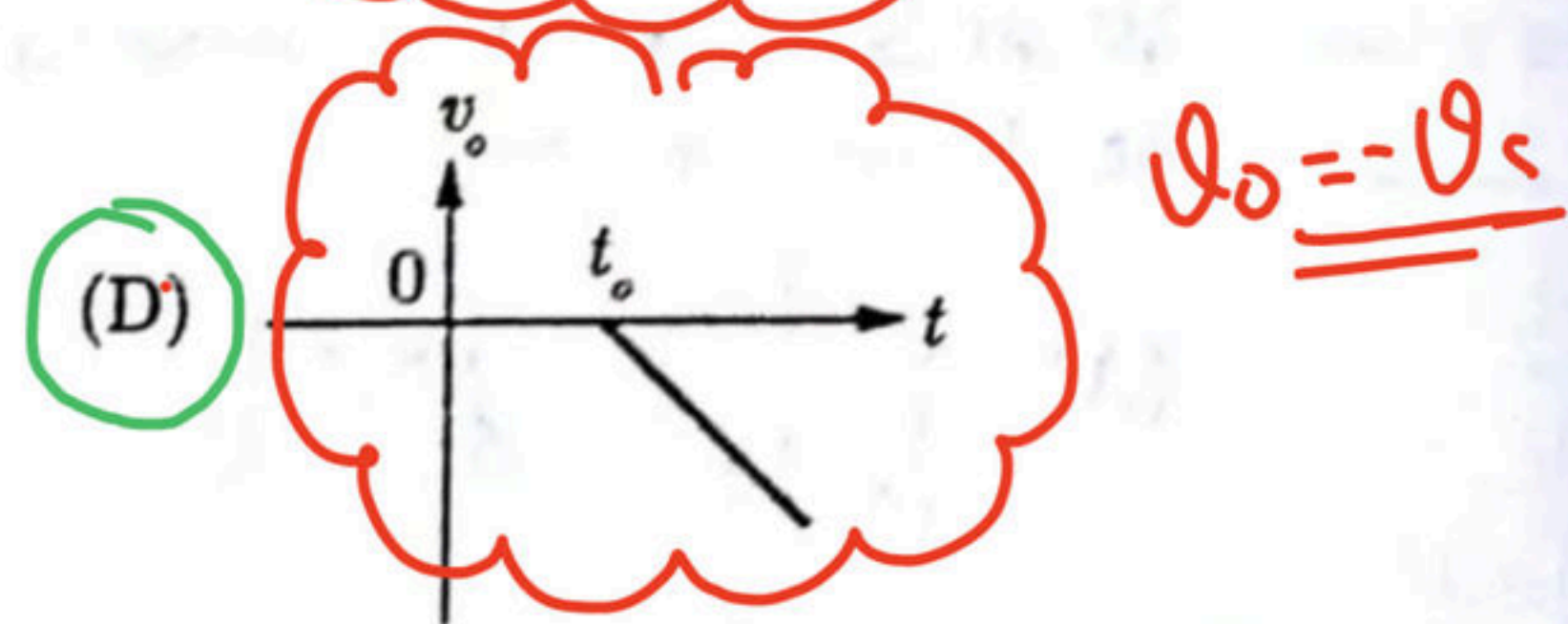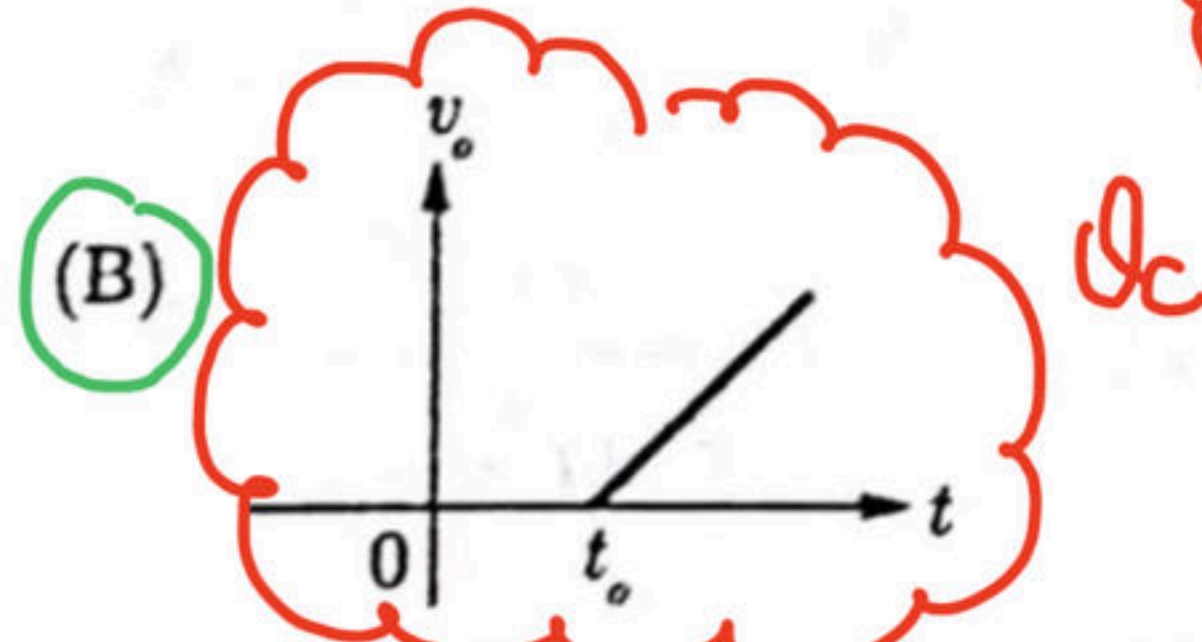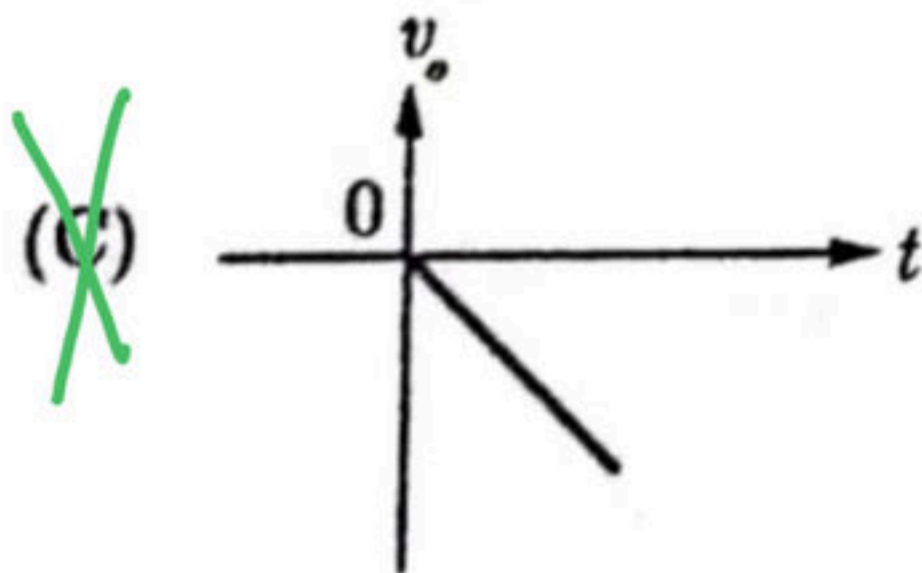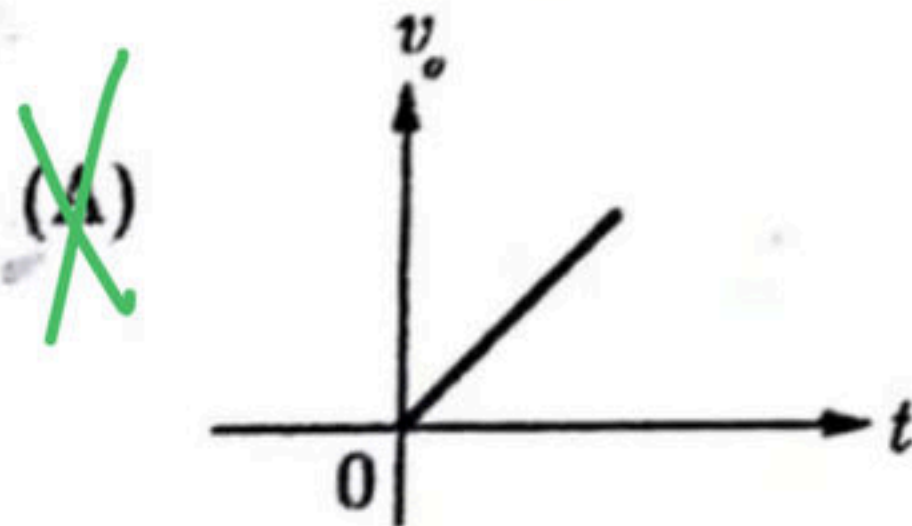

$$i = \frac{1.5}{200} \text{ mA}$$

$$V_c = \frac{1}{C} \int i dt$$

$$V_o = -V_c = -\frac{1}{C} \int i dt$$

$$V_o = -V_c$$

MCQ 8.1.41

(C) 10 μ A

Consider the circuit shown below. Assume op-amp is ideal and input v_1 , $v_2 > 0$


diode ch. is $i_d = I_s e^{V_D/V_T}$

$$V_{D1} = -V_{D1}$$

$$i = I_s e^{V_D/V_T}$$

$$V_D = V_T \ln\left(\frac{i}{I_s}\right)$$
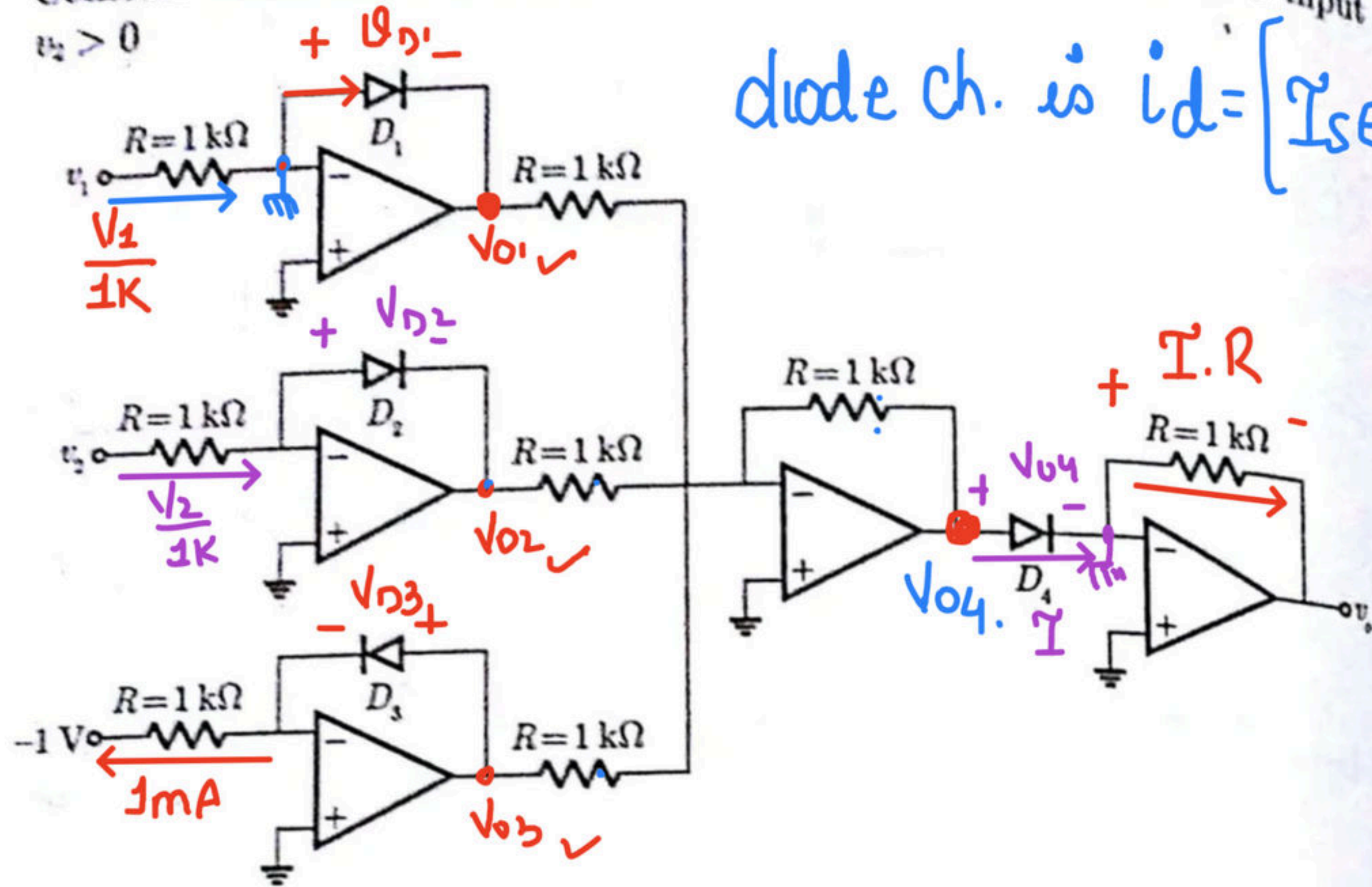
$$V_{D1} = V_T \ln\left(\frac{V_1}{I_s 1K}\right)$$



What is the value of output voltage

(A) $v_1 v_2$

(C) $-(v_1 + v_2)$

(B) $-v_1 v_2$

(D) $v_1 + v_2$

$$V_{O1} = -V_{D1} = -V_T \ln \left[\frac{V_1}{I_S \cdot 1k} \right]$$

$$V_{O2} = -V_{D2} = -V_T \ln \left[\frac{V_2}{I_S \cdot 1k} \right]$$

$$V_{D3} = V_T \ln \left[\frac{1mA}{I_S} \right]$$

$$V_{O3} = V_{D3} = V_T \ln \left(\frac{1mA}{I_S} \right)$$

$$V_{O4} = -V_{O1} - V_{O2} - V_{O3} = V_T \ln \left[\frac{V_1}{I_S \cdot 1k} \right] + V_T \ln \left[\frac{V_2}{I_S \cdot 1k} \right] - V_T \ln \left[\frac{1mA}{I_S} \right]$$

$$V_{O4} = V_T \left[\ln \left[\frac{V_1 V_2}{I_s^2 (1k)^2} \cdot \frac{\cancel{I_s}}{1mA} \right] \right]$$

$$V_{O4} = V_T \ln \left[\frac{V_1 V_2}{I_s \cdot 1k} \right]$$

Now $I = I_s e^{V_{O4}/V_T} = I_s e^{\ln \left[\frac{V_1 V_2}{I_s \cdot 1k} \right]}$

$$\Rightarrow e^{\ln x} = x \Rightarrow I = \cancel{I_s} \cdot \frac{V_1 V_2}{\cancel{I_s} \cdot 1k} = \frac{V_1 V_2}{1k}$$


$$V_0 = -I \cdot 1K$$

$$= -\frac{V_1 V_2}{1K} \cdot \cancel{1K}$$

$$V_0 = -\underline{\underline{V_1 V_2}}$$


MCQ B.1.43

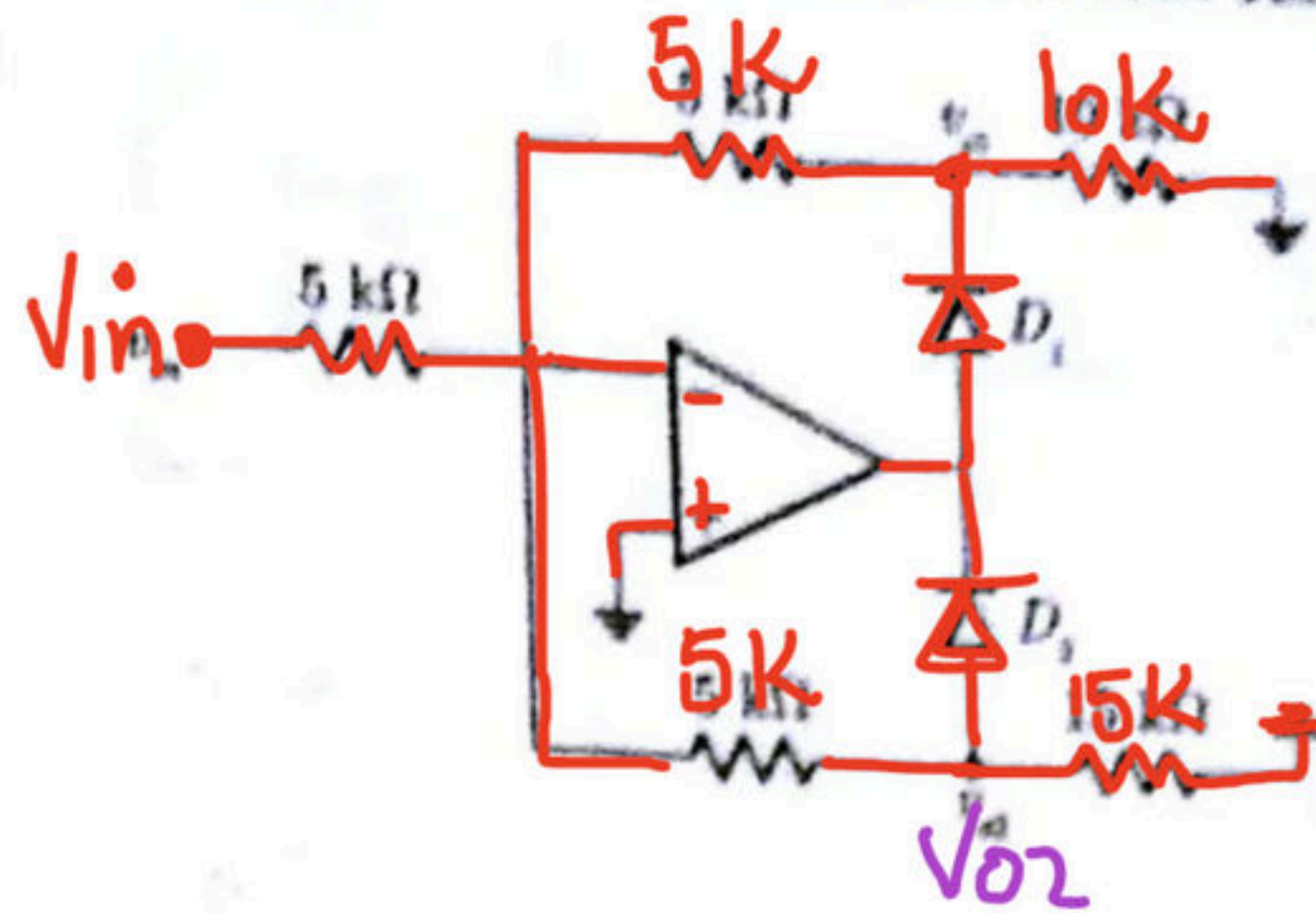Consider the circuit shown in below. Assume diodes and op-amps are ideal.




The transfer characteristic v_{o2} versus v_i will be


(A)

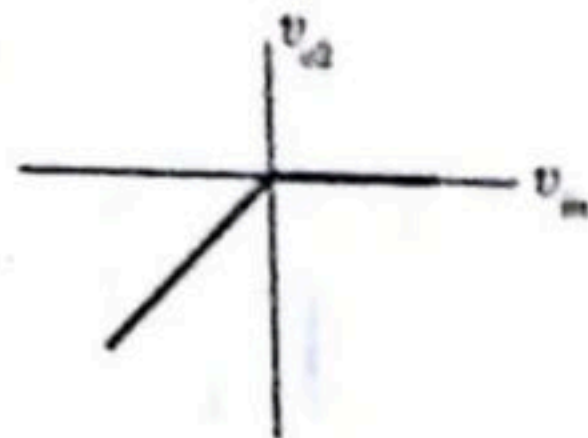


(B)

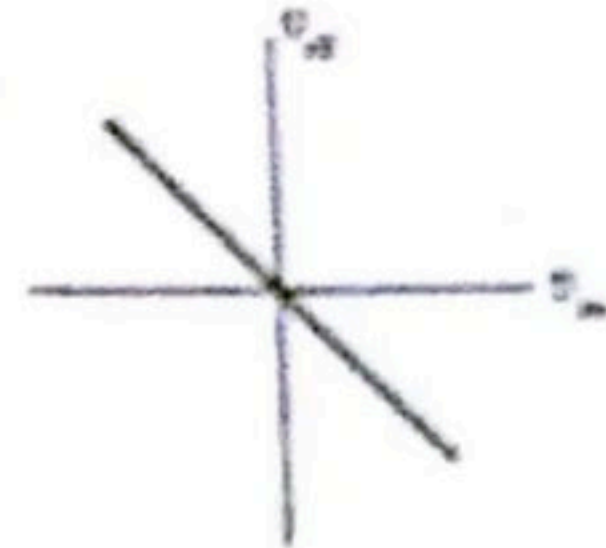


~~(C)~~

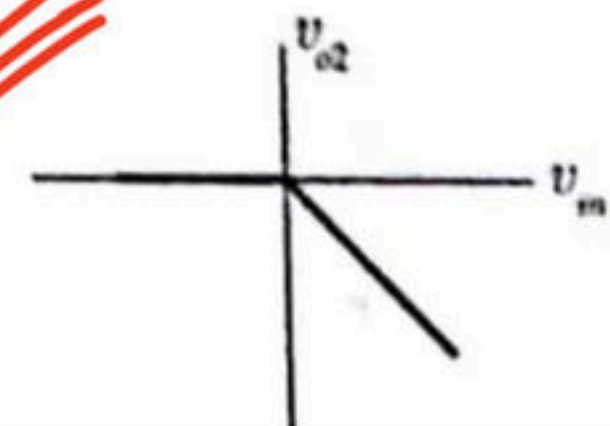

(D)

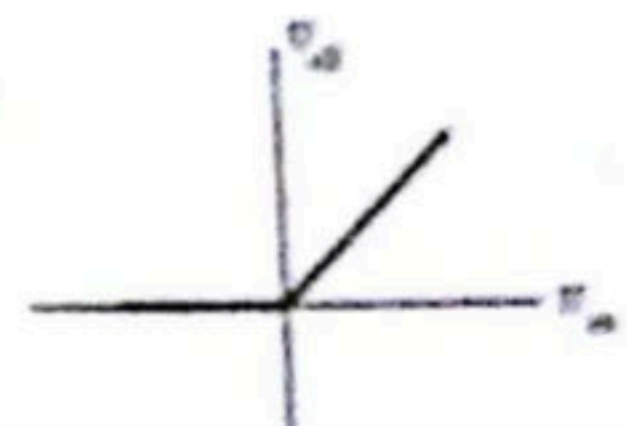


Initially diode off :-

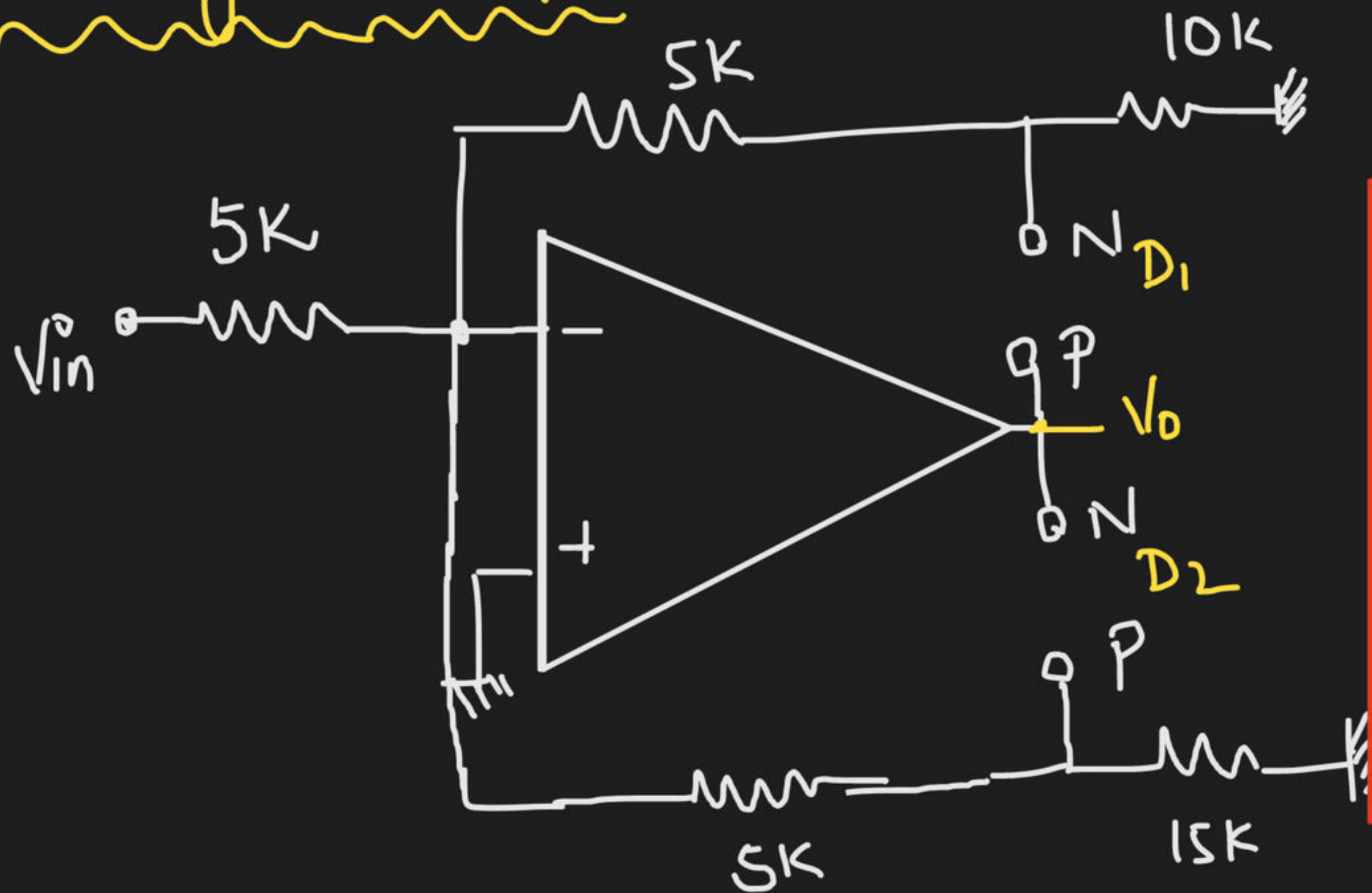


$V_{in} +ve, V_o = -V_{bias}$
 $D_2 ON$
 $D_1 OFF$
 $V_{in} -ve, D_2 OFF$
 $D_1 ON.$

for $V_{in} +ve$ $V_o = -V_{in}$

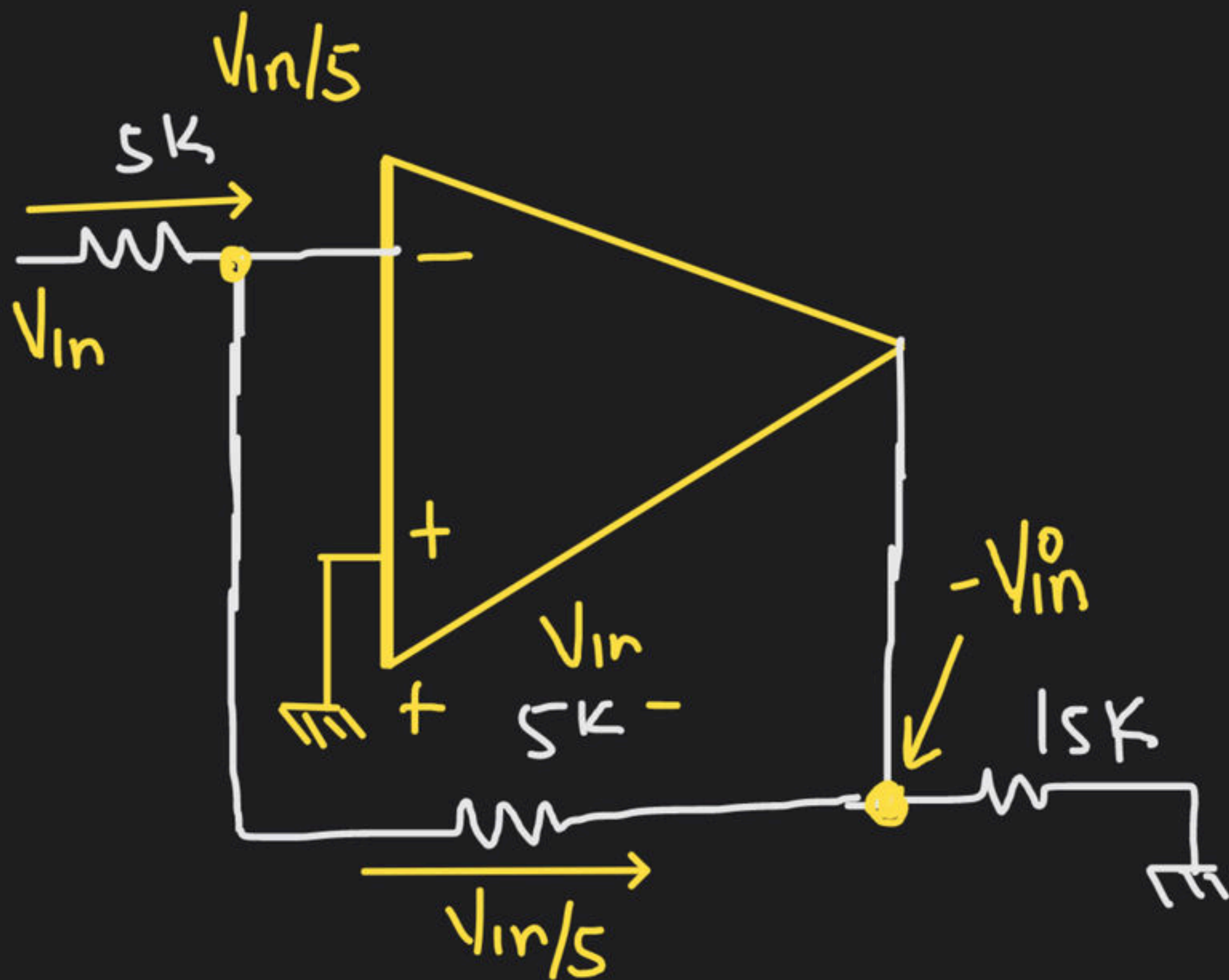

for $V_{in} -ve$


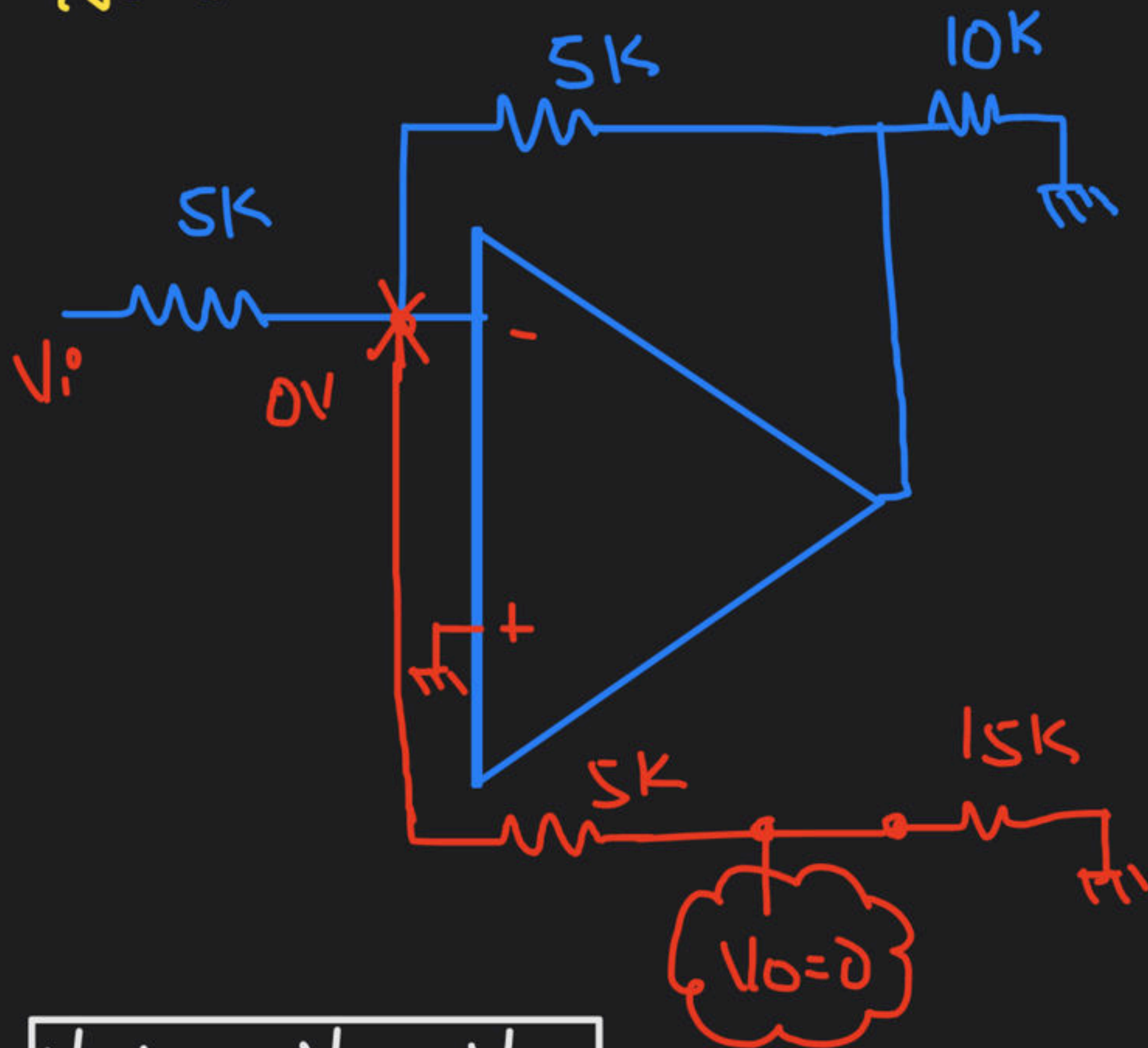


$V_{in} > 0$	$V_o = -V_{in}$
$V_{in} < 0$	$V_o = 0$


MCQ 8.1.29

In the given figure, if the input is a sinusoidal signal, the output will appear as

• Cut in 2V.

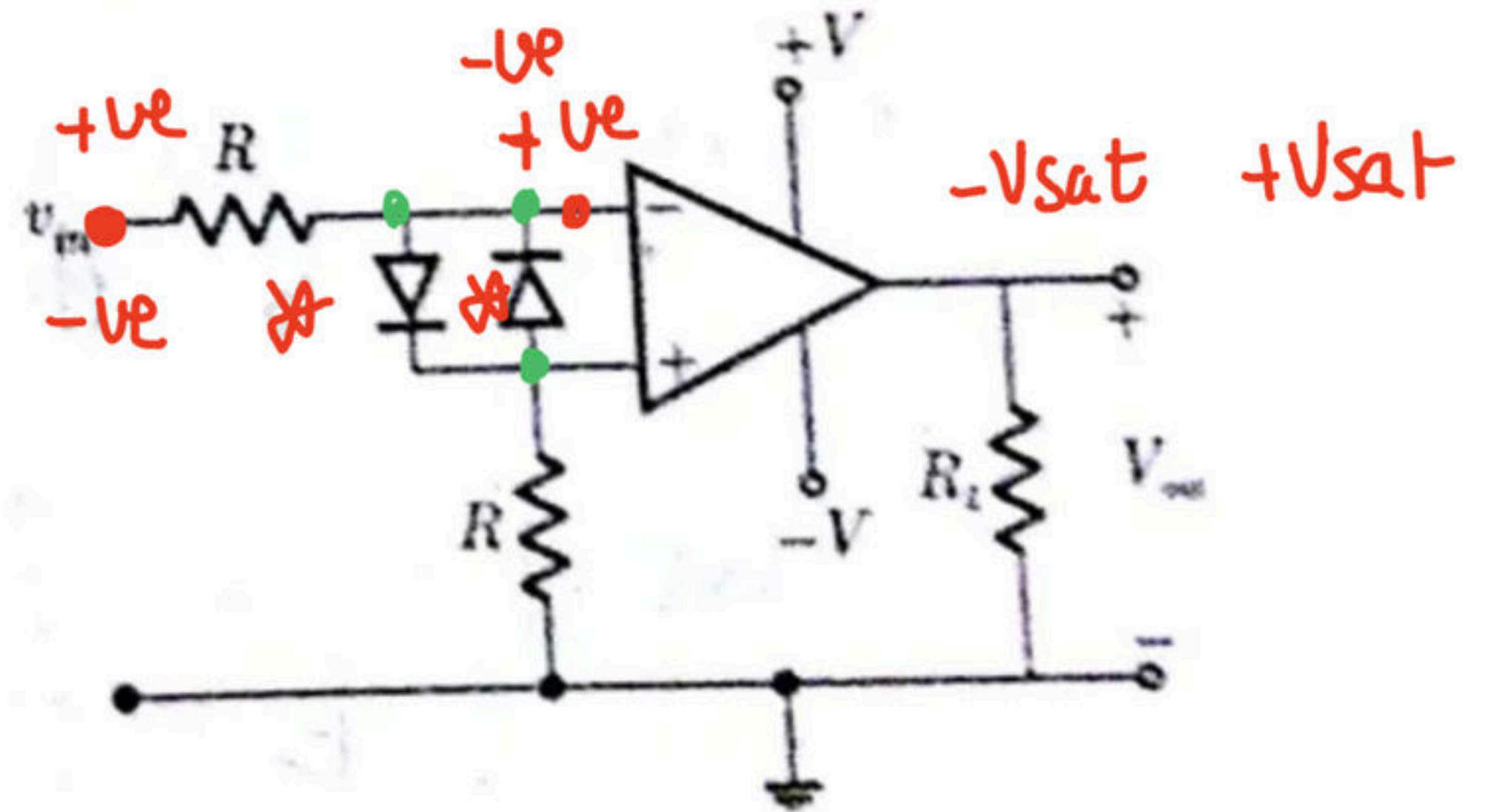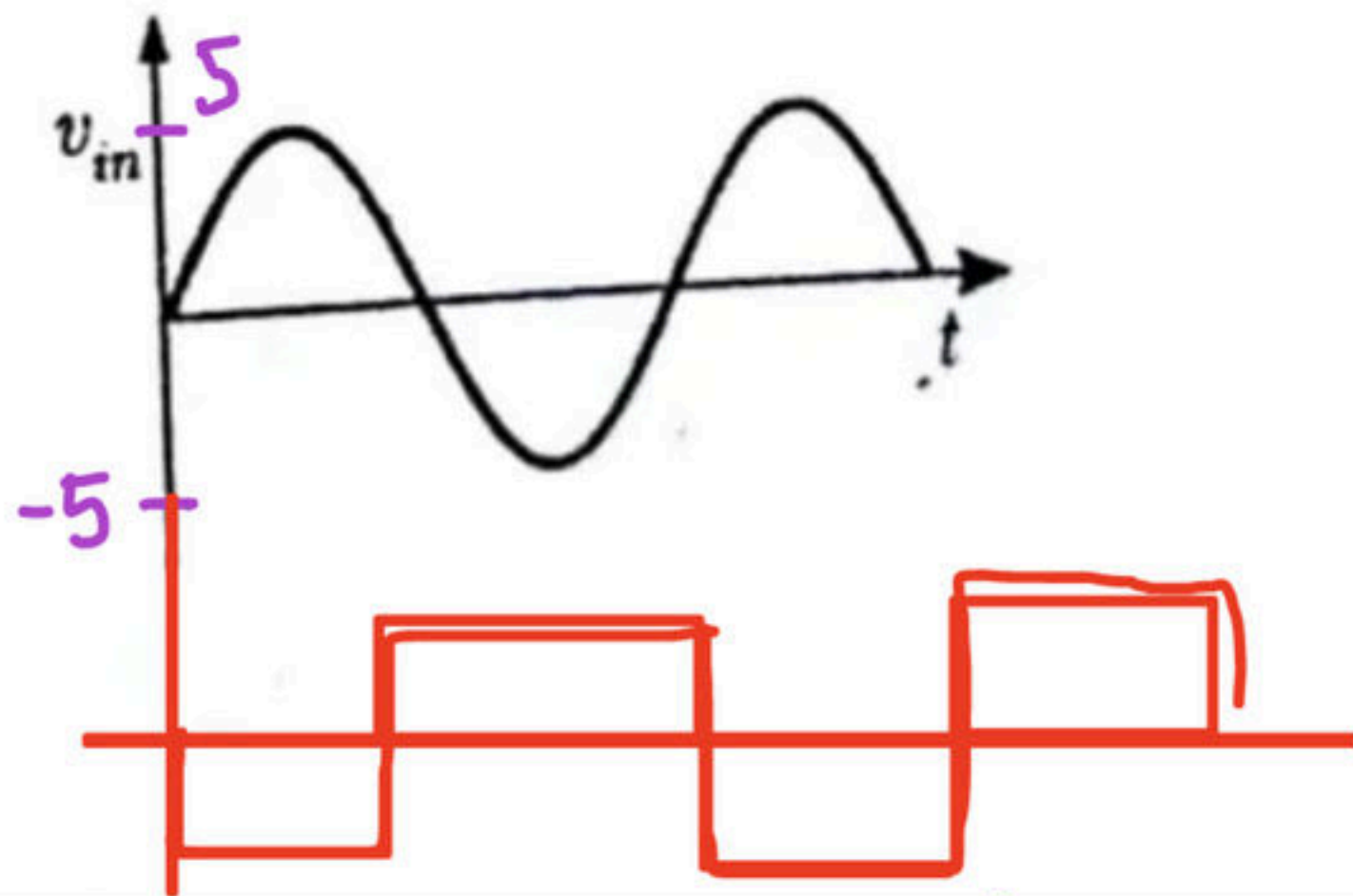

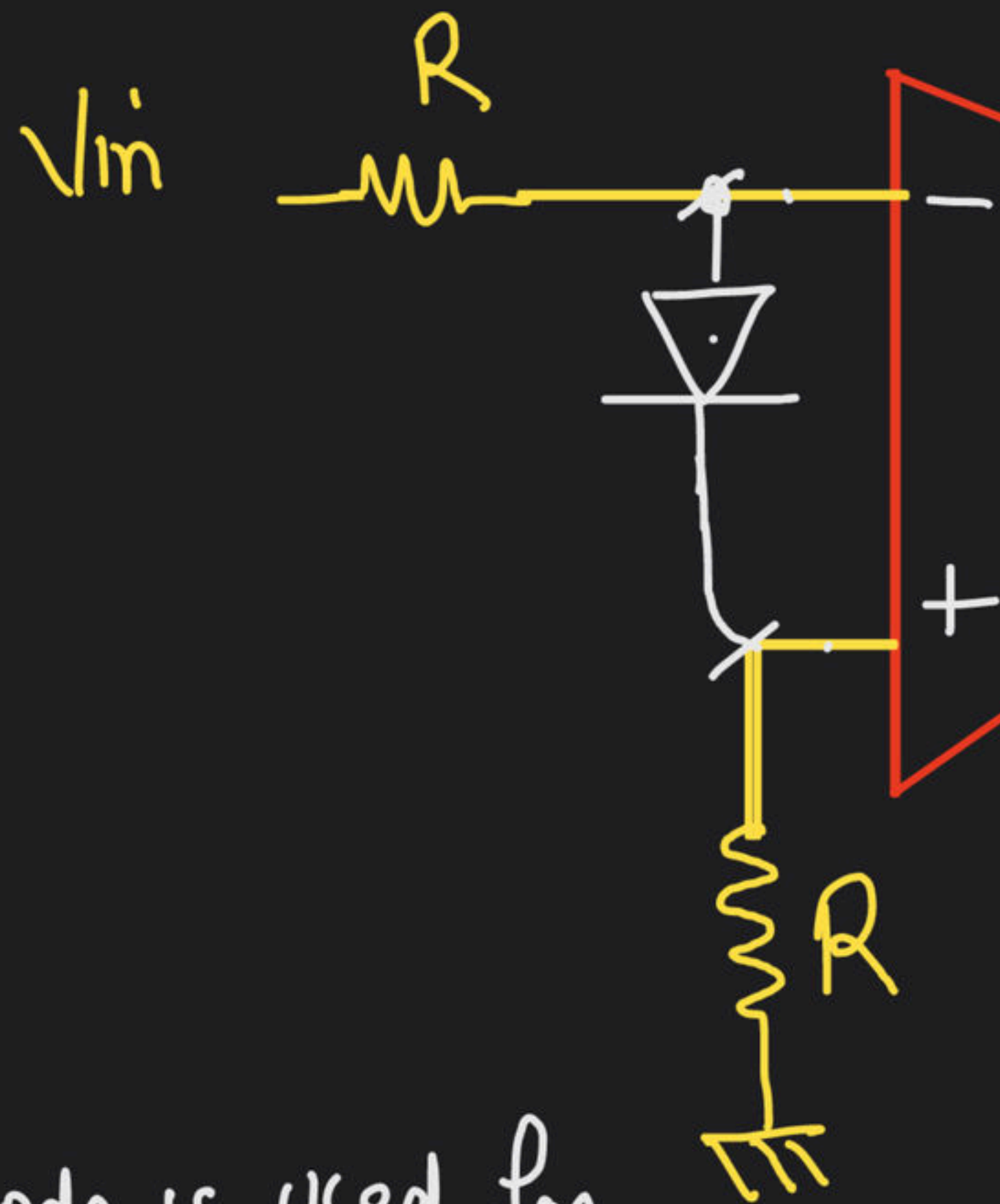- $V_0 \Rightarrow$
- a) Sine wave
 - b) triangular wave
 - ☒ c) Square wave with zero avg
 - d) Square wave with non zero avg.



diode cut in = 0.2

$V_{out} = 0$ $0 < V_{in} < 0.2$ diode OFF

$$V_{out} = -V_{sat}$$

• $V_{in} > 0.2$ then diode on

$$V_{out} = -\underline{\underline{V_{sat}}}$$

diode is used for

Protection :- input blw terminals shd not be large value

$$V_{in} > 0$$



$$A_d(V_+ - V_-) = 0.$$

$$V_{in} < 0$$

