



Analog Electronics - XXXIV

Lakshya GATE 2023: Course on Analog Electronics for ECE EE IN

**BE WITH PEOPLE
WHO INSPIRE YOU.**

**AND MAKE SURE
YOU INSPIRE
THEM TO BECOME
STRONGER AND
BETTER.**




Friends


Topic :- Ac and Dc load line

⇒ The bias point of Mosfet $\{I_D, V_{DS}\}$,

Example

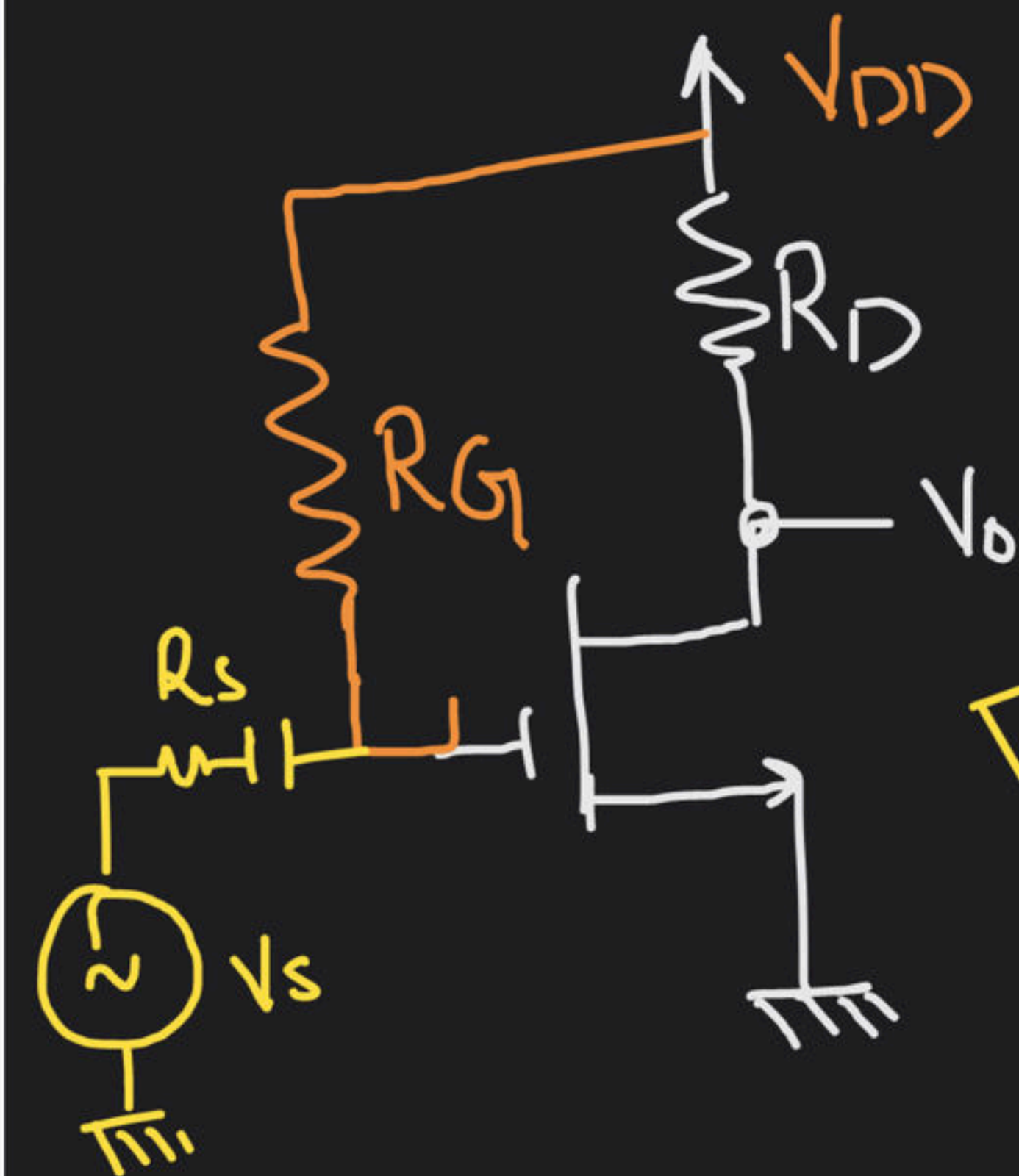


dc Analysis

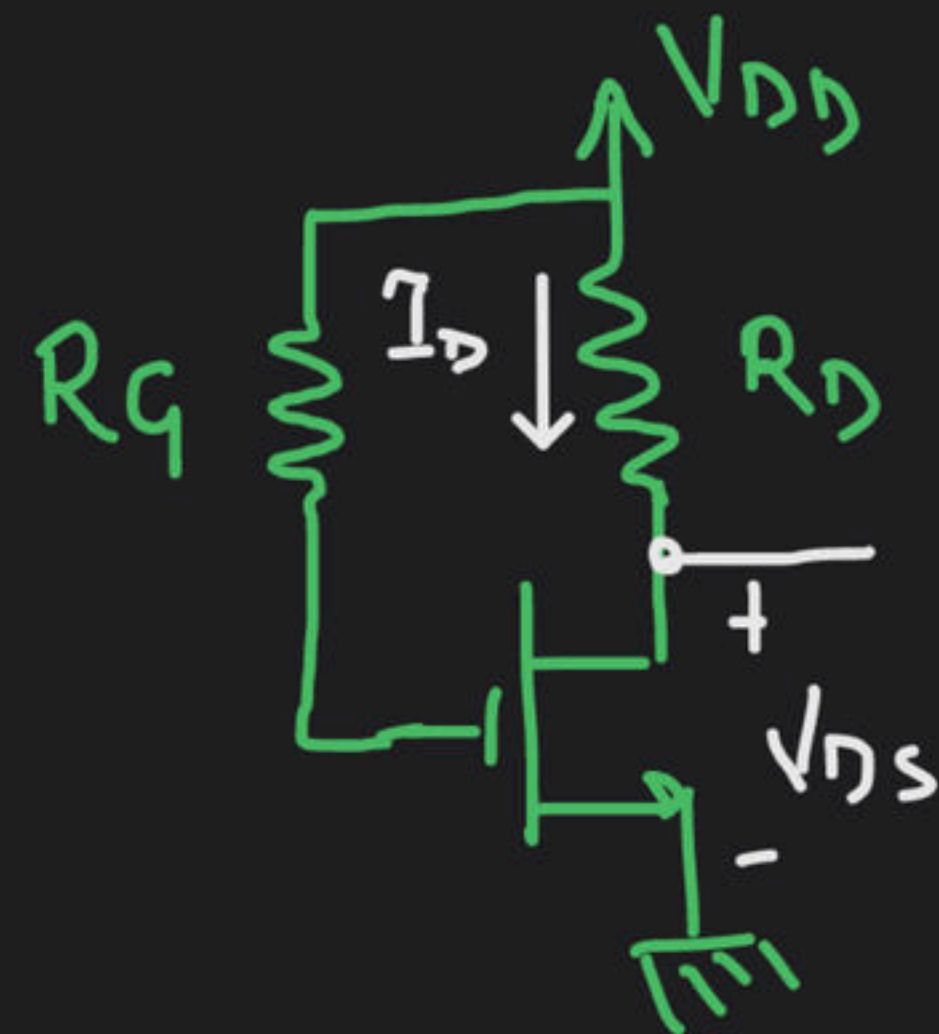

dc load line


$$V_{DD} = I_D R_D + V_{DS}$$

Ac Analysis ckt

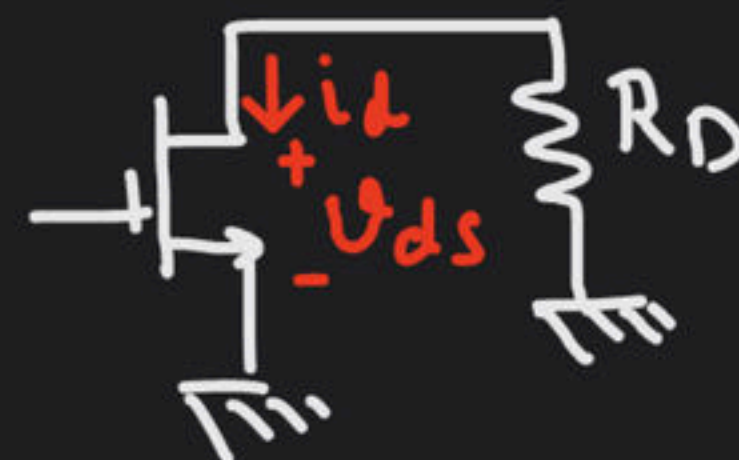

$$v_{ds} = -i_d R_D$$


ac load line

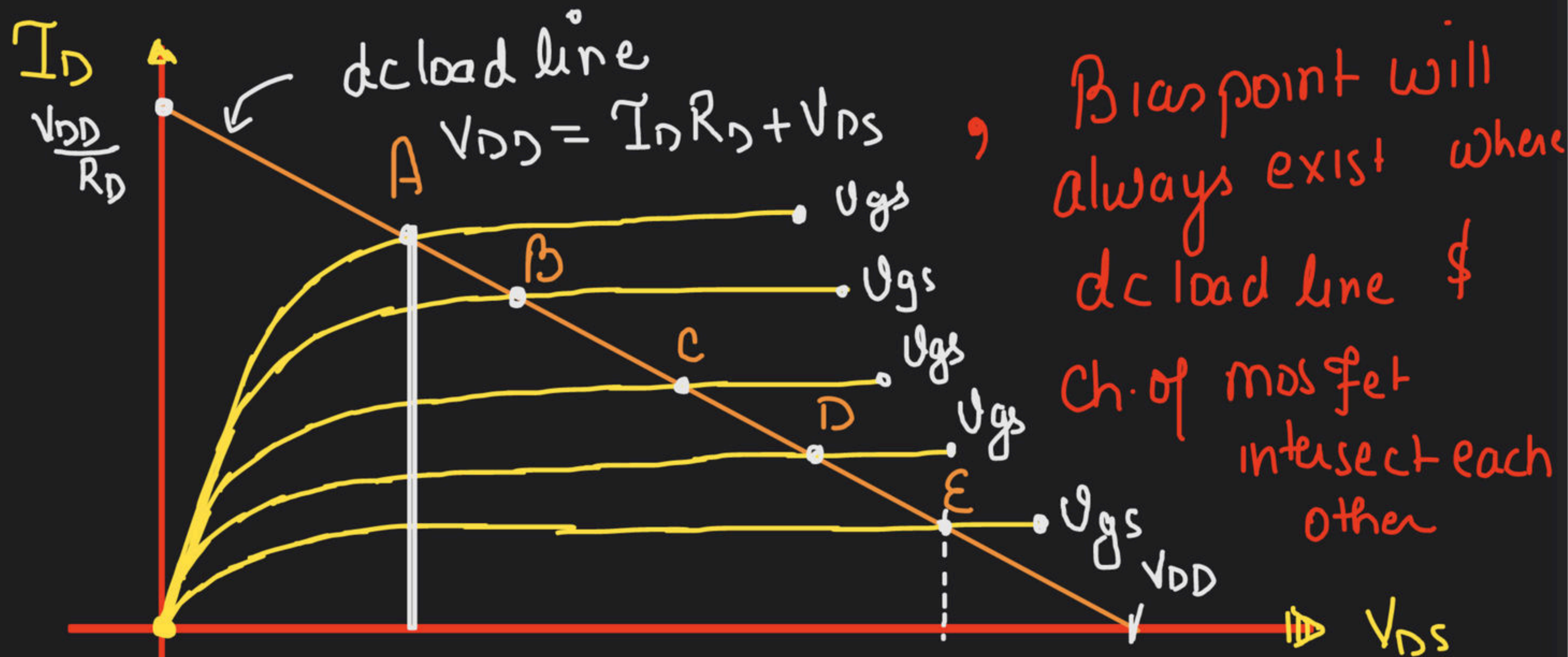


The bias point will exist only where the dc load line i.e. KVL and mosfet ch. are satisfied i.e. they both cut each other

we always bias the device @ middle of the plot.

• Now ac/dc load line meet @ Q point →

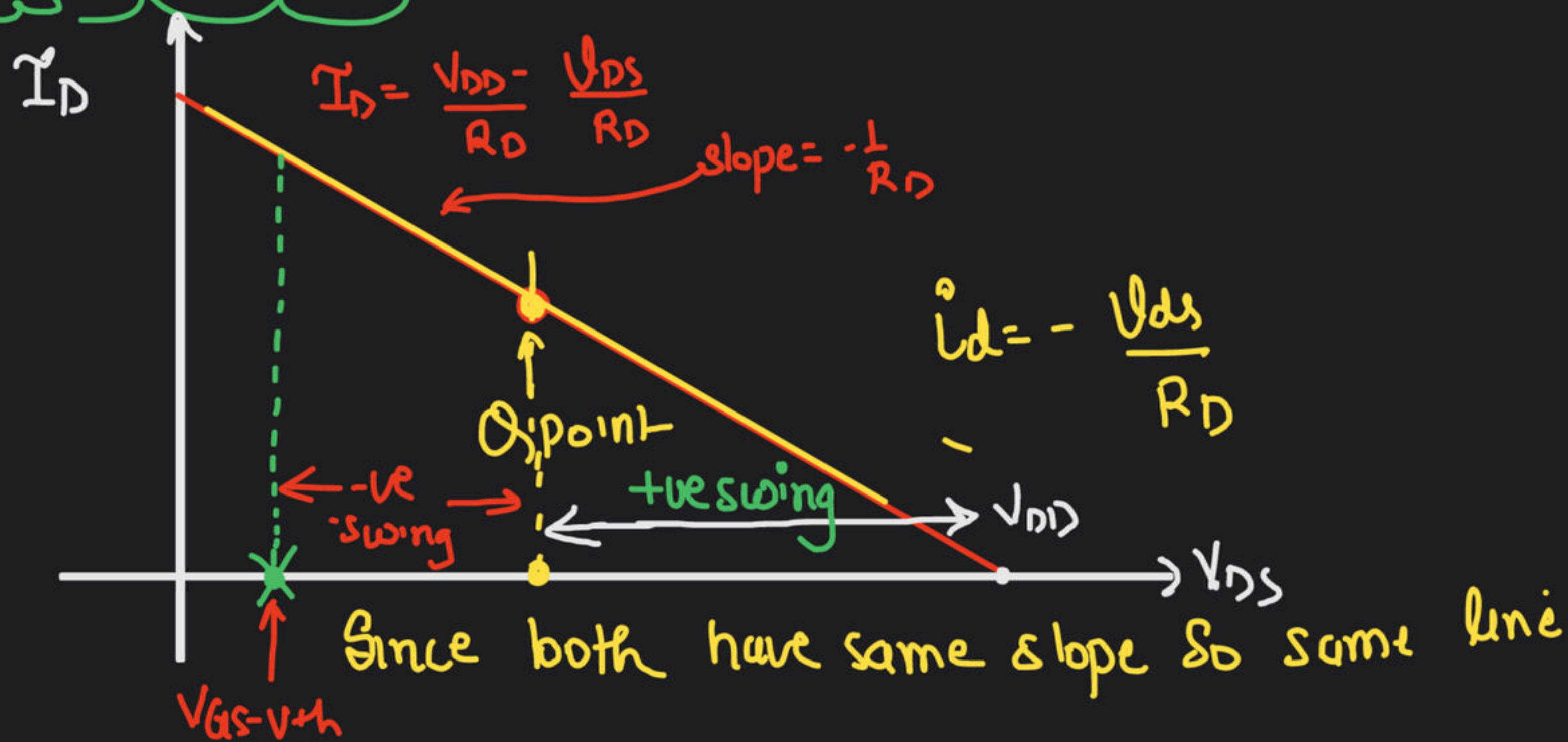


Q

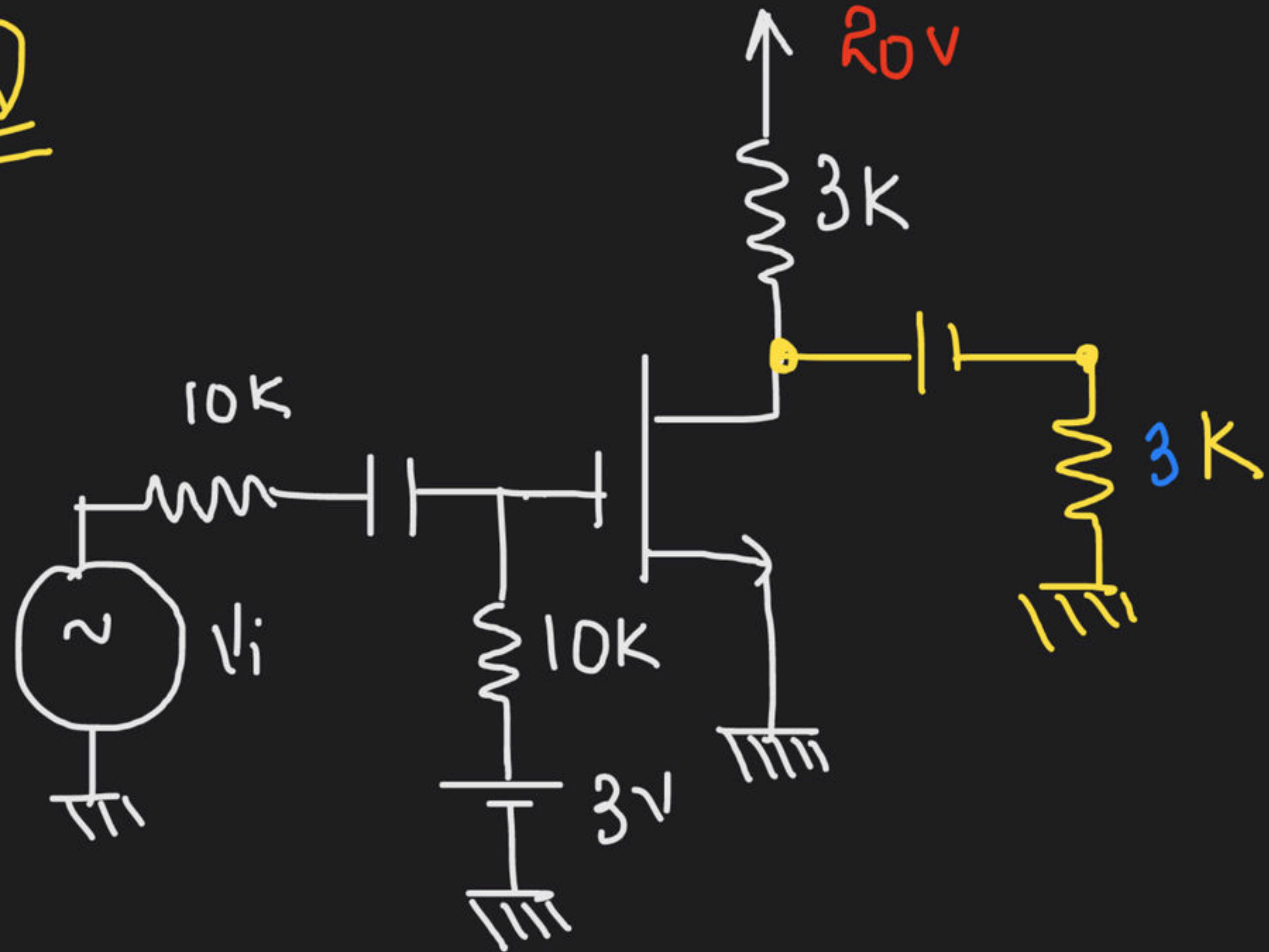


1) $V_{th} = 1V$,
 $\mu_n C_{ox} \frac{W}{L} = 1mA/V^2$
1) find $I_D = ?$

@dc

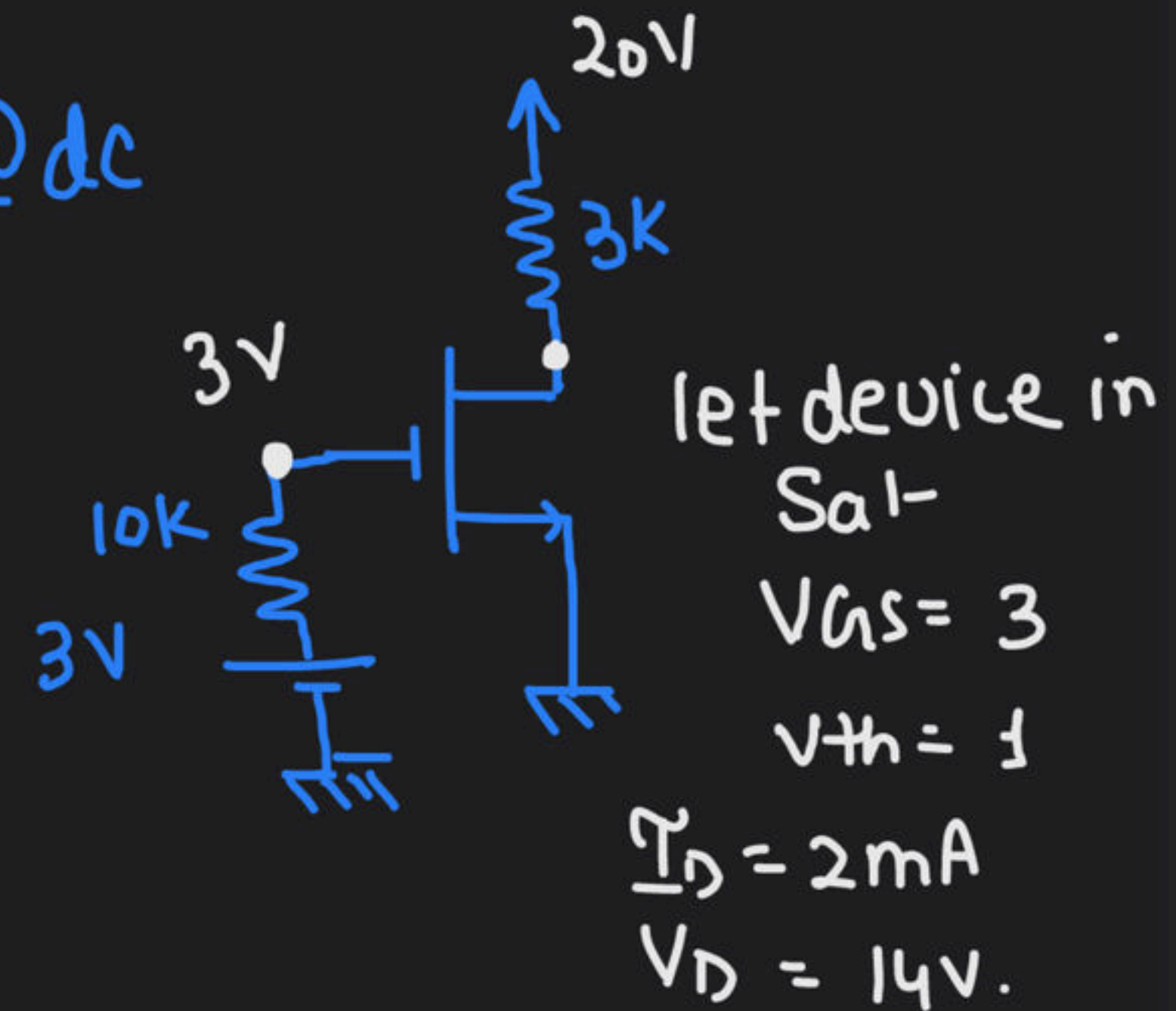


Bias point $\Rightarrow I_D, V_{DS}$
(2mA, 14V)


@ ac analysis

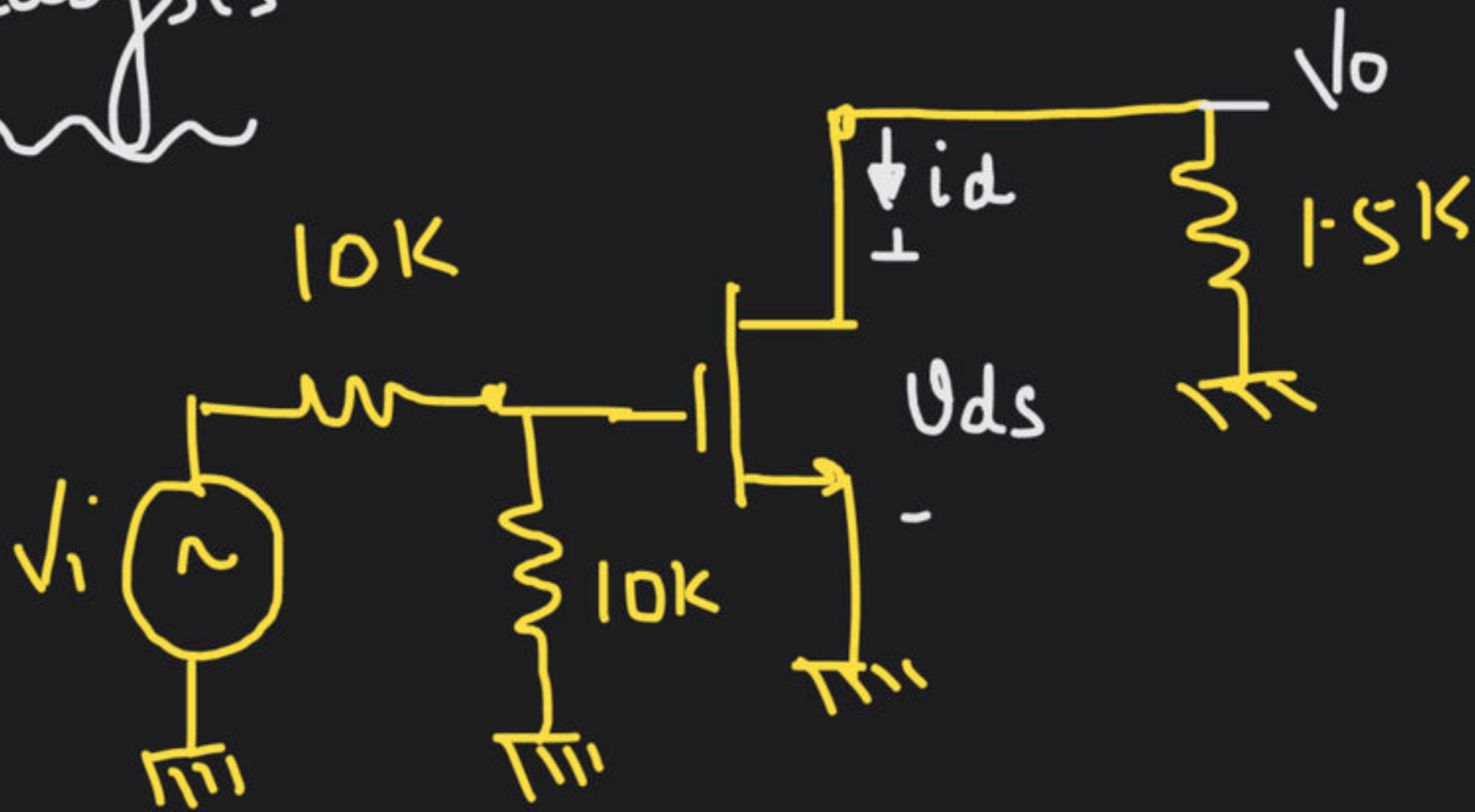

ac load line
 $v_{ds} = -1.5K i_d$

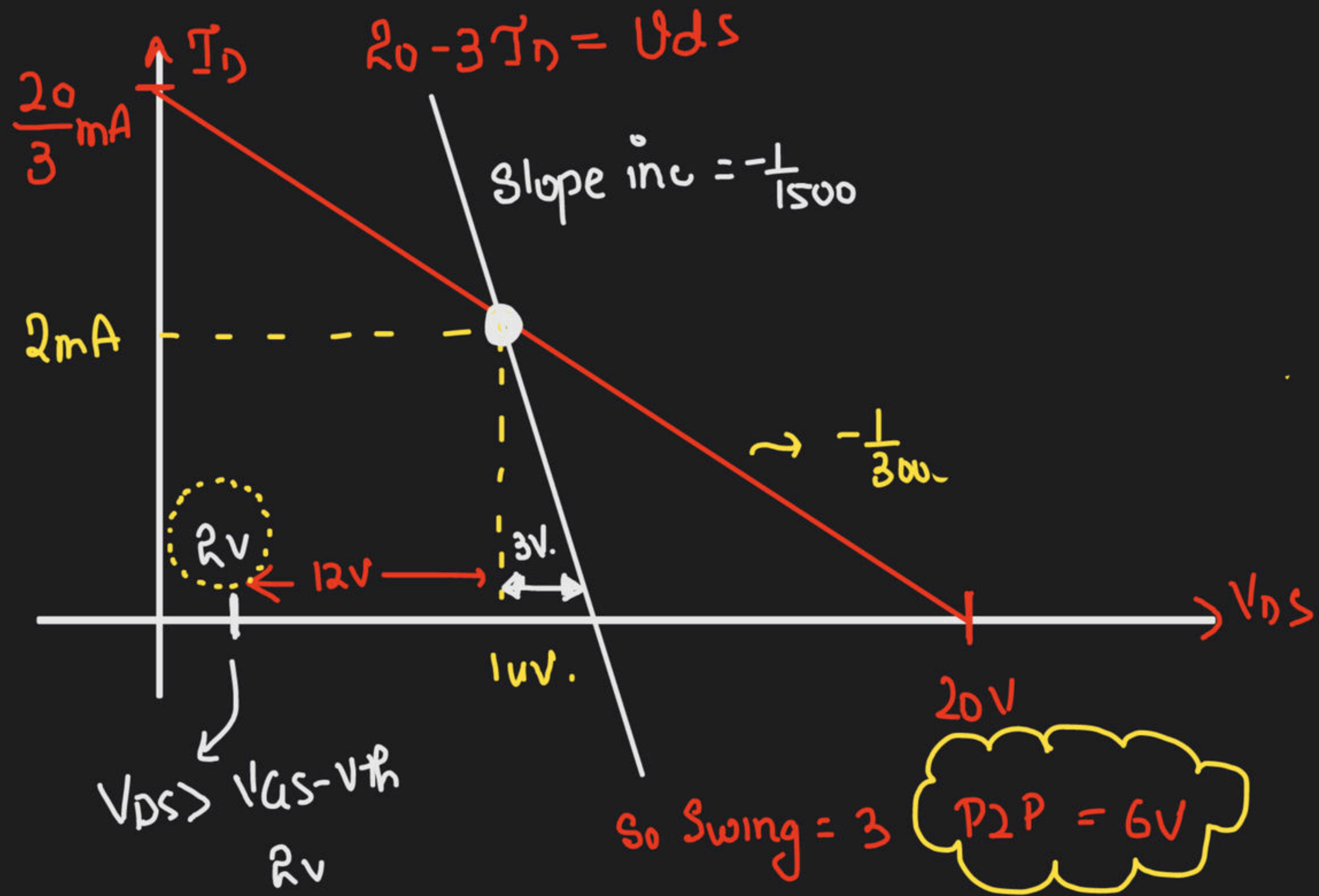


11

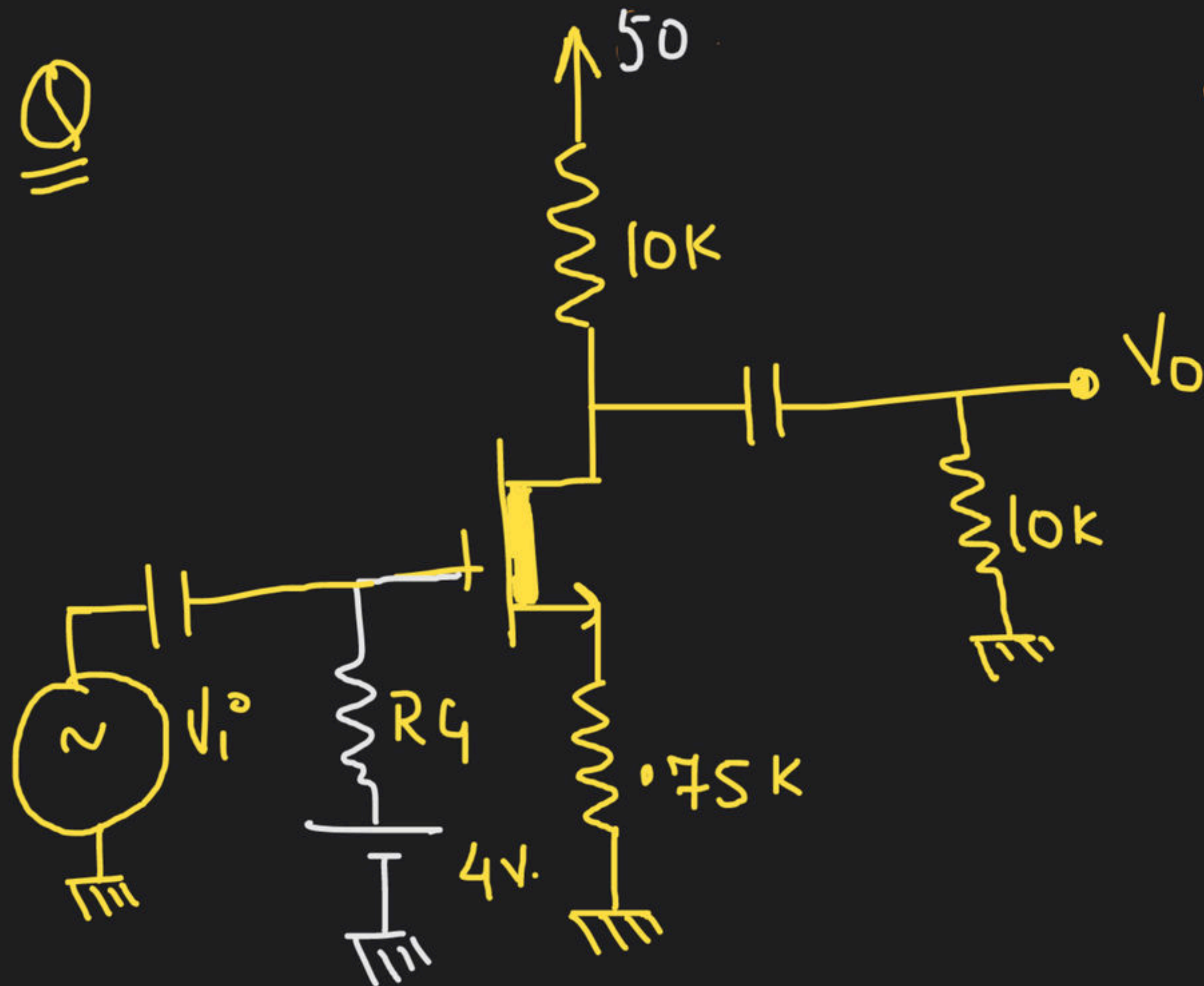

$$\mu_n C_{ox} \frac{W}{L} = 0.5 \text{ mA/V}^2$$

$$V_{th} = -1 \text{ V}$$

Solve @ dc

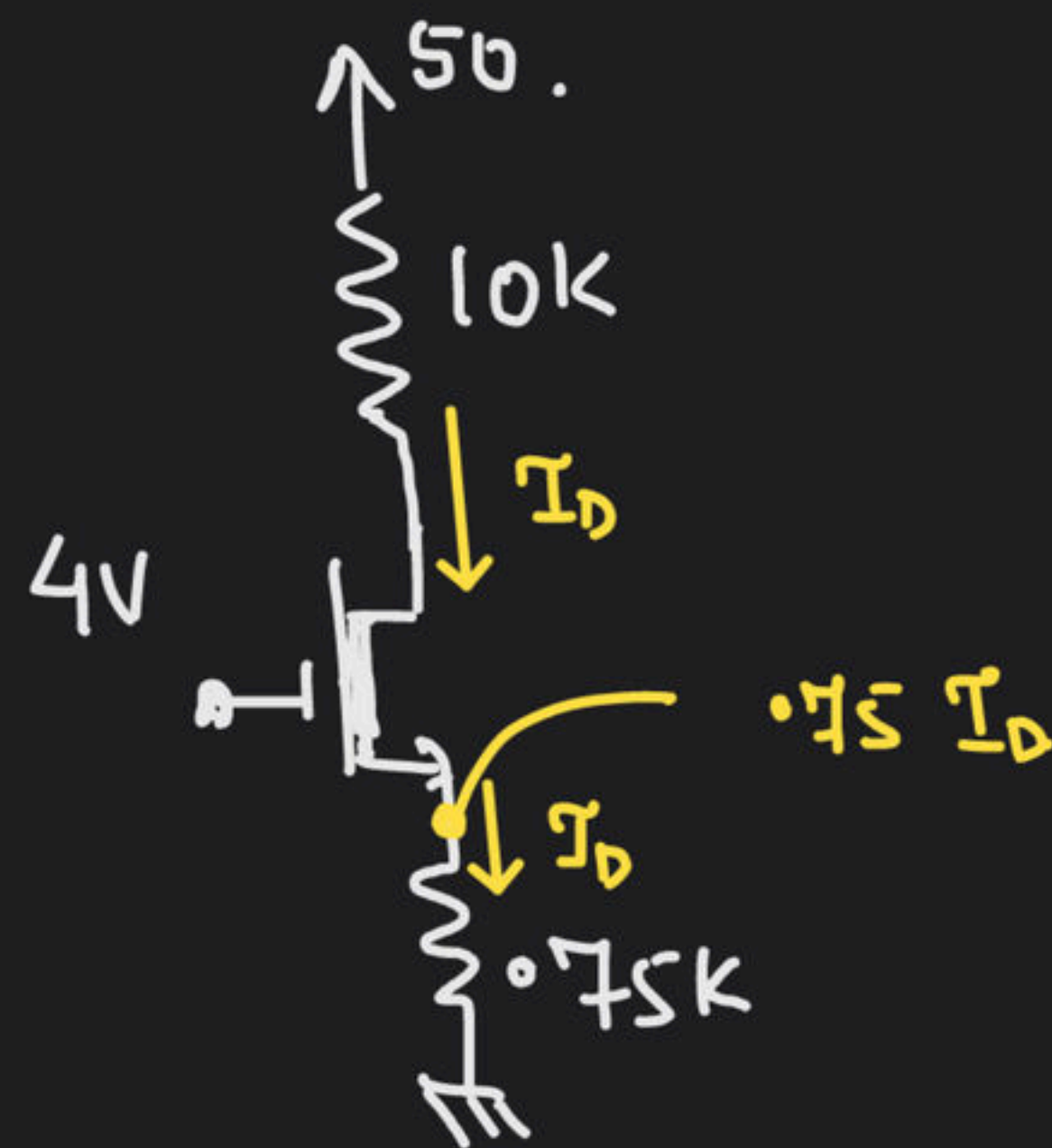

@Sat

$$I_D = \frac{1}{2} \times 0.5 \left(4 - 0.75 I_D - (-1) \right)^2$$

$$4 I_D = (5 - 0.75 I_D)^2$$

$$4 I_D = 25 + 0.5625 I_D^2 - 7.5 I_D$$


$$I_D = 2.47 \text{ mA.}$$

$$V_{DS} = 50 - (10 \times 0.75 \times 2.47)$$

$$\underline{\underline{V_{DS}}} = 23.447$$

$$V_{GS} = 4 - 0.75 I_D = 2.14$$

Now CKT @ ac

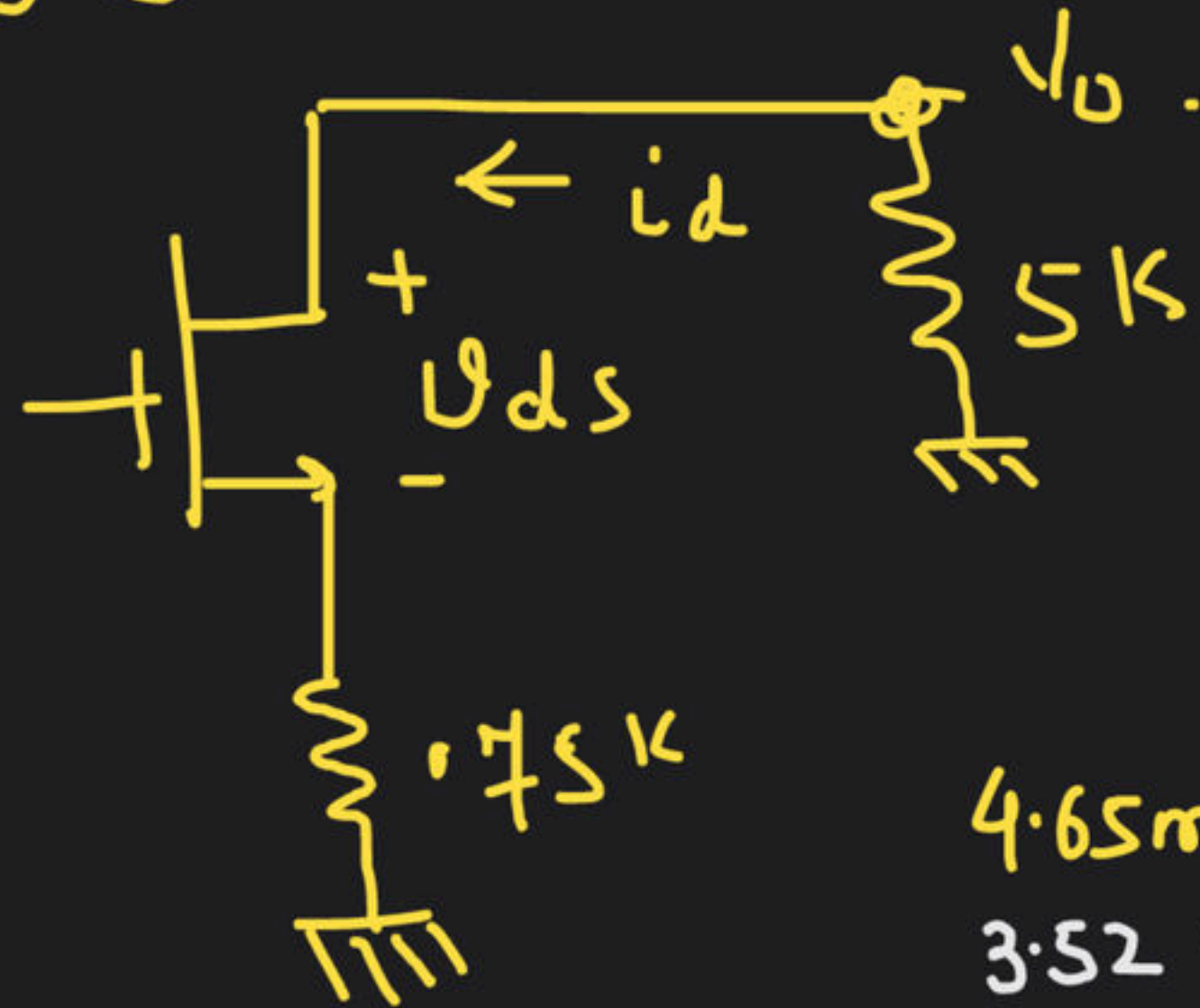


$$V_{ds} = -5.75k \cdot i_d$$

$$(V_{GS} - V_{th}) = 3.15$$

4.65mA
3.52

2.47mA

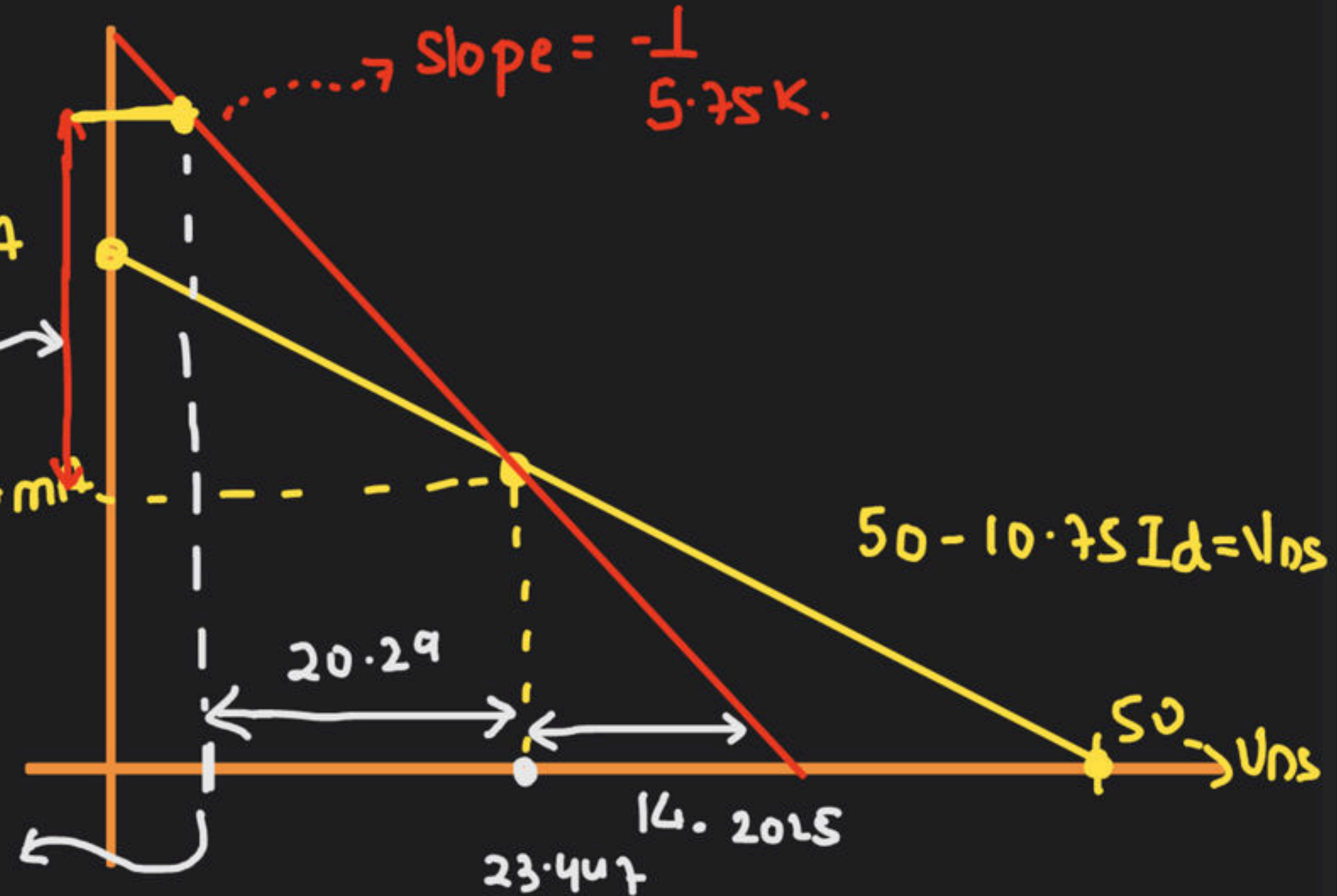


i_d swing 2.47 mA

$$V_o = -5000 i_d$$

$$\text{swing @ } V_o = \underline{\underline{+12.35}}$$

$$P2P = \underline{\underline{24.7V}}$$


Q

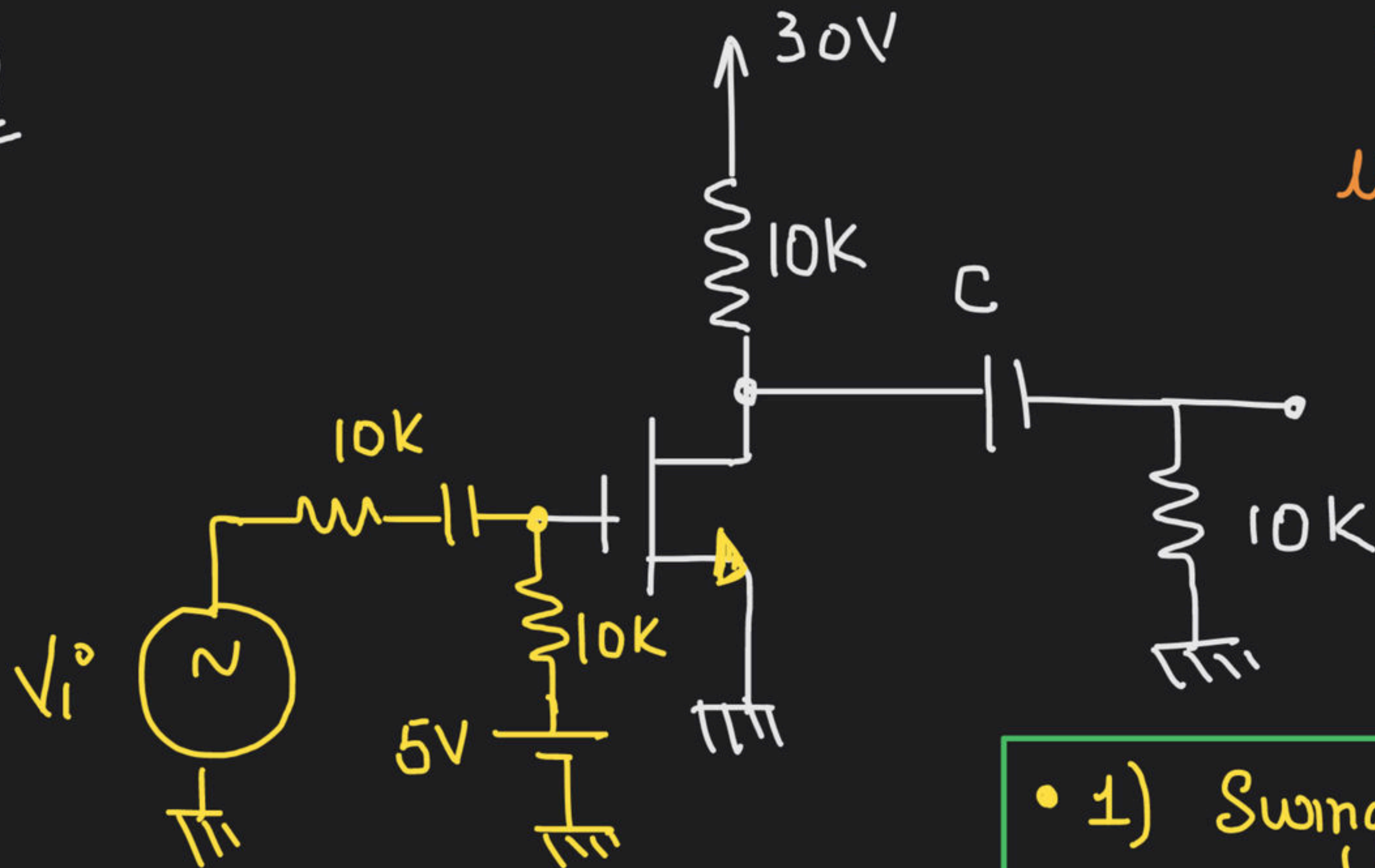

$$V_{th} = 1V$$
$$\mu n C_{ox} \frac{W}{L} = 0.2 \text{ mA/V}^2$$

- 1) Swing available @ o/p
- a) 14 ~~b) 8~~ c) 12 d) 10

@ dc

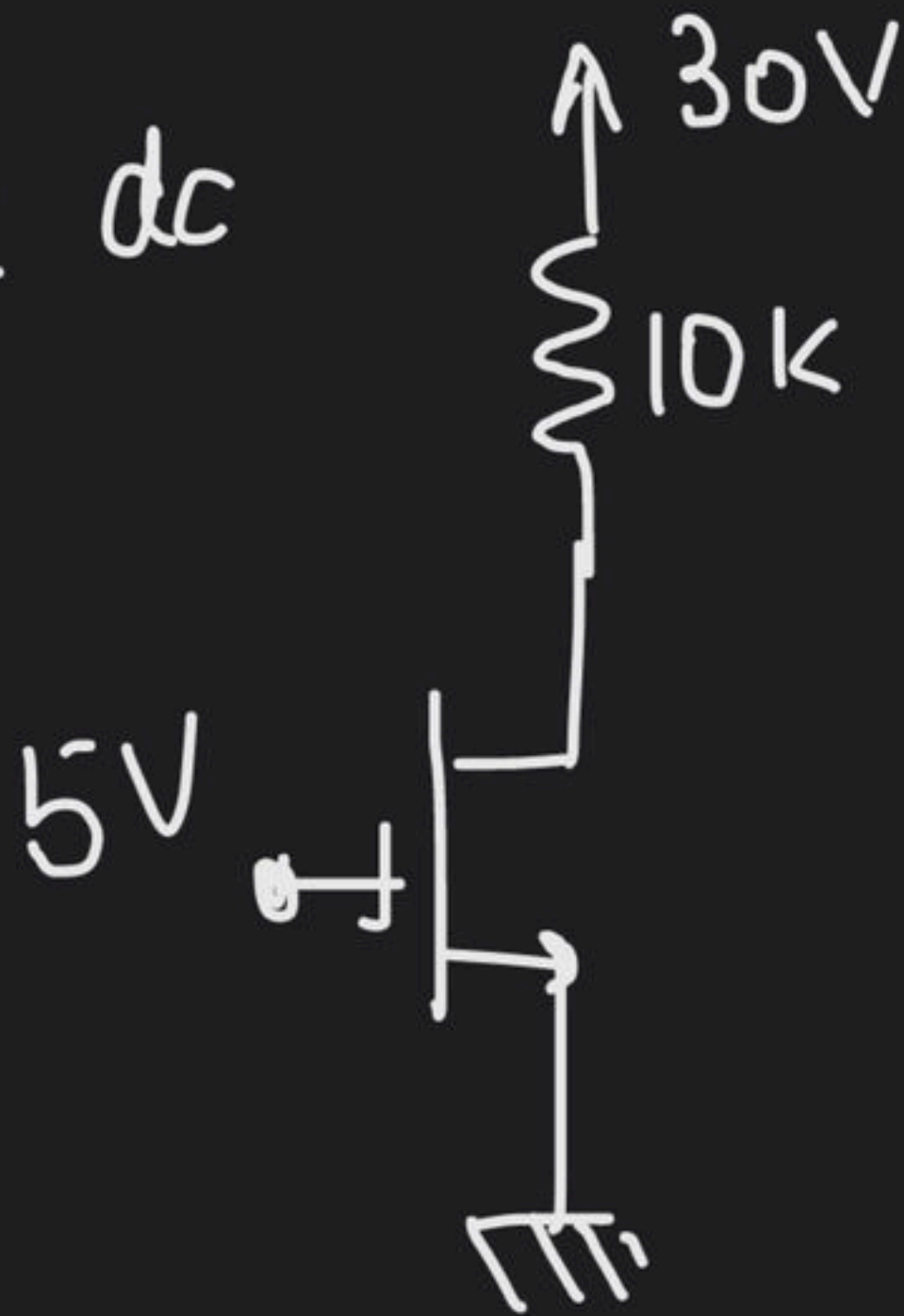

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$


$$= \frac{1}{2} \times 0.2 \times 10^{-4} (5 - 1)^2 = 1.6 \text{ mA}$$

$$V_{DS} = 14 \text{ V}$$

ac Analysis



$$V_{ds} = -5000 i_d$$

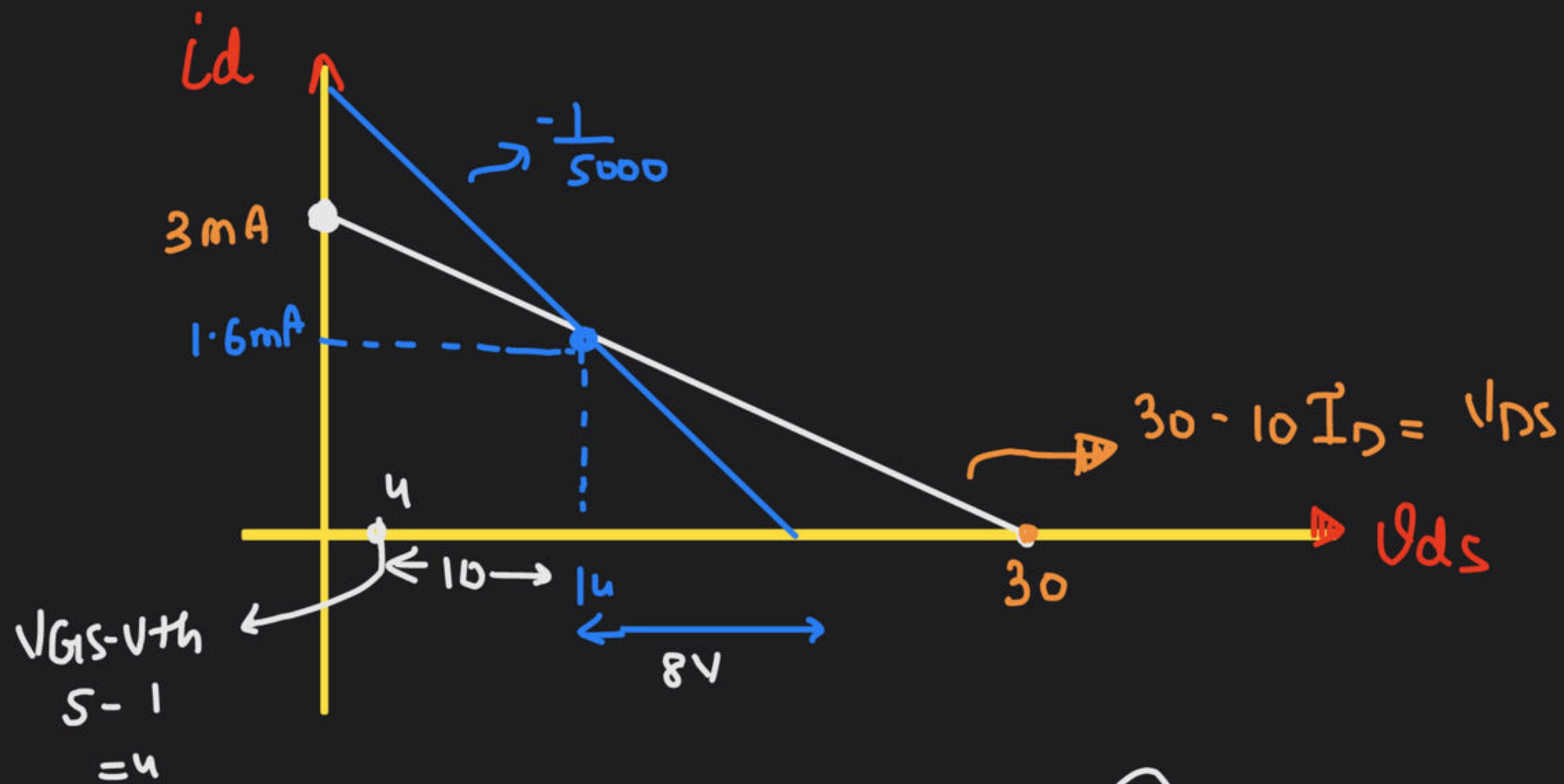

Find allowed swing of input signal \Rightarrow .


a) 8

b) 6

~~c) 4~~

d) 2

AC analysis ckt

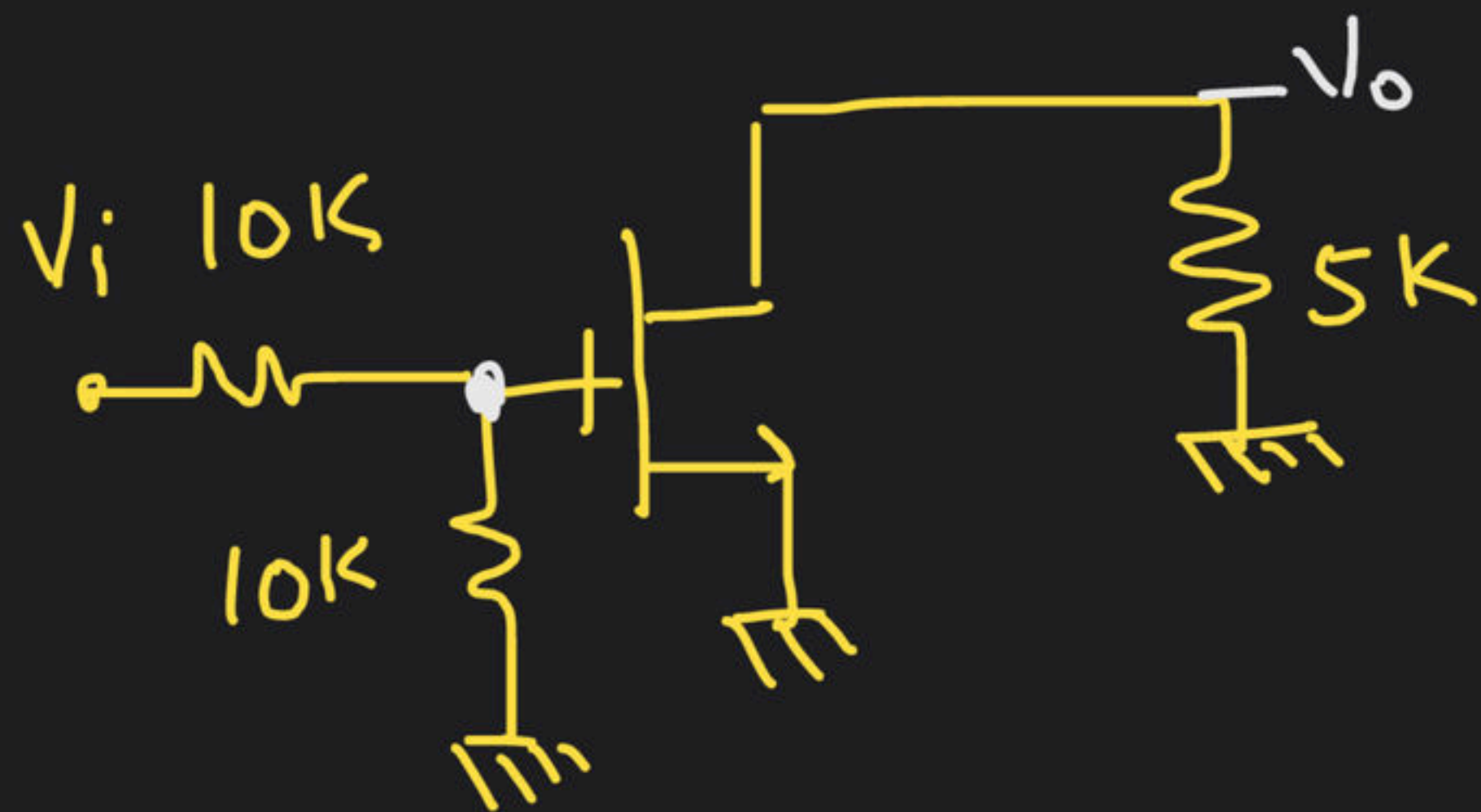

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} \times I_D}$$

$$= \sqrt{2 \times 1.6 \times 10^{-3} \times 2 \times 10^{-3}}$$

$$g_m = 8 \times 10^{-4}$$


$$V_o = -g_m \theta_{gs} 5000$$

$$= -8 \times 10^{-4} \times \frac{1}{2} \times 5000 \theta_i$$

$$V_o = -2 \theta_i$$

Topic Current mirror using MOSFET

The Basic Current mirror \Rightarrow

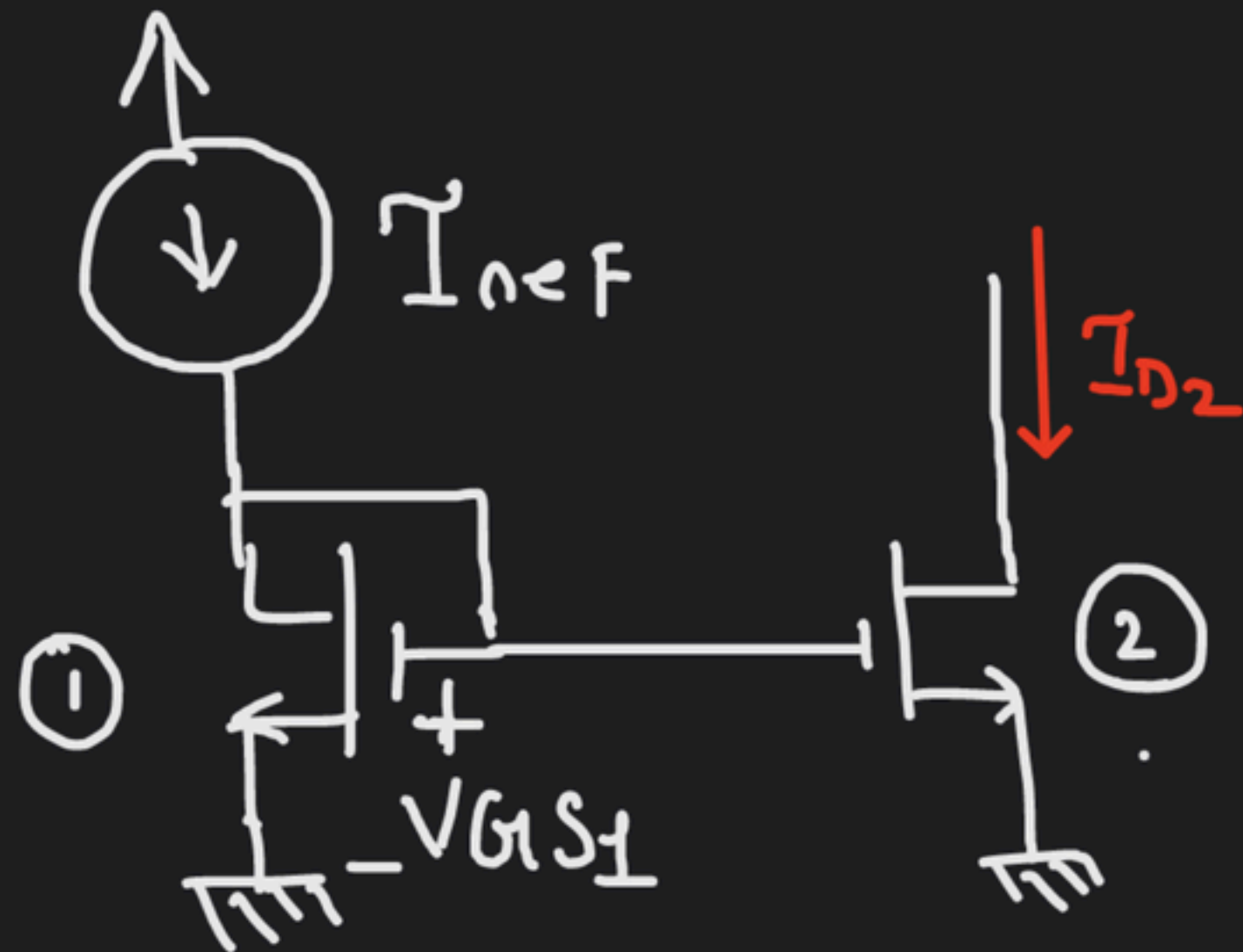

• let both are identical devices

I_{REF} flow in drain of M_1
and V_{GS1} voltage will be

developed

$$I_{D1} = I_{\text{ref}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{th})^2$$

$$\sqrt{\frac{I_{\text{ref}}}{K_n}} + V_{th} = V_{GS1}$$

Here $V_{GS1} = V_{GS2}$ thus

assume that
 M_2 is in
Sat mode


$I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS2} - V_{th})^2$ Since both
device are same so $I_{\text{ref}} = I_{D2}$



Analog Electronics - XXXIV

Lakshya GATE 2023: Course on Analog Electronics for ECE EE IN

Q Find Current I_D 5V.

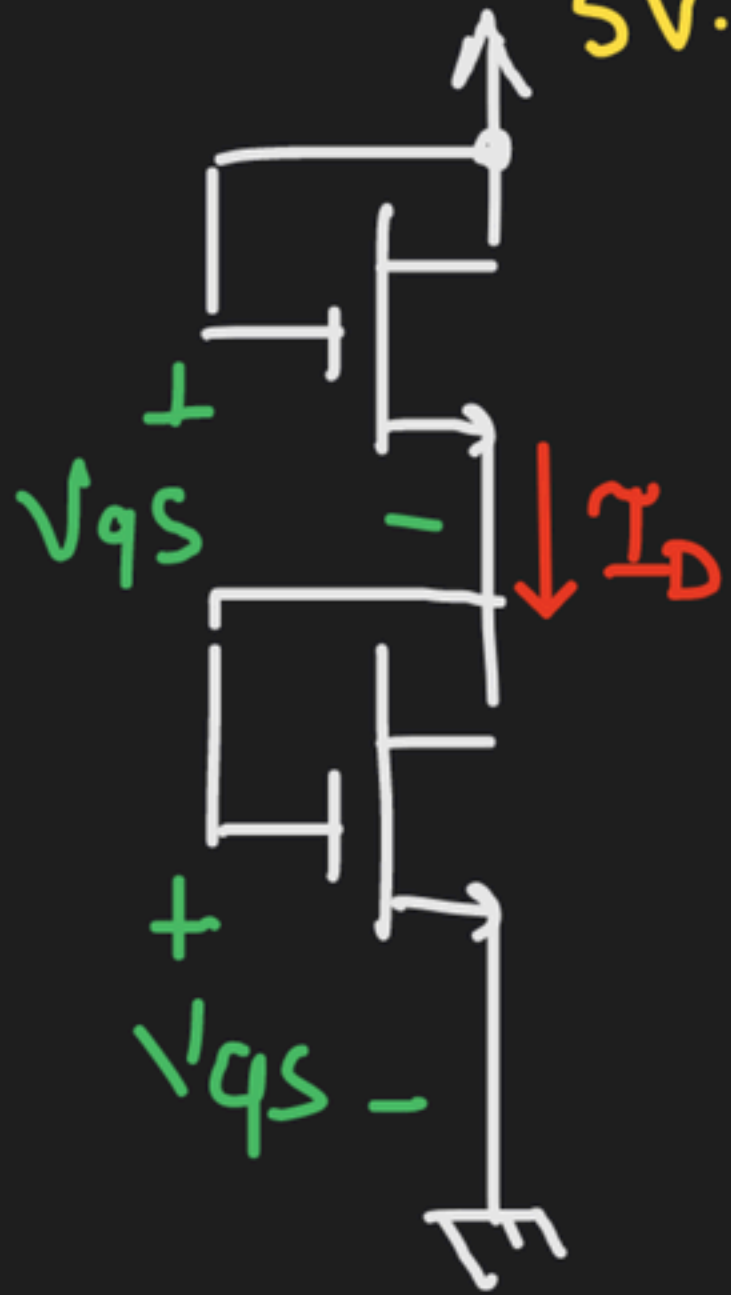

• $\mu_n C_{ox} \frac{W}{L}$ of both device = 1 mA/V^2

$$V_{th} = 1$$

• Step 1 Both in Sat

Identical device, V_{gs} same

$$5 = 2V_{gs}$$

$$\underline{V_{gs} = 2.5}$$

$$I_D = \frac{1}{2} \times 1 \times (2.5 - 1)^2 = \underline{1.125 \text{ mA}}$$

Q

Find I_D

10V.



$$\mu_n C_{ox} \frac{W}{L} = 1 \text{ mA/V}^2$$

$$V_{th} = 1 \text{ V}$$

Q

Find I_D



$$\mu_n C_{ox} \frac{W}{L} = 2 \text{ mA/V}^2$$

$$\mu_n C_{ox} \frac{W}{L} = 4 \text{ mA/V}^2$$

$V_{th} = 1 \text{ V}$ for both
Find I_D .

Since device shd be in sat-

$$V_{GD} < V_{th}$$

$$V_G - V_D < V_{th}$$

$$V_D > V_G - V_{th}$$

$$\underline{V_{DS} > V_{GS} - V_{th}}$$

▲ 1 • Asked by Anisha

Please help me with this doubt

Common Data For Q. 5 and 6 :

A p -channel depletion mode MOSFET has the following parameters

$$K_p = 0.5 \text{ mA/V}^2, V_{TH} = 2 \text{ V}$$

If $V_{SG} = 0$, current I_D for $V_{SD} = 1 \text{ V}$ is


(A) 0 mA

(B) 1.5 mA

(C) 2 mA


(D) 0.5 mA

MCQ 4.1.5

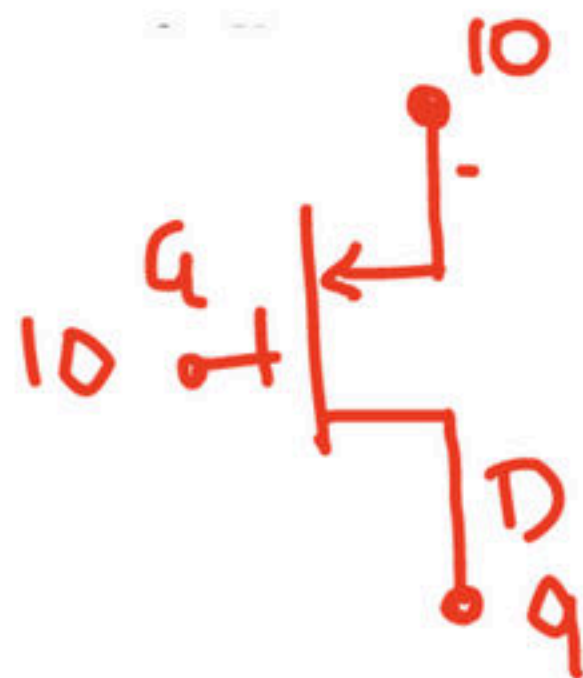

$$V_{GS} < V_{th}$$

$$10 - 9 < 2 \text{ Ohmic}$$

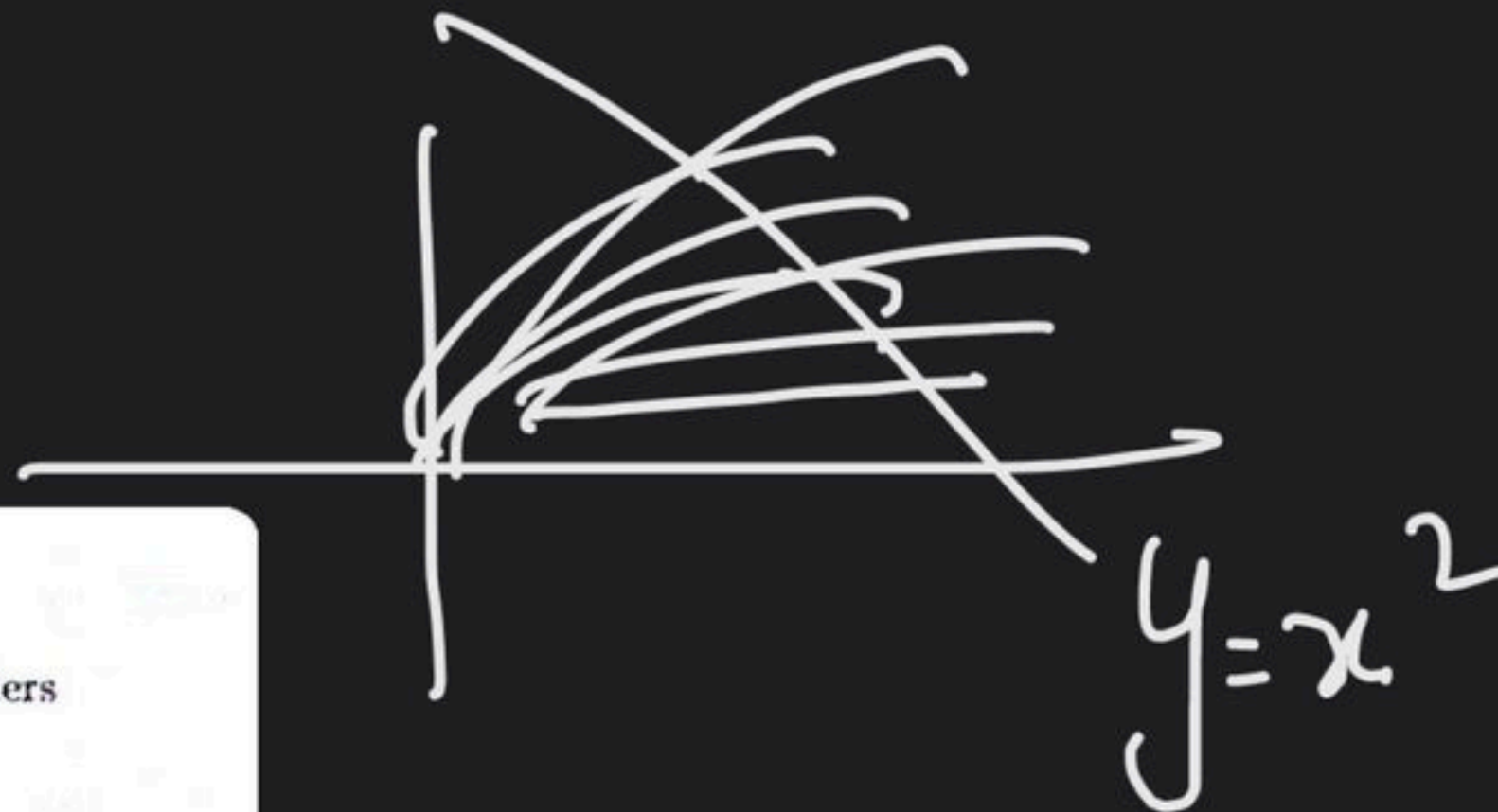

$$\text{and } y = 5$$









▲ 1 • Asked by Yuvraj


output resistance mai problem hai???

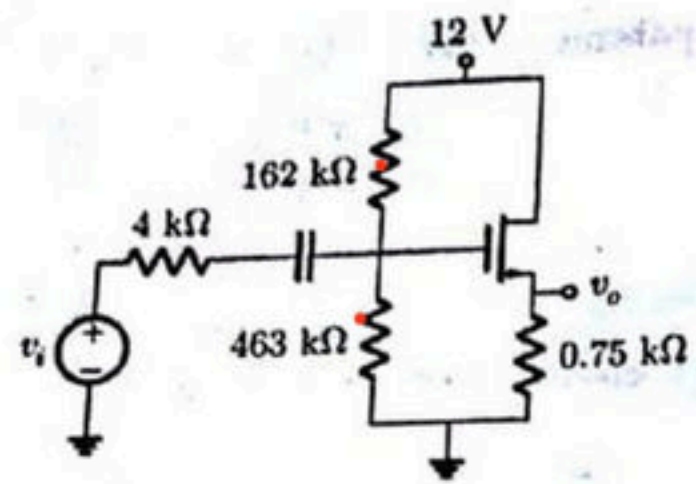

⇒

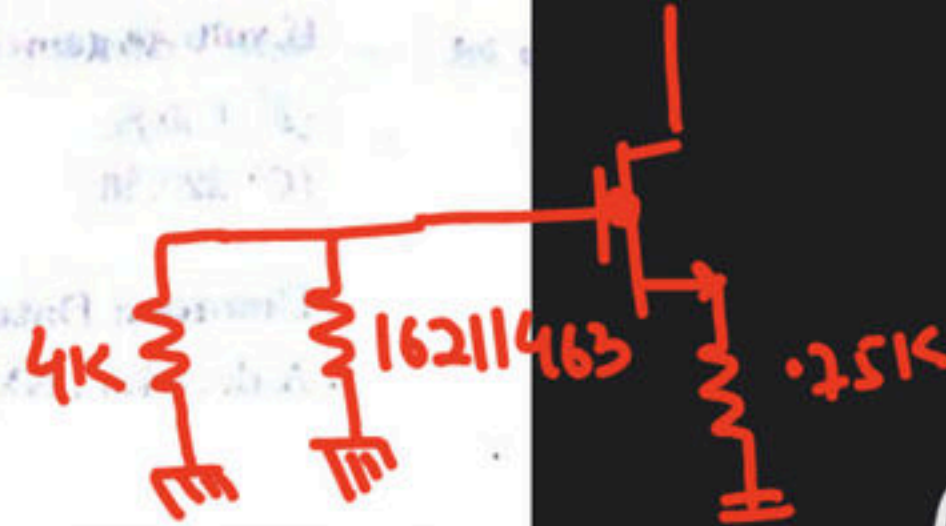

⇒

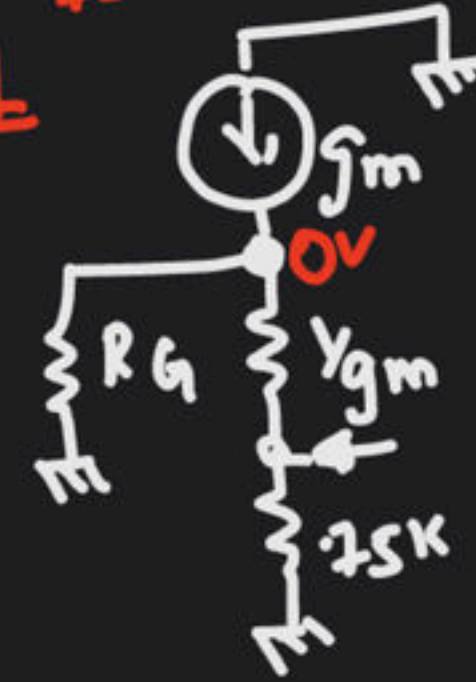

$$R = (25k \parallel r_o) \parallel R_{gs}$$

- MCQ 5.1.15 Small signal transconductance is
 (A) 29.52 mA/V
 (B) 59.04 mA/V
 (C) 11.3 mA/V
 (D) 5.65 mA/V
- MCQ 5.1.16 The small signal voltage gain $A_v = \frac{v_o}{v_i}$ is
 (A) 1.20
 (B) 0.86
 (C) 1.13
 (D) 0.98
- MCQ 5.1.17 Output resistance of the amplifier circuit is
 (A) 707 Ω
 (B) 12.5 k Ω
 (C) 67.1 Ω
 (D) 78.7 Ω