

# Analog Electronics - LVIII

Lakshya GATE 2023: Course on Analog Electronics for ECE EE IN




The image features a motivational quote in white, bold, sans-serif capital letters. The text is arranged in six lines and is centered within a rectangular frame defined by a thin red border. The background of the frame is a photograph of a rugged, rocky mountain peak under a hazy, overcast sky. The mountain's surface is dark and textured, with some lighter patches where the rock is more exposed. The sky is a pale, muted blue-grey. The overall composition is simple and impactful, with the text being the primary focus.

**DON'T LET  
ONE BAD DAY  
MAKE YOU  
FEEL LIKE YOU  
HAVE A BAD  
LIFE.**



Q1

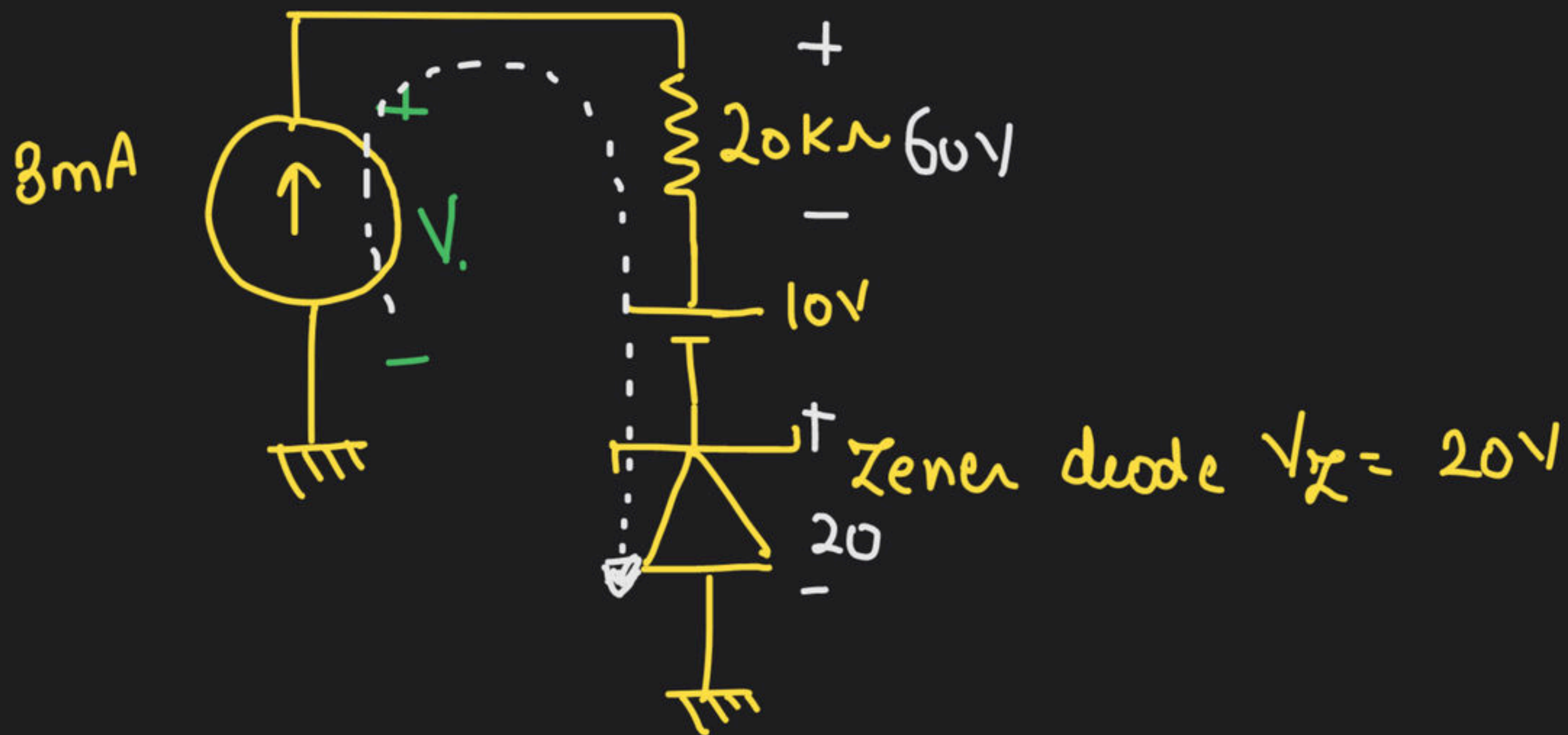



a) 0

b) 30

c) 70

☒ d) 90

# Velocity Saturation $\Rightarrow$

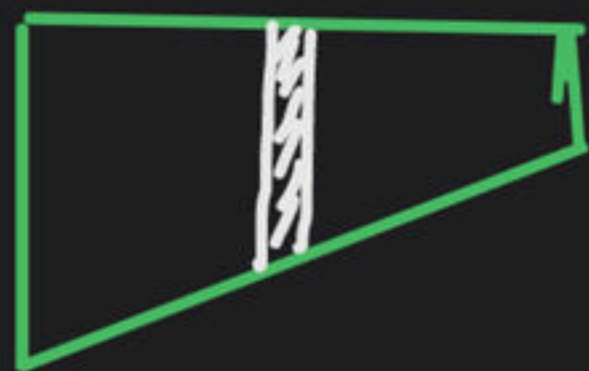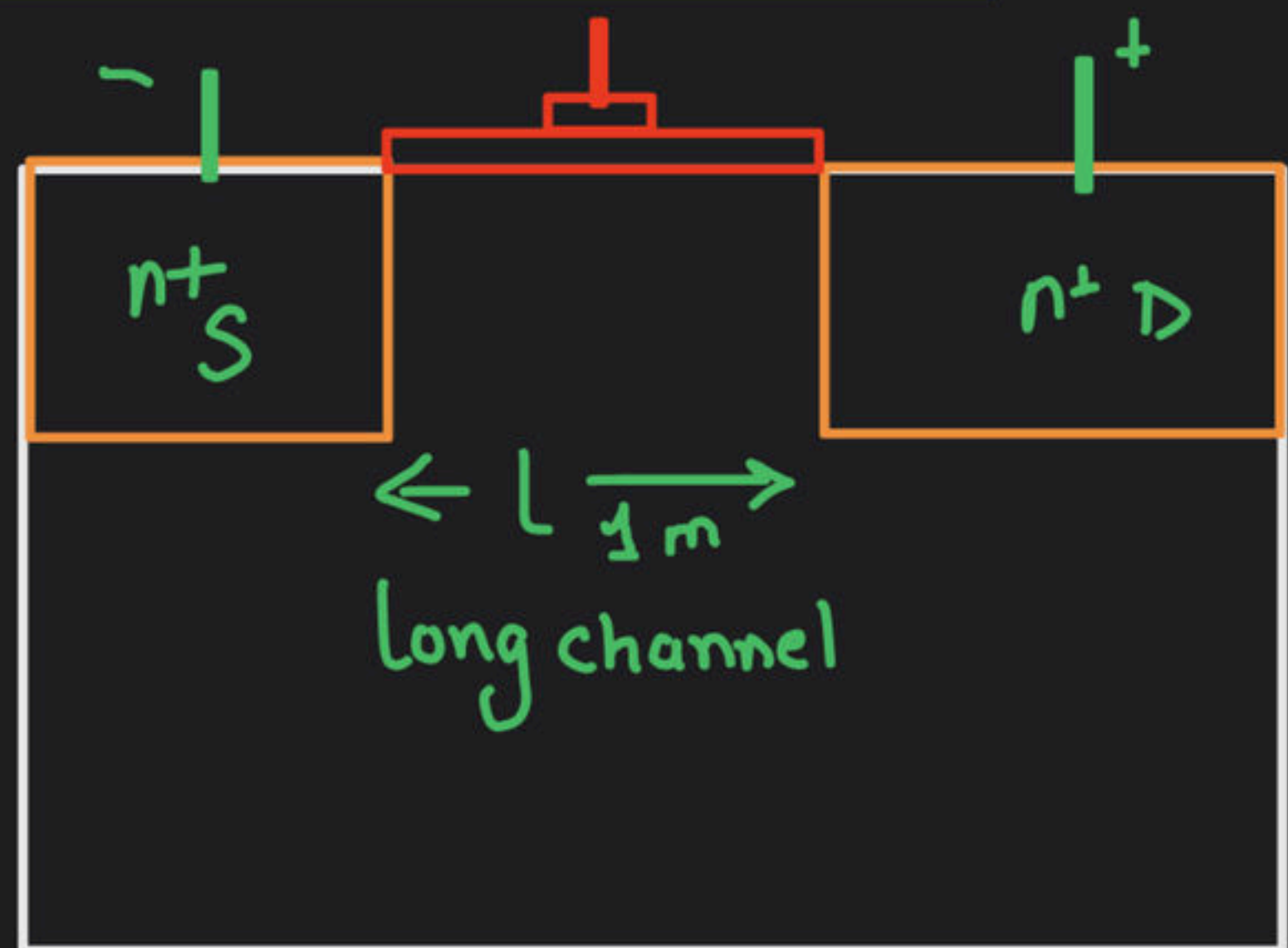

why velocity Saturation :- because when channel

$$Q(x) = C [V_{GS} - V(x) - V_{th}] \omega \cdot \Delta x$$


$$I_- = \frac{dQ}{dt} = C [V_{GS} - V(x) - V_{th}] \omega \underbrace{\frac{\Delta x}{\Delta t}}$$

$$v = \mu E(x)$$

- due to velocity Sat. the  $\frac{\Delta x}{\Delta t}$  i.e. velocity is const.



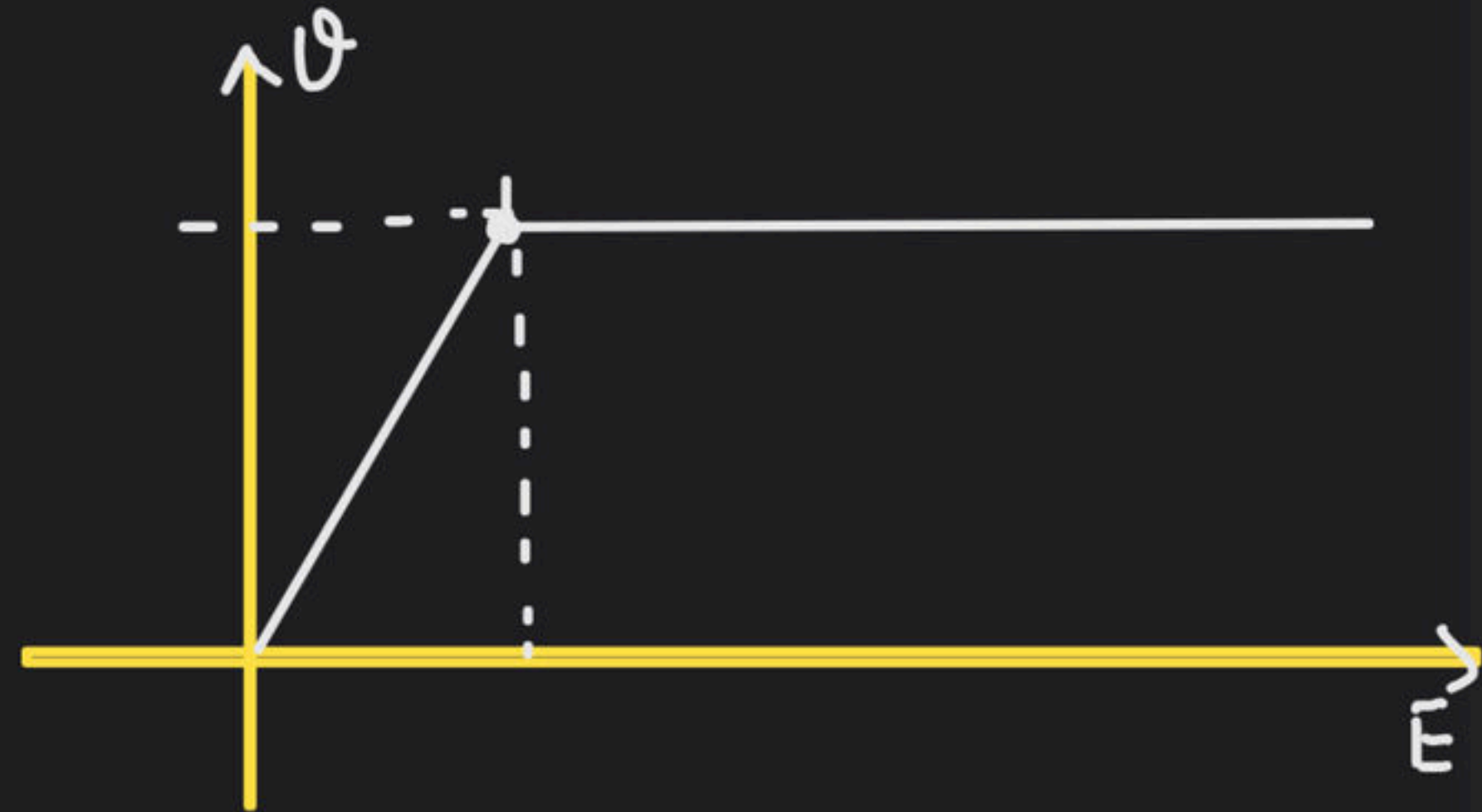length reduces then the Electric field in channel  
obtain a very high value that leads to saturated  
or fixed velocity of charges



So Now Current of the  
device

$$I = C [V_{GS} - V(x) - V_{th}] \omega \cdot \{v_{sat}\}$$

So what happen due to velocity Saturation:-

Reason :-

Reducing channel length of device

It leads to

1. When Velocity Sat Occur then the device  
Current is independent of  $V_{DS}$

2.  $I_D$  in saturation  $\left\{ \text{Prop. to } (V_{GS} - V_{th})^2 \right\}$  but  
now it is prop to  $(V_{GS} - V_{th})$ .

3. If we use these MOSFET as amplifier then Gain reduces.

---



Body effect in MOSFET  $\Rightarrow$  only for ECE

(Nmos) (body p)

$$V_{th} = 2\phi_{FP} + \frac{qN_a x_d \tau}{C_{ox}} + \phi_{ms} - \frac{Q_{ox}}{C_{ox}}$$

$$V_{th} = 2\phi_{FP} + \frac{qN_a}{C_{ox}} \sqrt{\frac{2\epsilon}{qN_a} (2\phi_{FP} + V_{SB})} + \phi_{ms} - \frac{Q_{ox}}{C_{ox}}$$

$$g_m = \frac{\partial i_d}{\partial V_{gs}}$$

$$i_d = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$

$$\partial i_d / \partial V_{gs} = \left\{ \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) \right\}$$



So if the device has body effect then  $V_{th}$  depend on  $V_{SB}$  also. thus. ( $i_d$  in Sat mode)

$$i_d = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [V_{GS} - V_{th}]^2$$

$$\frac{\partial i_d}{\partial V_{SB}} = \frac{\partial i_d}{\partial V_{th}} \cdot \frac{\partial V_{th}}{\partial V_{SB}} = (-) \mu_n C_{ox} \frac{W}{L} [V_{GS} - V_{th}] \cdot \frac{q_v N_A}{C_{ox}} \sqrt{\frac{2\epsilon}{q_v N_A}}$$

$\frac{1}{2} (2\phi_{fp} + V_{SB})^{-1/2}$


$$\frac{\partial i_d}{\partial V_{SB}} = -g_m \frac{1}{C_{ox}} \sqrt{2\epsilon q_v N_A} \frac{1}{2} (2\phi_{fp} + V_{SB})^{-1/2}$$

$$\frac{\partial i_d}{\partial V_{bs}} =$$

$$g_m \frac{\sqrt{2qNa\epsilon}}{C_{ox}} \frac{1}{2} \left[ 2\phi_{FP} + V_{SB} \right]^{-1/2}$$

$g_{mb}$

Body Gate  
Back Gate

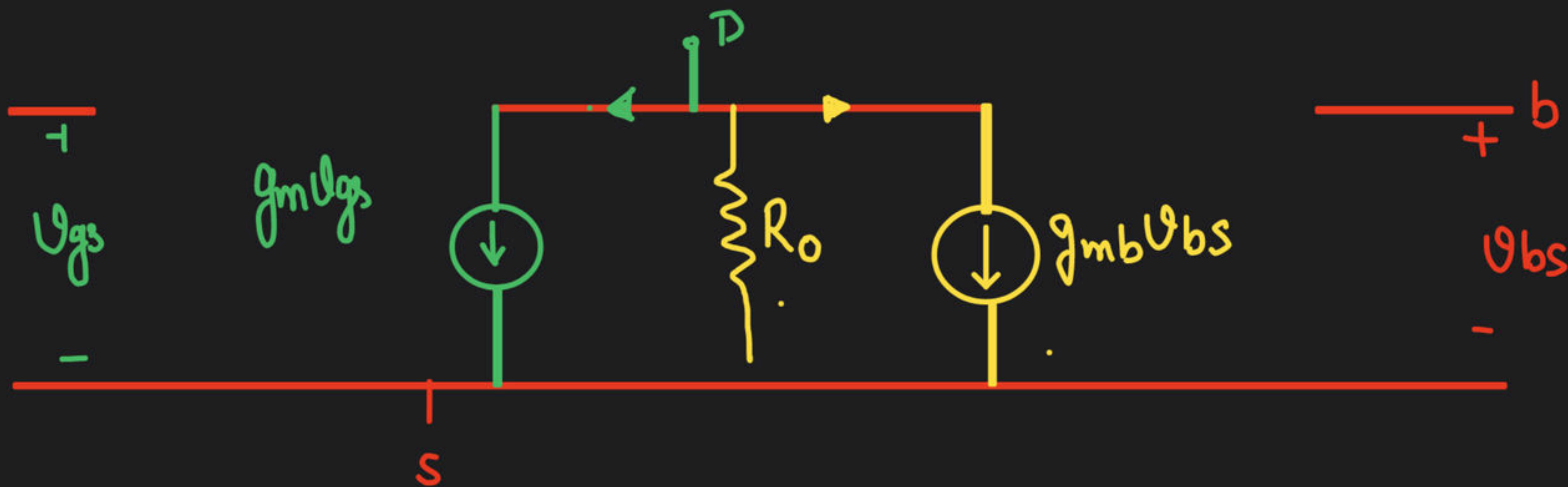



$V_{SB} \uparrow \rightarrow V_{th} \uparrow \rightarrow I_{Ddec}$

NMOS



$$\frac{\partial I_D}{\partial V_{SB}} = -ve$$

$$\frac{\partial I_D}{\partial V_{BS}} = +ve$$

Q

$V_i > 2$

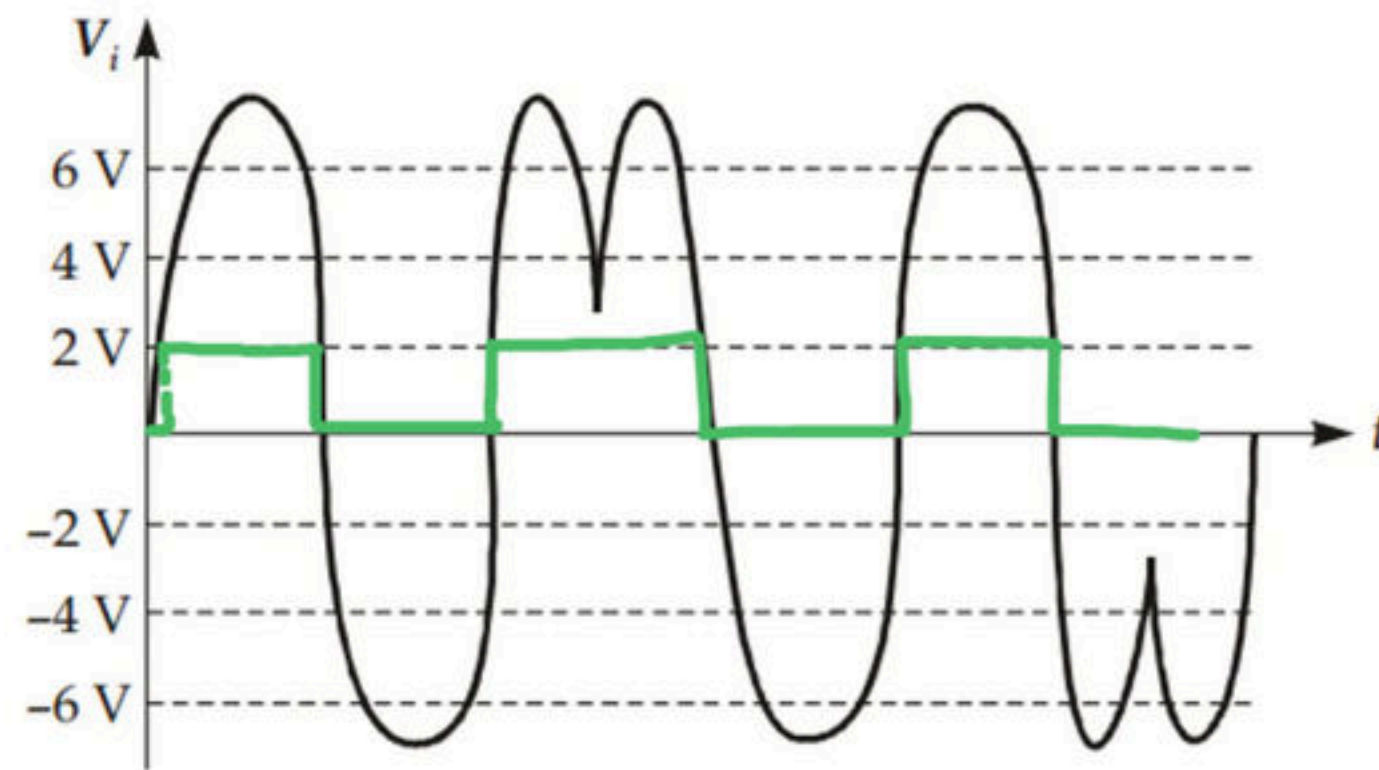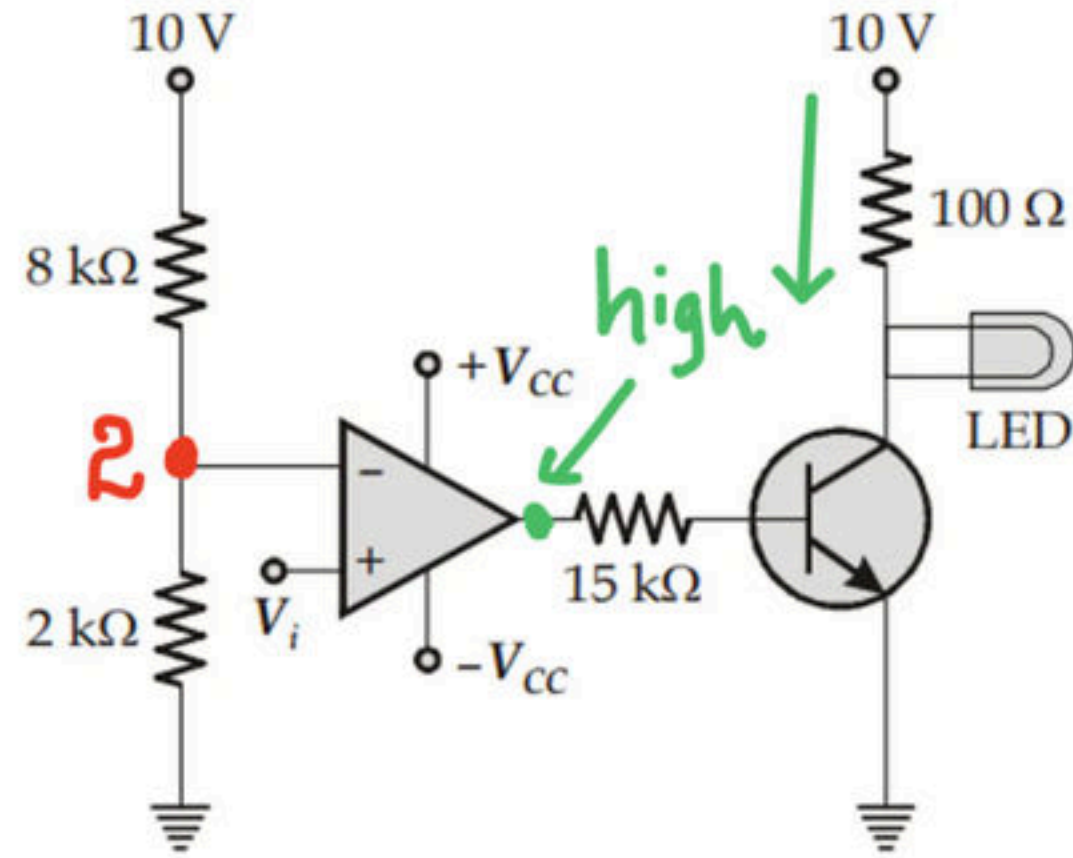Q.66 The following signal  $V_i$  of peak voltage 8 V applied to the non-inverting terminal of an ideal op-amp. The transistor has  $V_{BE} = 0.7$  V,  $\beta = 100$ ,  $V_{LED} = 1.5$  V,  $V_{CC} = 10$  V and  $-V_{CC} = -10$  V.




The number of times the LED glows is \_\_\_\_\_.

[EC-2016 : 1 Mark]

- ~~a) 3~~
- b) 2
- c) 4
- d) 5



Q11

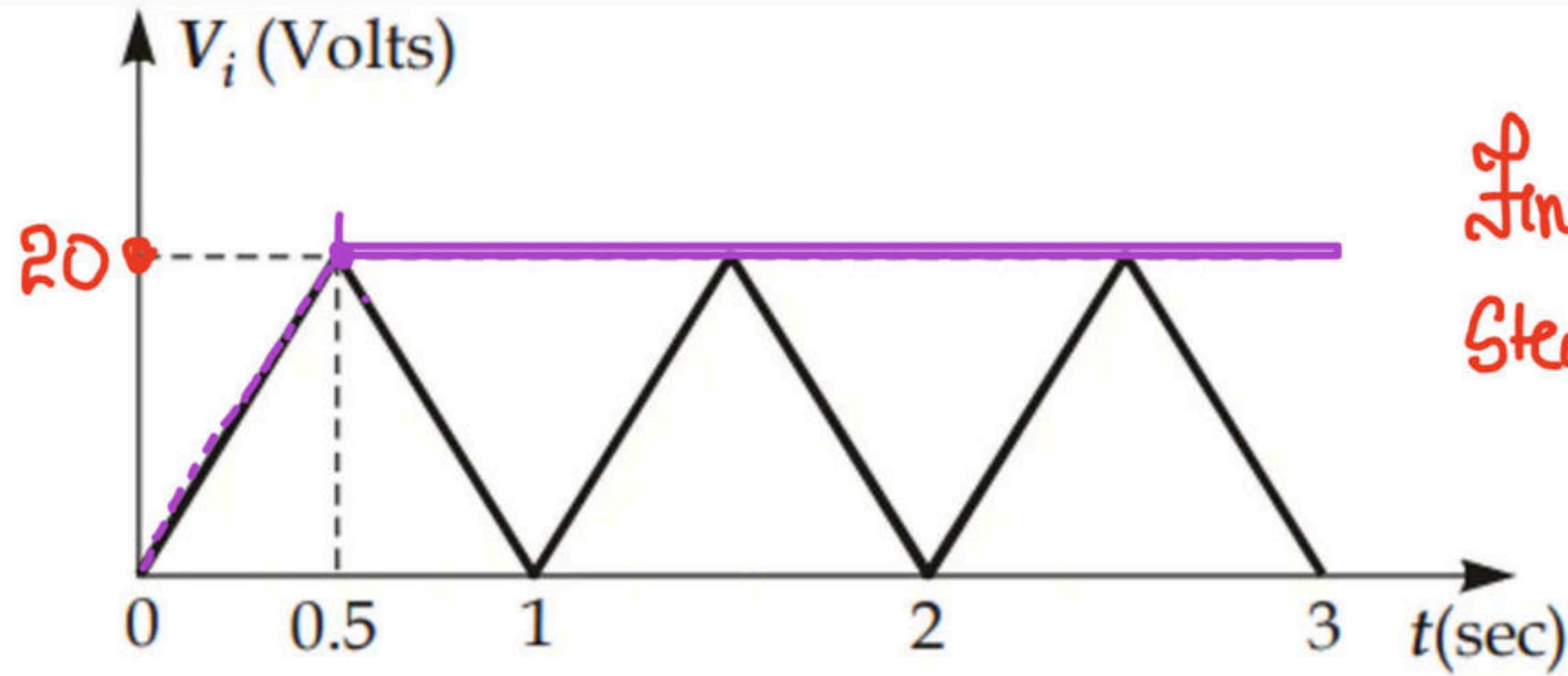



Find avg value of o/p @  
Steady state

a) 10

b) 15


~~c) 20~~

d) 25

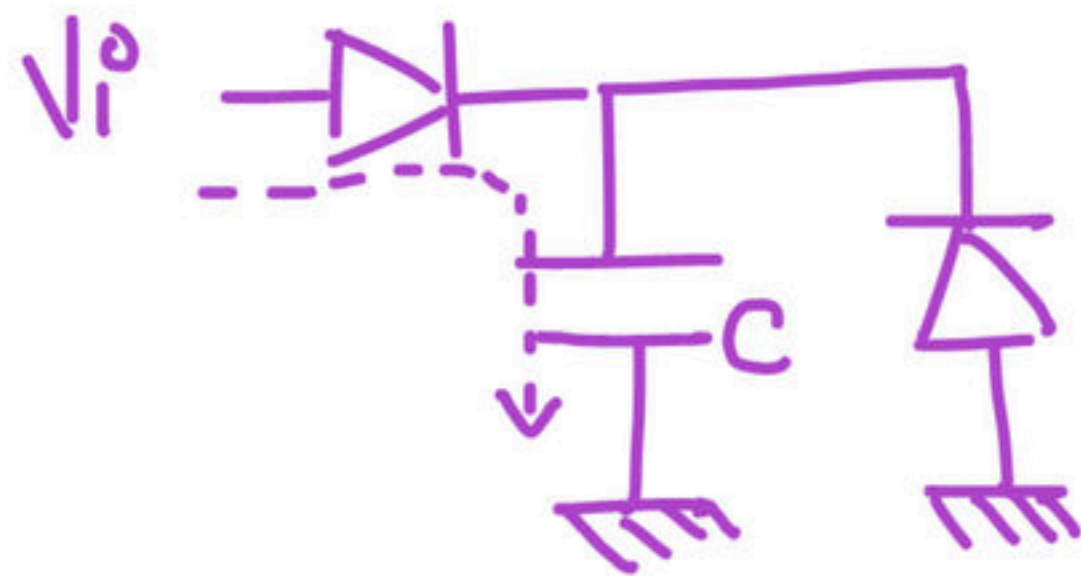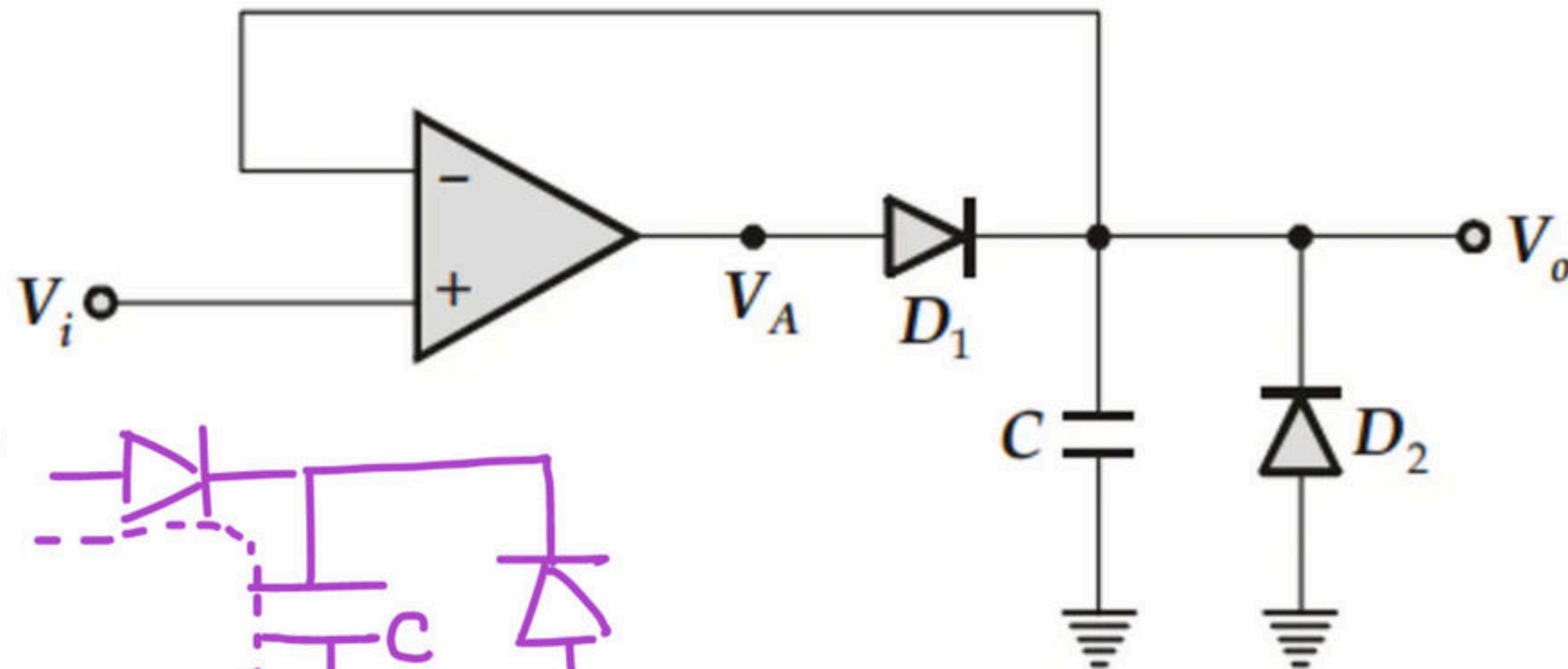

[EE-1992 : 2 Marks]

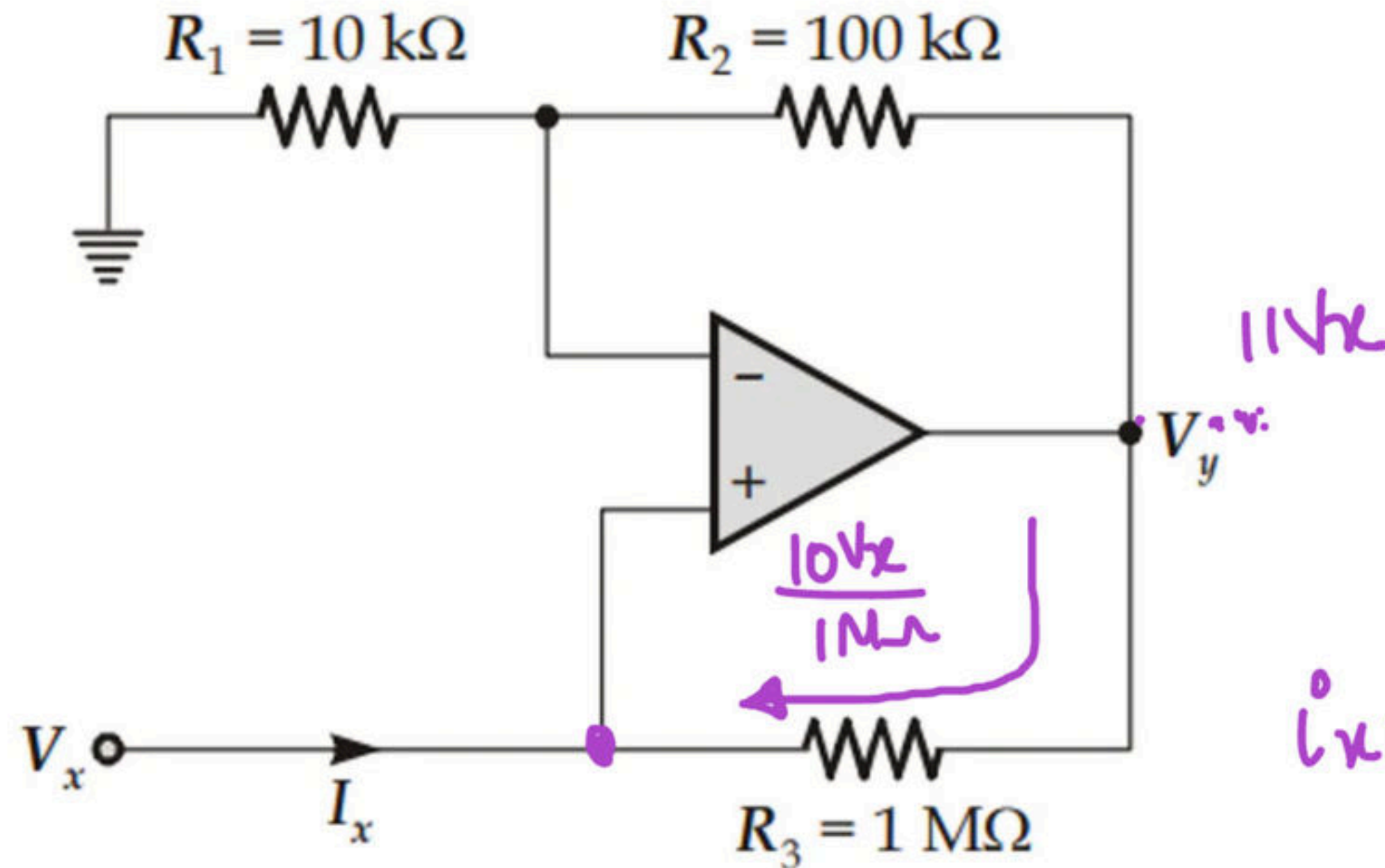The input resistance  $R_{IN} (= V_x/I_x)$  of the circuit in figure is



- (a)  $+100\text{ k}\Omega$   
 (c)  $+1\text{ M}\Omega$

- ☒ (b)  $-100\text{ k}\Omega$   
 (d)  $-1\text{ M}\Omega$


[EE-2004 : 2 Marks]

$$i_x = -\frac{10\text{V}}{1\text{M}\Omega}$$

$$\frac{V_x}{i_x} = -\frac{10^6}{10}$$





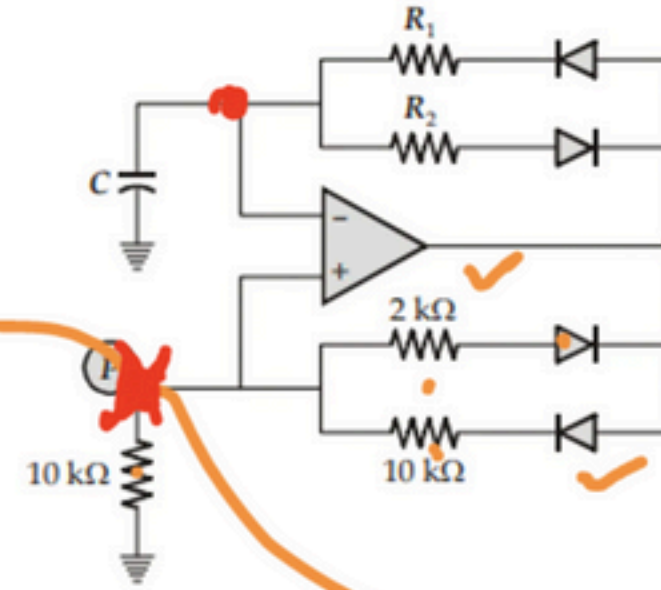
Q.18 A relaxation oscillator is made using op-amp as shown in figure. The supply voltages of the op-amp are  $\pm 12\text{ V}$ . The voltage waveform at point  $P$  will be



⑥


$V_p = ?$   
12/-12

-10

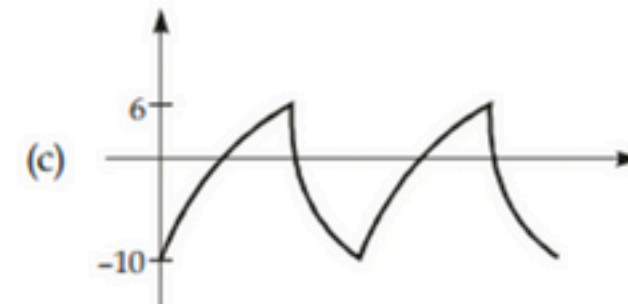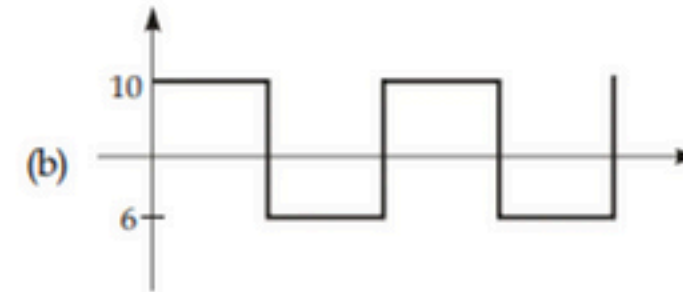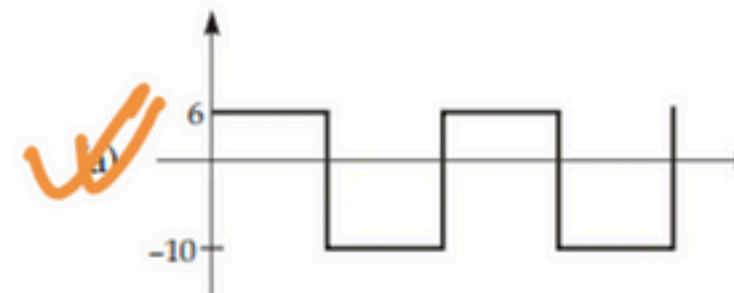

Q

Consider the circuit shown in the figure. In this circuit  $R = 1 \text{ k}\Omega$ , and  $C = 1 \mu\text{F}$ . The input voltage is sinusoidal with a frequency of 50 Hz, represented as a phasor with magnitude  $V_i$  and phase angle 0 radian as shown in the figure. The output voltage is represented as a phasor with magnitude  $V_o$  and phase angle  $\delta$  (in radian) relative to the phase angle of the input voltage?

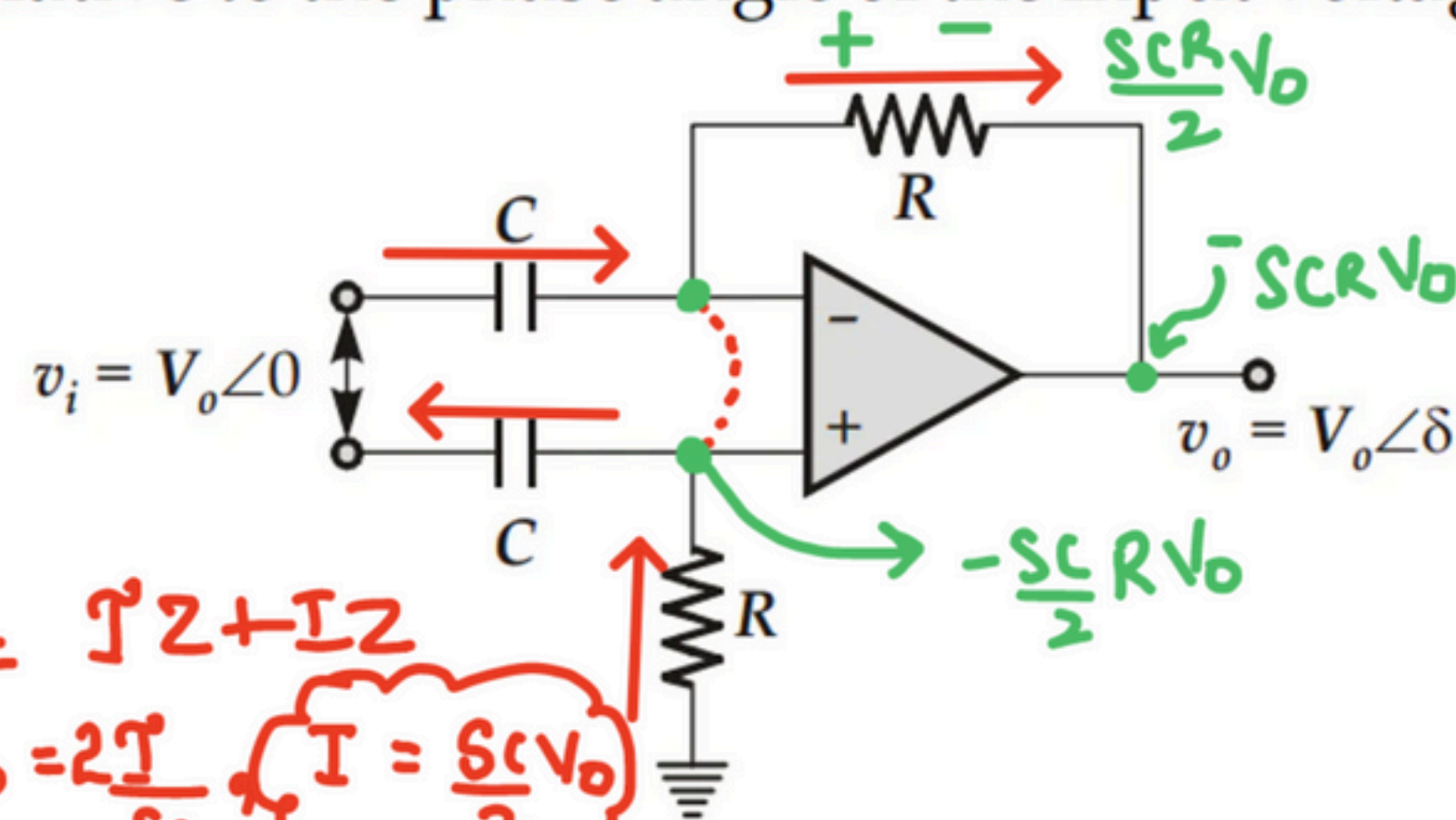

$$V_o = IZ + IZ$$

$$V_o = 2 \frac{I}{sC} \quad \text{where} \quad I = \frac{sCV_o}{2}$$

(a) 0

(b)  $\pi$

(c)  $\frac{\pi}{2}$

~~(d)~~  $-\frac{\pi}{2}$

$$V_{out} = -sCRV_o$$

$$= -j\omega CRV_o$$


$$= -90^\circ$$

[EE-2015 : 1 Mark]



Q

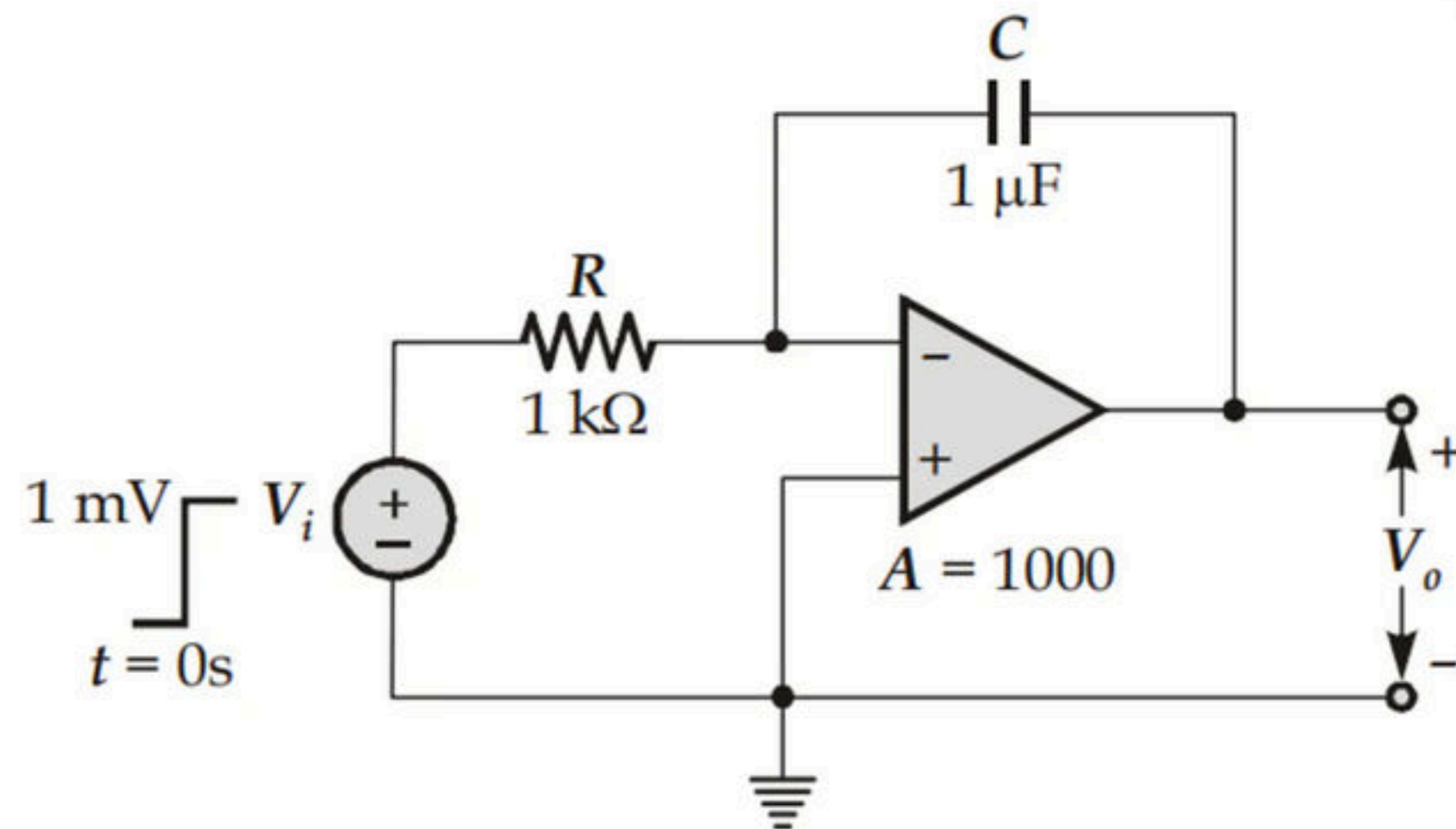
The op-amp shown in the figure has a finite gain  $A = 1000$  and an infinite input resistance. A step voltage  $V_i = 1 \text{ mV}$  is applied at the input at time  $t = 0$  as shown. Assuming that the operational amplifier is not saturated, the time constant (in millisecond) of the output voltage,  $V_o$ , is  $\frac{1}{s}$



- (a) 1001  
(c) 11

- (b) 101  
(d) 1

[EE-2015 : 2 Marks]

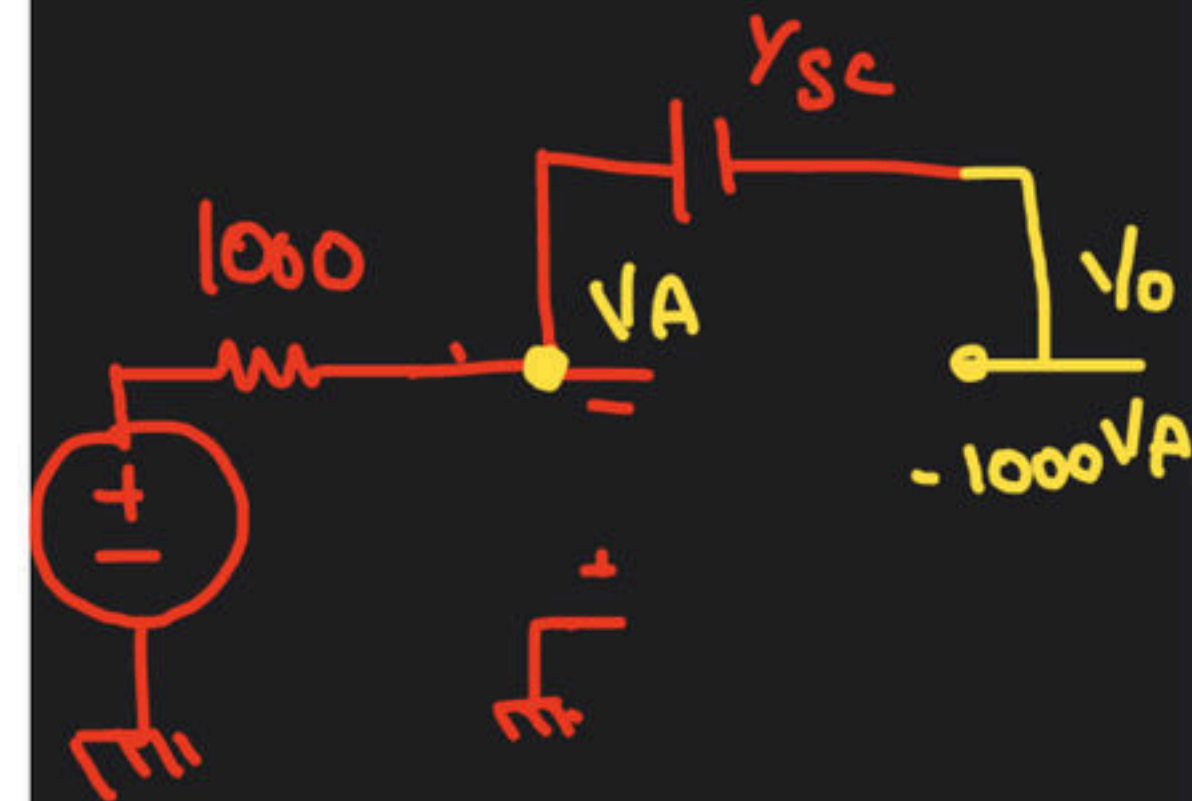

$$\frac{V_i - V_A}{1000} = \frac{V_A + 1000V_A}{1/s}$$

$$V_i = V_A [1001 \times 1000] s + V_A$$

$$V_i = V_A [1.001] s + V_A$$

$$V_A = \left[ \frac{V_i}{1 + 1.001s} \right]$$

$$V_o = -1000 \text{ V/A} = - \frac{1000 \text{ V/A}}{(1 + 1.001 \text{ s})}$$

$$= - \frac{1000 \text{ A} \times 10^{-3}}{s(1 + 1.001 \text{ s})}$$


$$= \left[ \frac{A}{s} + \frac{B}{s + \underbrace{1.001}_{\text{time constant}}} \right]$$

$$\rightarrow e^{-t/1.001}$$




Q

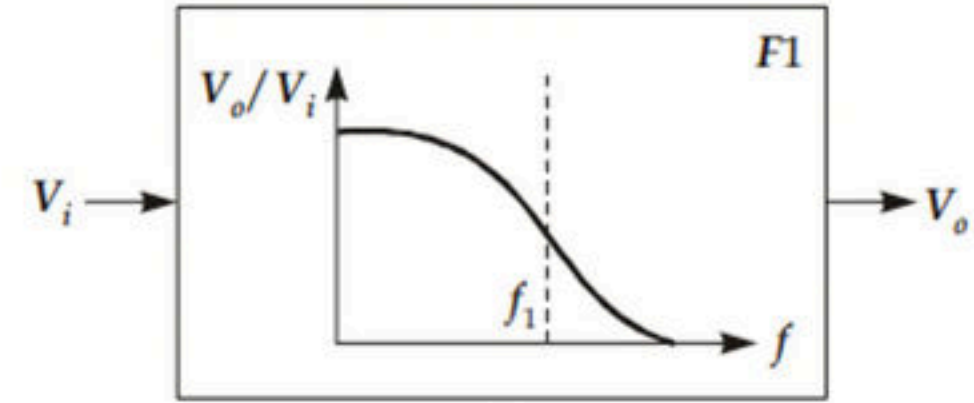
Q.41 The filters  $F1$  and  $F2$  having characteristics as shown in Fig. (a) and (b) are connected as shown in Fig. (c).



(a)

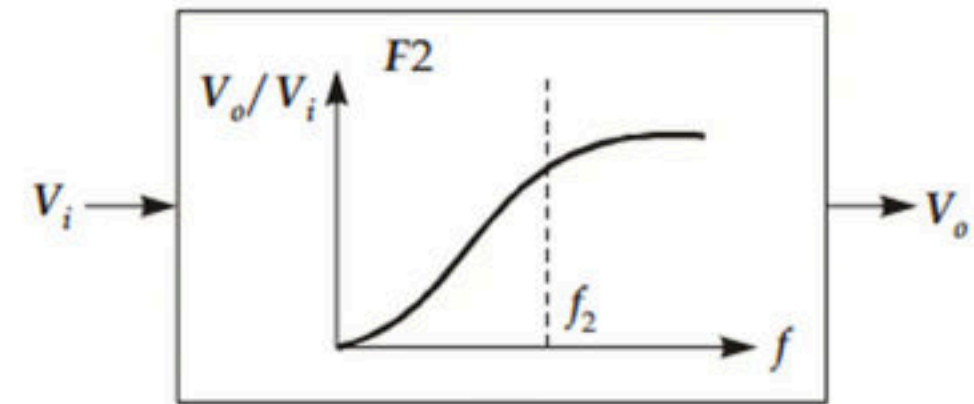

(b)

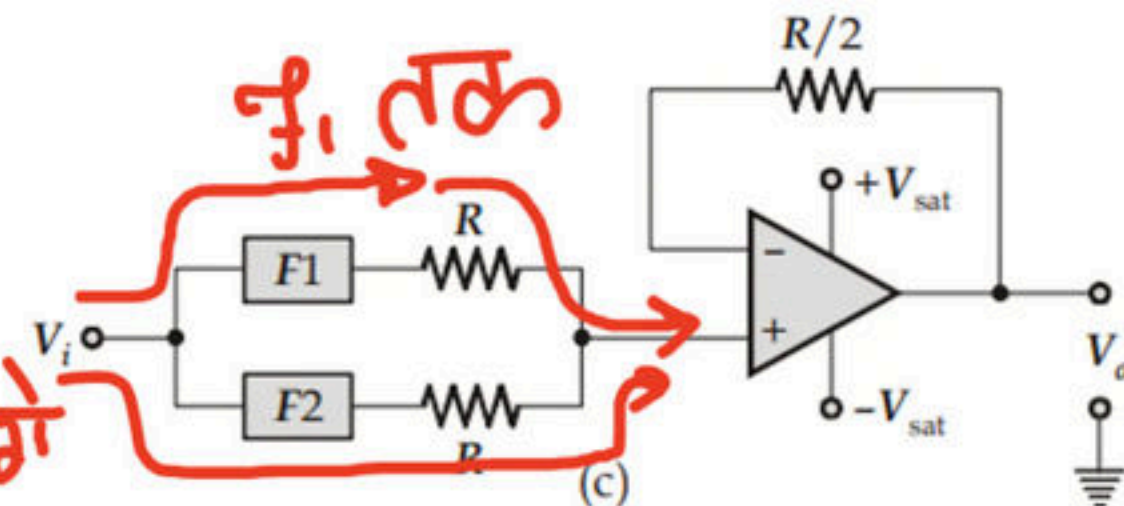

The cut-off frequencies of  $F1$  and  $F2$  are  $f_1$  and  $f_2$  respectively. If  $f_1 < f_2$ , the resultant circuit exhibits the characteristic of a

- (a) Band-pass filter (b) Band-stop filter  
(c) All-pass filter (d) High Q-filter


[EE-2015 : 1 Mark]

$Q = \frac{\omega_0}{\text{B.W.}}$



→ BPF with Small B.W.

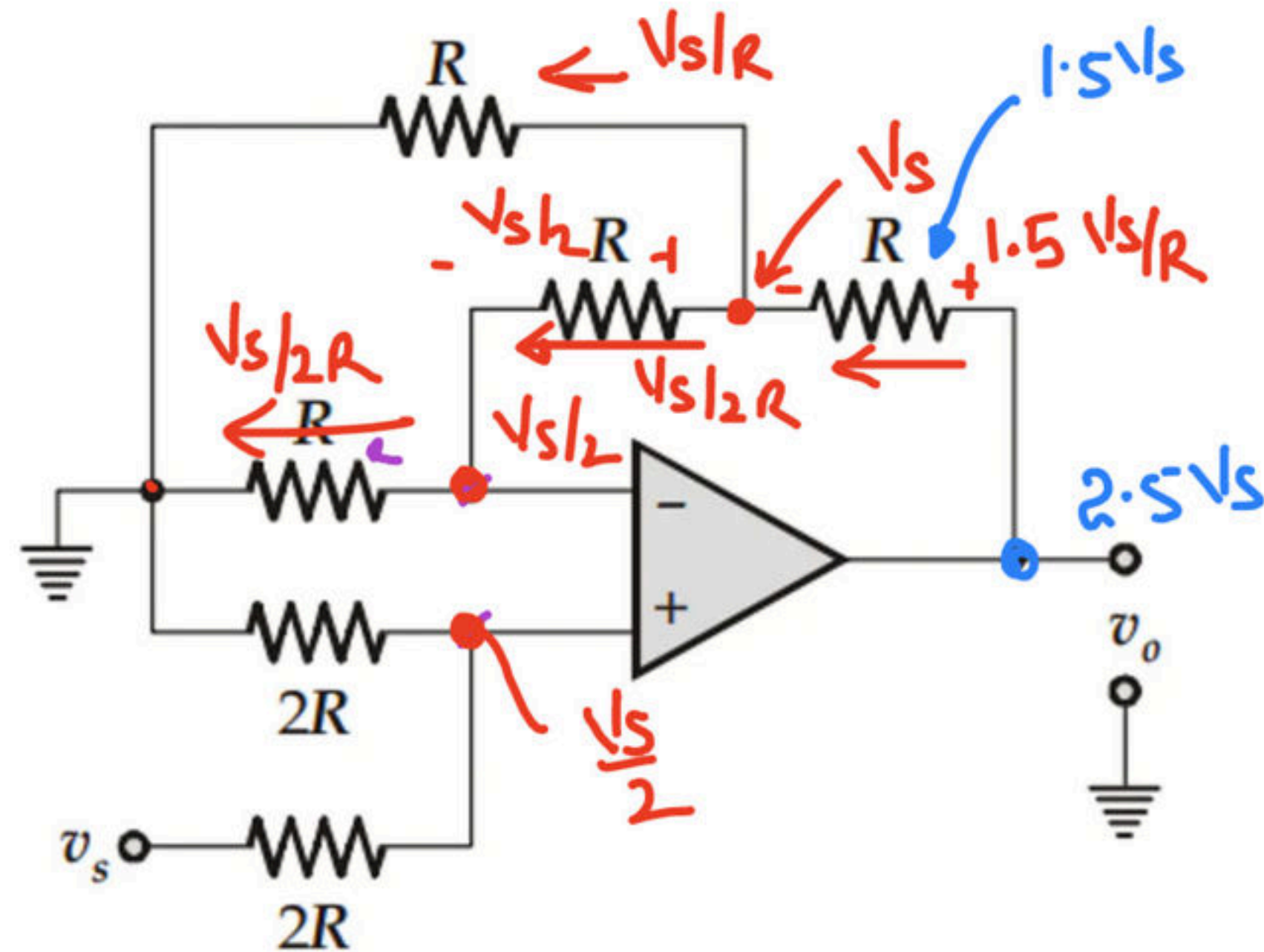For the circuit shown below, assume that the op-amp is ideal. Which one of the following is true?



(a)  $v_o = v_s$

(b)  $v_o = 1.5 v_s$

☒ (c)  $v_o = 2.5 v_s$

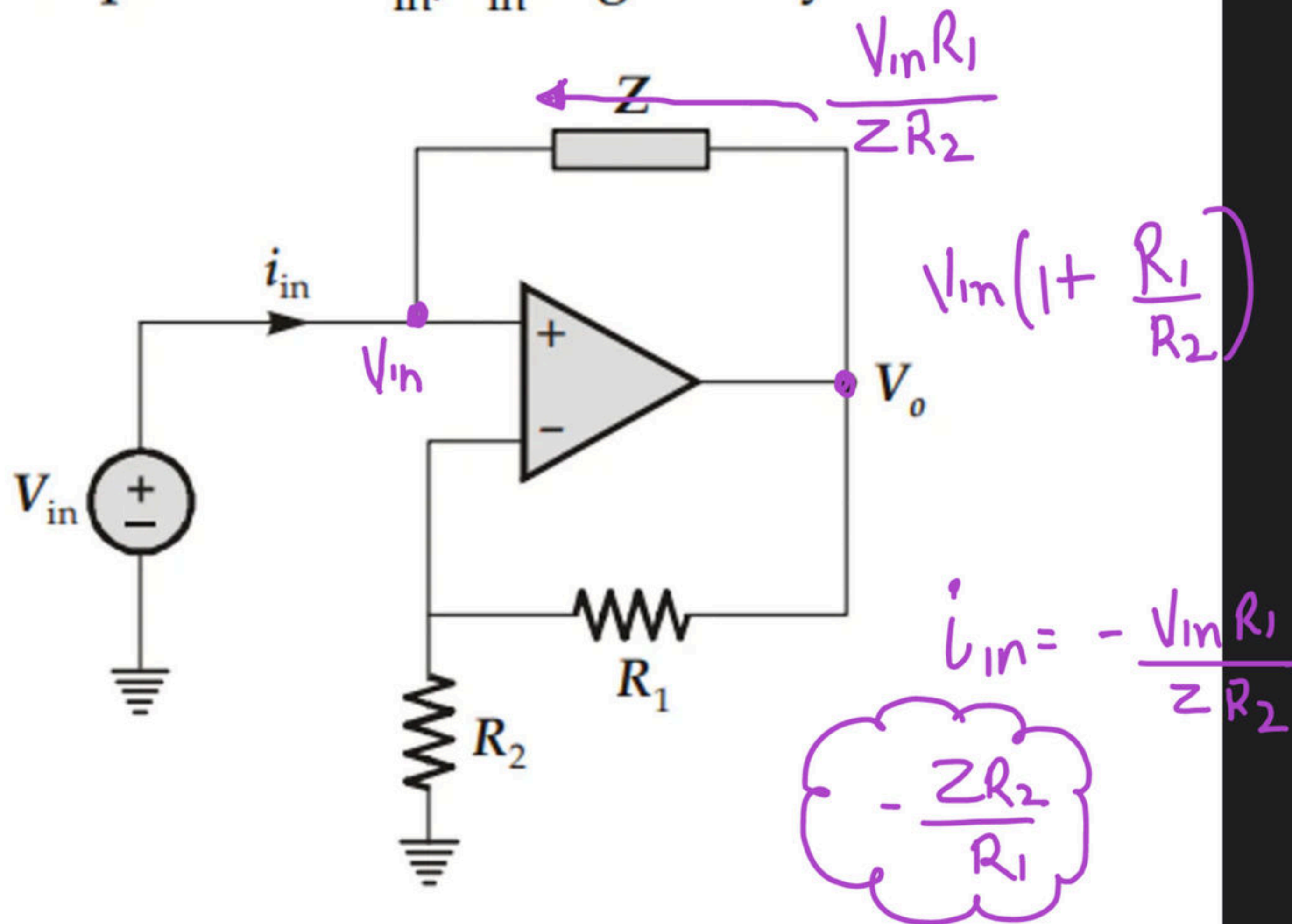
(d)  $v_o = 5 v_s$

[EE-2017 : 2 Marks]





The op-amp shown in the figure is ideal. The input impedance  $V_{in}/i_{in}$  is given by



(a)  $Z \frac{R_1}{R_2}$


~~(b)~~  $-Z \frac{R_2}{R_1}$

(c)  $Z$

(d)  $-Z \frac{R_2}{R_1 + R_2}$

[EE-2018 : 1 Mark]

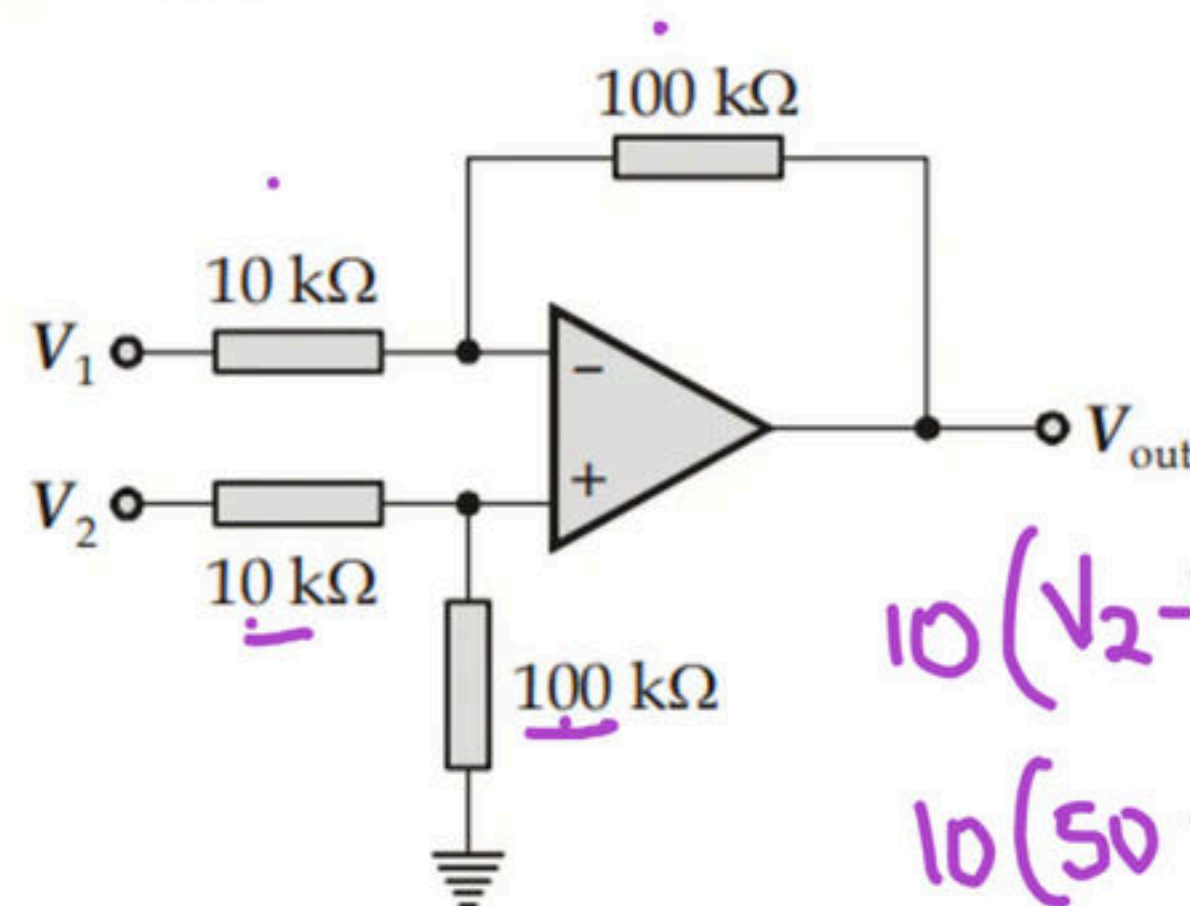Q.49 In the circuit below, the operational amplifier is ideal. If  $V_1 = 10$  mV and  $V_2 = 50$  mV, the output voltage ( $V_{out}$ ), is



$10(V_2 - V_1)$   
 $10(50 - 10) = 400$

~~(a)~~ 400 mV

(b) 500 mV

(c) 600 mV

(d) 100 mV

[EE-2019 : 2 Marks]



- (a) -1 V to -2 V      (b) -2 V to -4 V  
(c) +1 V to -2 V      (d) +2 V to -4 V

[EE-2014 : 2 Marks]

Q.26 A non-ideal diode is biased with a voltage of  $-0.03$  V, and a diode current of  $I_1$  is measured. The thermal voltage is  $26$  mV and the ideality factor for the diode is  $15/13$ . The voltage, (in V), at which the measured current increases to  $1.5I_1$  is closest to

- (a) -4.50      ~~(b) -0.09~~  
(c) -0.02      (d) -1.50


[EE-2020 : 2 Marks]

Q.27 Consider the diode circuit shown below. The diode,  $D$ , obeys the current-voltage characteristic,

$$I_D = I_s \left( \exp \left( \frac{V_D}{nV_T} \right) - 1 \right)$$

where  $n > 1$ ,  $V_T > 0$ ,  $V_D$  is the voltage across the diode and  $I_D$  is the current through it. The circuit

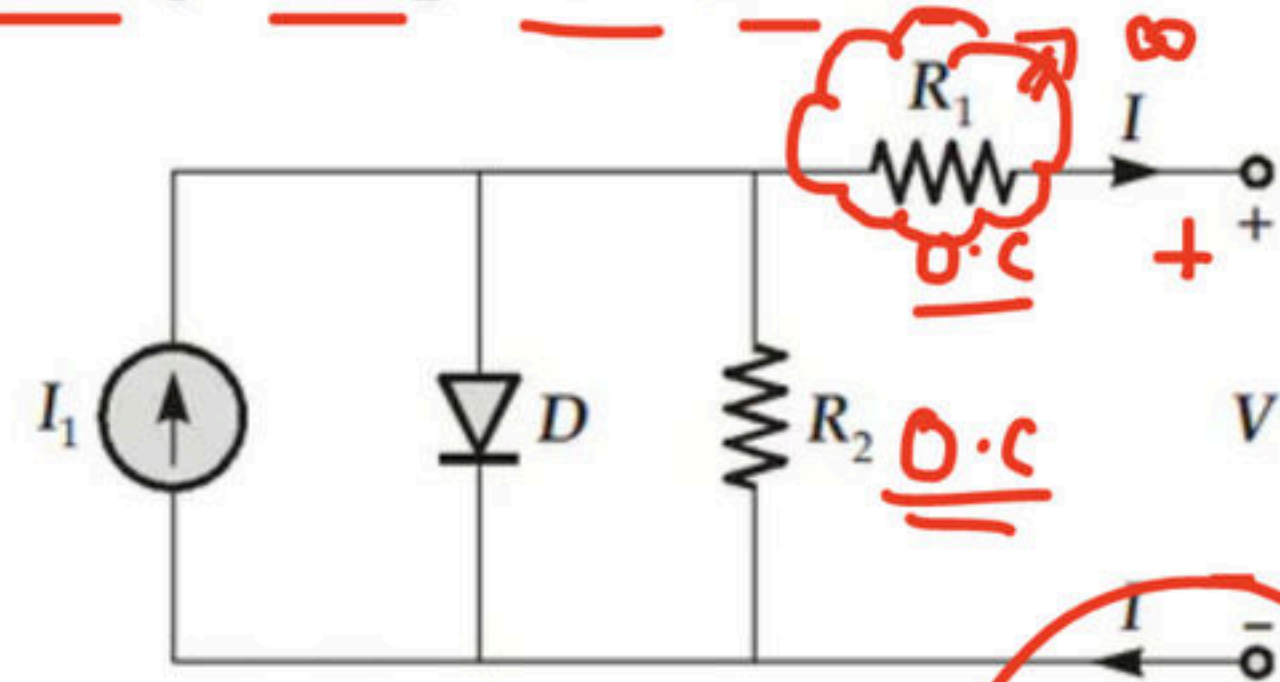is biased so that voltage,  $V > 0$  and current,  $I < 0$ . If you had a design this circuit to transfer maximum power from the current source ( $I_1$ ) to a resistive load (not shown) at the output, what values  $R_1$  and  $R_2$  would you choose?



- (a) ~~Small  $R_1$  and small  $R_2$~~   
(b) ~~Large  $R_1$  and large  $R_2$~~   
(c) Small  $R_1$  and large  $R_2$   
(d) ~~Large  $R_1$  and small  $R_2$~~

$R_1 = 0$   
 $R_2 = \infty$

[EE-2020 : 2 Marks]

$R_2 = 0$  large





$$I = I_s (e^{V/nV_T} - 1)$$

$$I_1 = -0.632 I_s$$

$$1.5 I_1 = -0.948 I_s = I_s (e^{V/nV_T} - 1)$$

$$V = -0.088 \dots$$

$$= -\underline{\underline{0.09}}$$





