



Analog Electronics - LVII

Lakshya GATE 2023: Course on Analog Electronics for ECE EE IN

**PUSH YOURSELF, BECAUSE NO ONE ELSE IS GOING TO
DO IT FOR YOU.**

Listbark.com

• Cascading of Amplifiers.

Amplifier with upper
cut off freq. ω_H
 $T.F = \left\{ \frac{A}{1 + s/\omega_H} \right\}$

We have connected n Amplifier
in Cascade



The overall T.F will be

$$@ \omega_H^* \text{ magnitude} = \frac{A^n}{\sqrt{2}}$$

$$\frac{A^n}{\left\{1 + \frac{\omega_H^{*2}}{\omega_H^2}\right\}^{n/2}} = \frac{A^n}{\sqrt{2}}$$

$$\frac{A^n}{[1 + s/\omega_H]^n}$$

→ @ Zero freq, magnitude is A^n .

→ new ω_H^* will be the
freq where magnitude is

$$\frac{A^n}{\sqrt{2}}$$

$$\left\{ 1 + \frac{\omega_H^{*2}}{\omega_H^2} \right\}^{n/2} = 2^{1/2}$$

$$\frac{\omega_H^{*2}}{\omega_H^2} = 2^{1/n} - 1$$

$$\omega_H^* = \sqrt{2^{1/n} - 1} \omega_H.$$

We have connected 'n' identical devices together

def T.F of a system is $\left\{ \frac{A s/\omega_L}{1 + s/\omega_L} \right\}$

we connect n identical Amplifier together,

$$\frac{A^n (s/\omega_L)^n}{(1 + s/\omega_L)^n}$$

@ new value of ω_L^* magnitude is $\frac{A^n}{\sqrt{2}}$

$$\frac{\cancel{A^n} (\omega_L^*/\omega_L)^n}{\left(1 + \frac{\omega_L^{*2}}{\omega_L^2}\right)^{n/2}} = \frac{\cancel{A^n}}{\sqrt{2}}$$

$$\sqrt{2} \left(\frac{\omega_L^*}{\omega_L}\right)^n = \left\{1 + \frac{\omega_L^{*2}}{\omega_L^2}\right\}^{n/2}$$

$$2 \left(\frac{\omega_L^{*2}}{\omega_L^2}\right)^n = \left(1 + \frac{\omega_L^{*2}}{\omega_L^2}\right)^n$$

$$2^{1/n} \frac{\omega_L^{*2}}{\omega_L^2} = 1 + \frac{\omega_L^{*2}}{\omega_L^2}$$

$$(2^{1/n} - 1) \omega_L^{*2} = \omega_L^2$$

$$\omega_L^* = \frac{\omega_L}{\sqrt{2^{1/n} - 1}}$$



• If we cascade n identical Amplifiers \Rightarrow

$$\omega_H^* = \sqrt{2^n - 1} \omega_H$$

$$\omega_L^* = \frac{\omega_L}{\sqrt{2^n - 1}}$$

Q

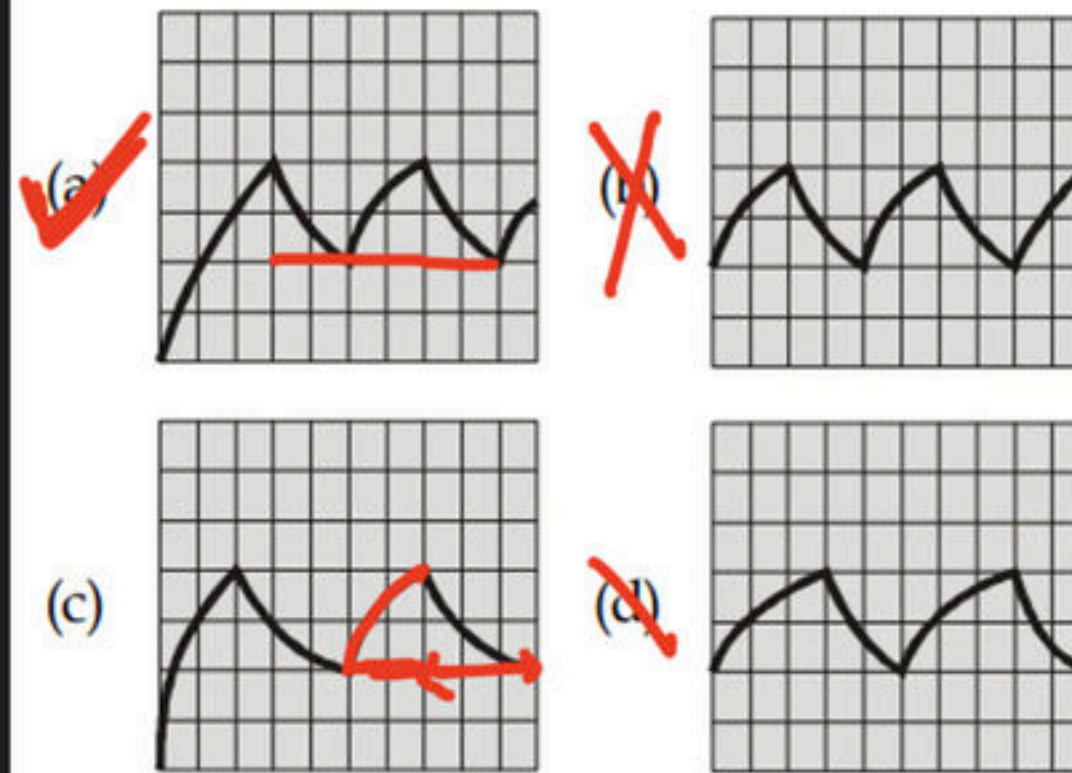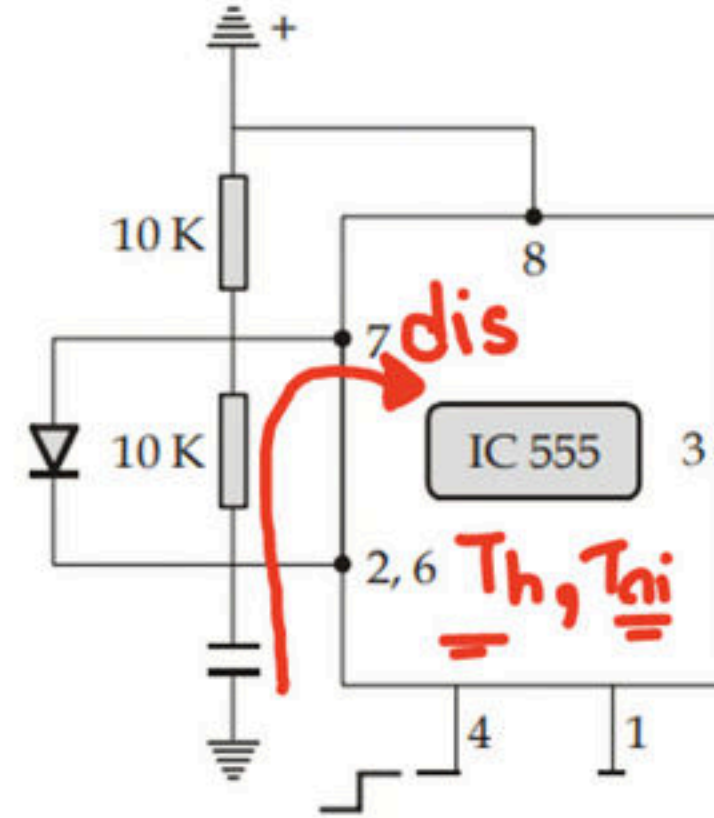
IC 555 in the figure is configured as an **astable** multivibrator. It is enabled to oscillate at $t = 0$ by applying a high input to pin 4. The pin description is 1 and 8-supply, 2-trigger, 4-reset, 6-threshold, 7-discharge. The waveform appearing across the capacitor starting from $t = 0$, as observed on a storage CRO is




[EE-2007 : 2 Marks]

$$RC = 10K \cdot C$$


$$RC = 10K \cdot C$$



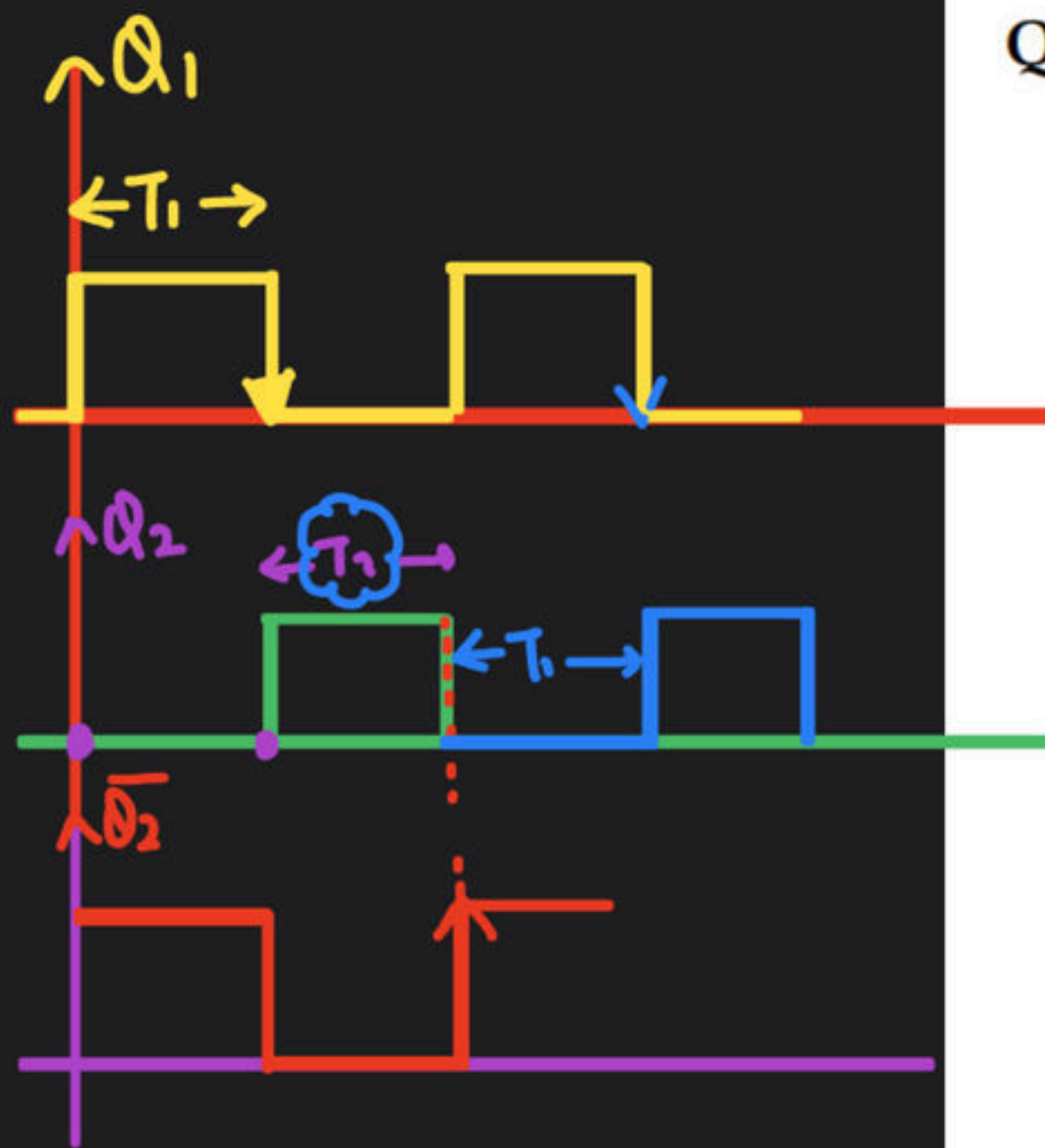


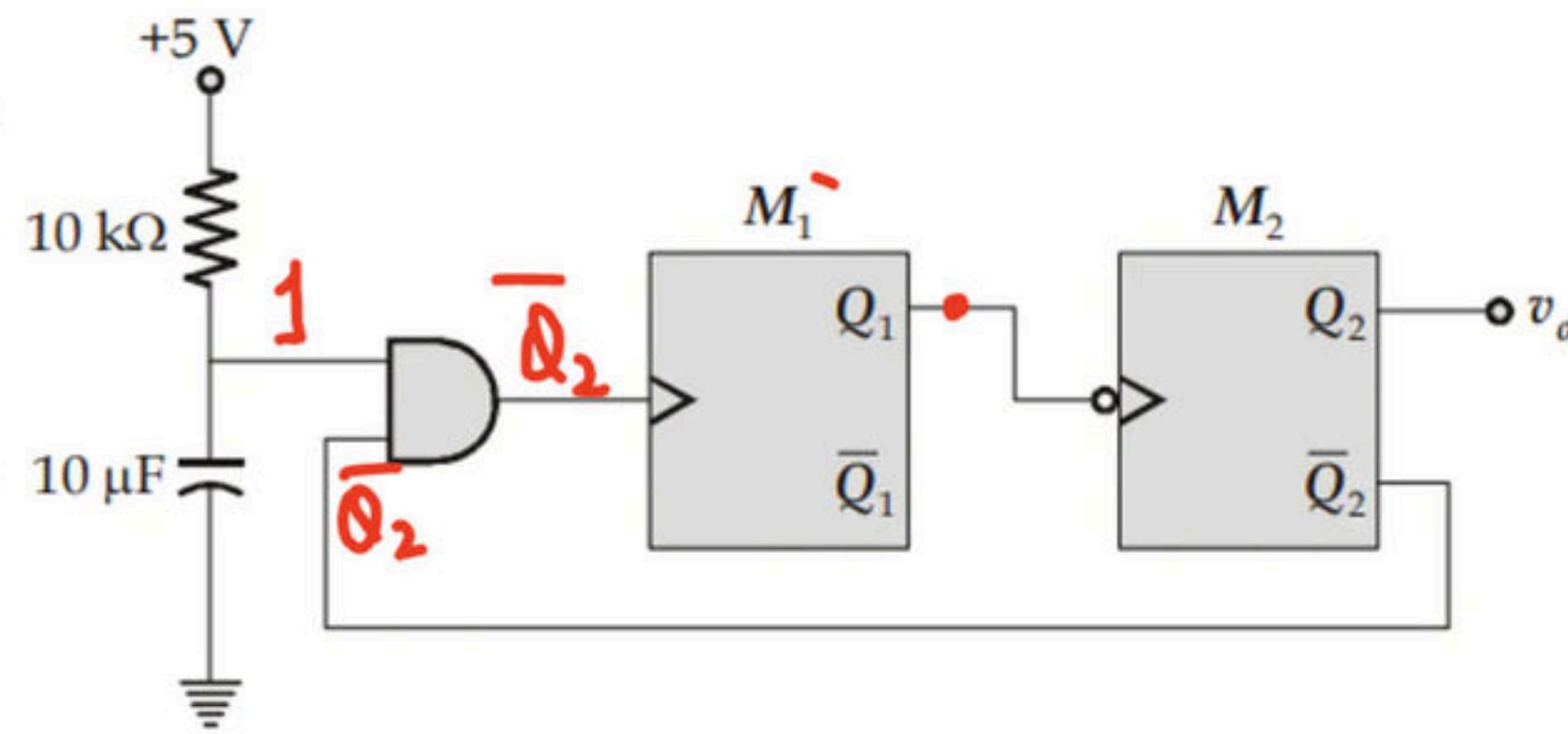Q.6 Two monoshot multivibrators, one positive edge triggered (M_1) and another negative edge triggered (M_2), are connected as shown in figure.



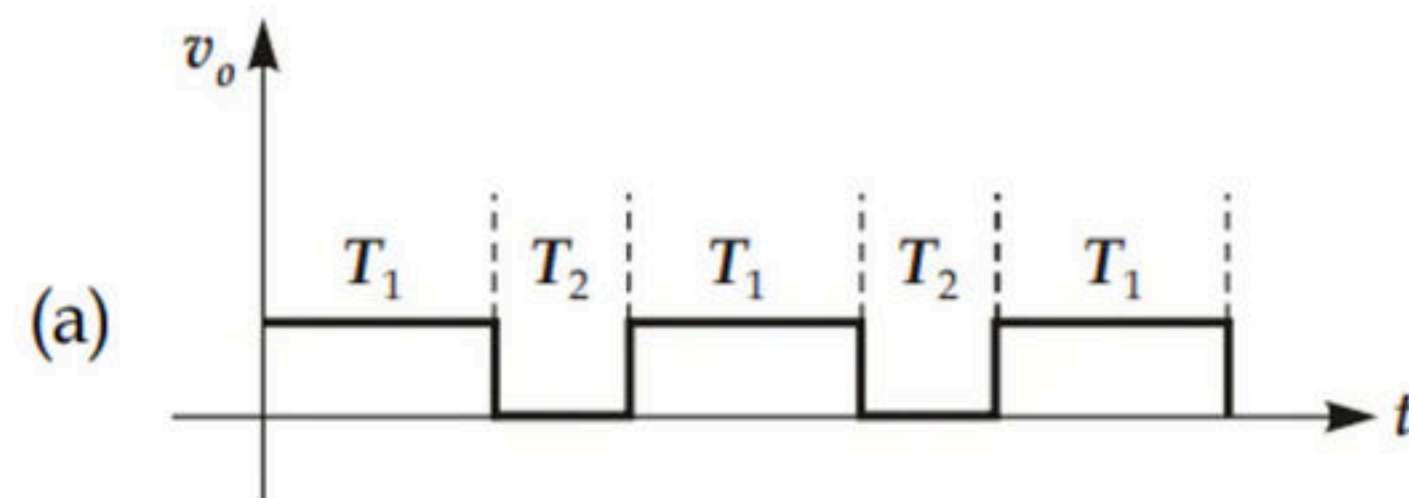The monoshots M_1 and M_2 when triggered produce pulses of width T_1 and T_2 respectively, where $T_1 > T_2$. The steady-state output voltage V_o of the circuit is



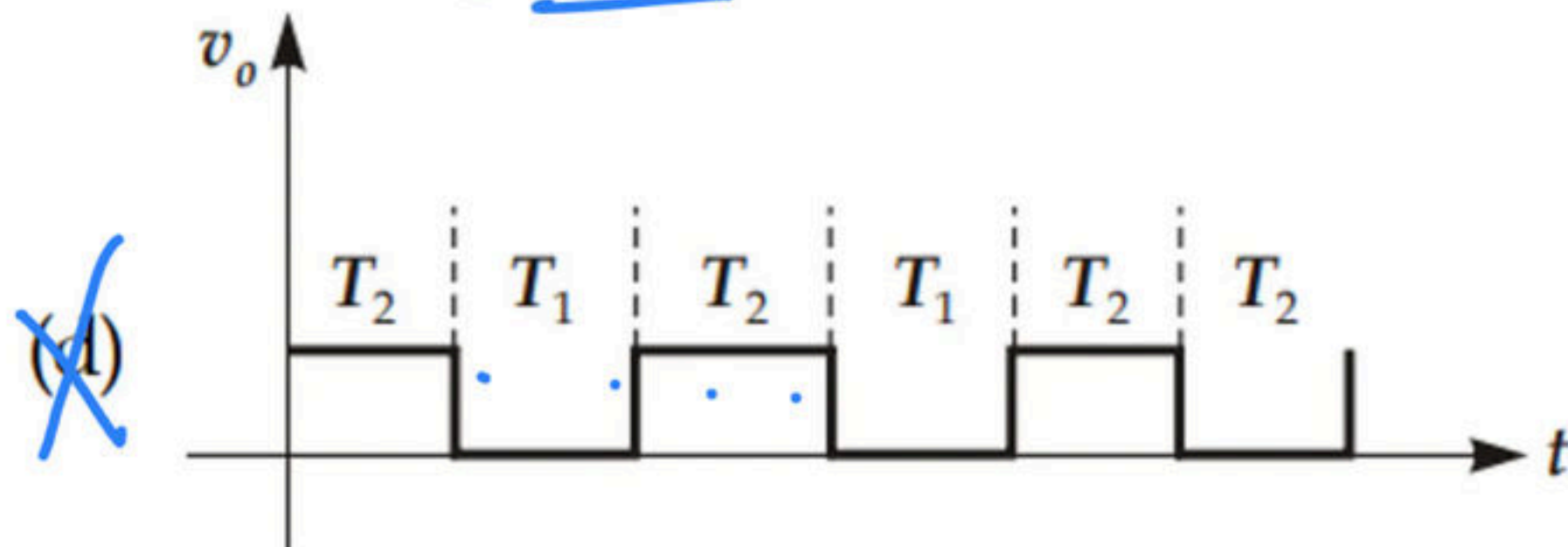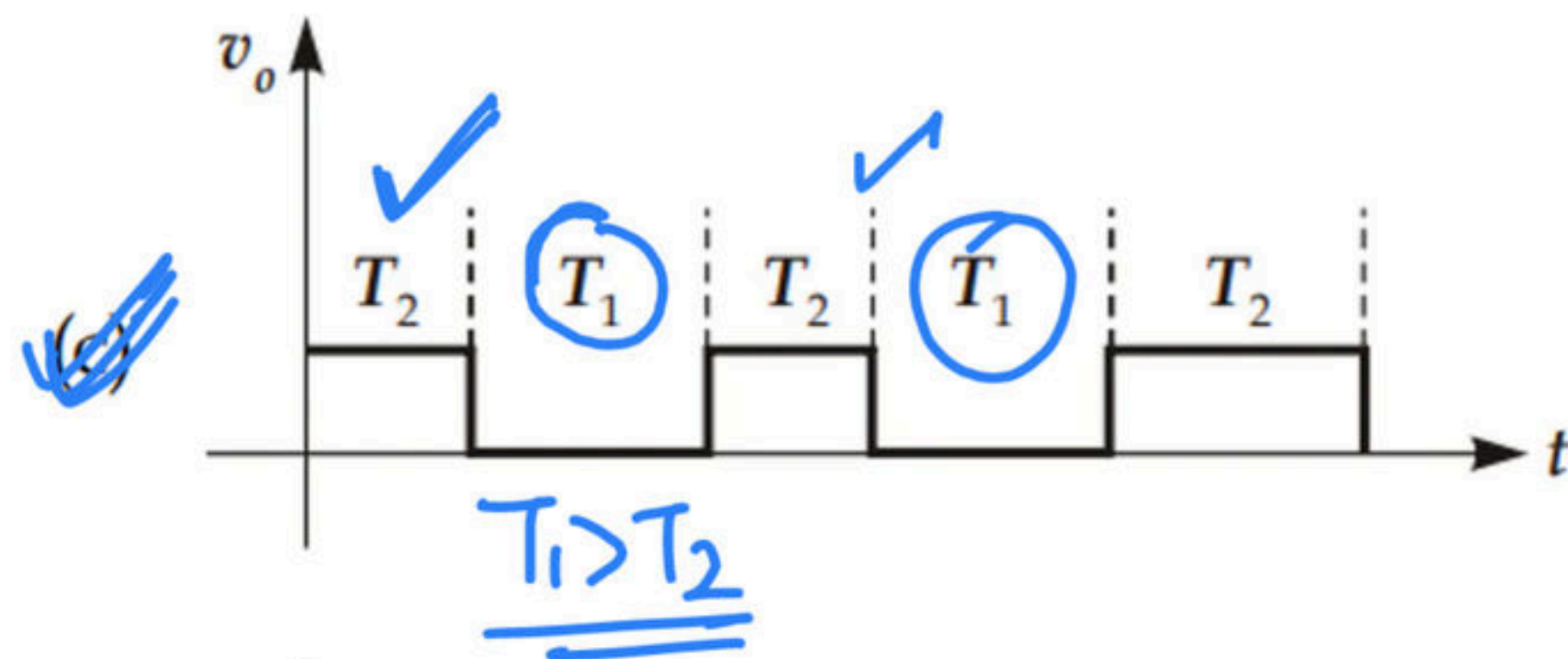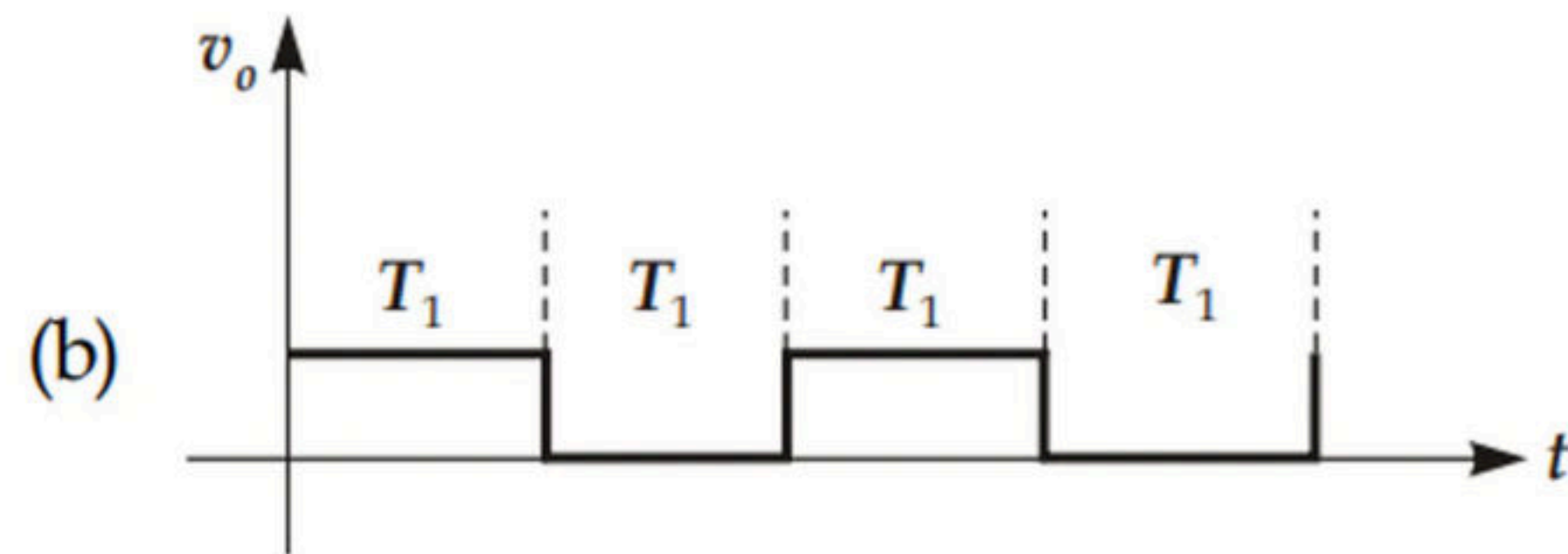


[EE-2014 : 2 Marks]


Q

An RC-coupled amplifier is assumed to have a single-pole frequency transfer function. The maximum lower cut-off frequency allowed for the amplifier to pass 50 Hz ^{Symmetrical.} Square wave with no more than 10% tilt is _____.

1) RC HPF

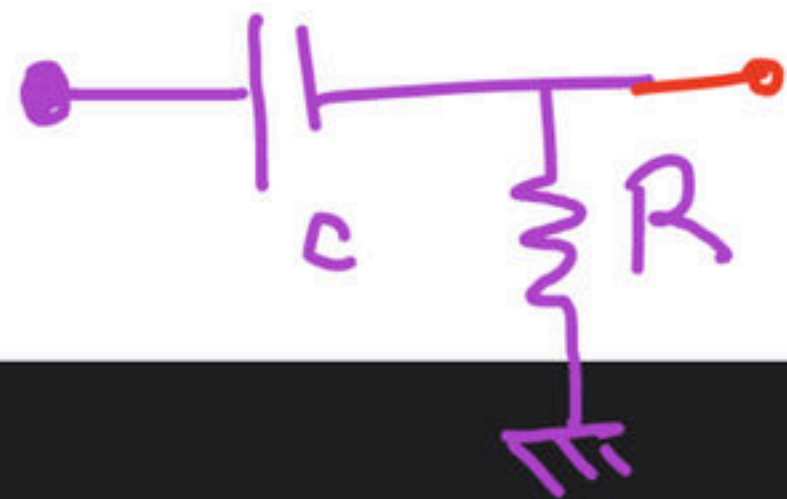

[EC-1995 : 1 Mark]

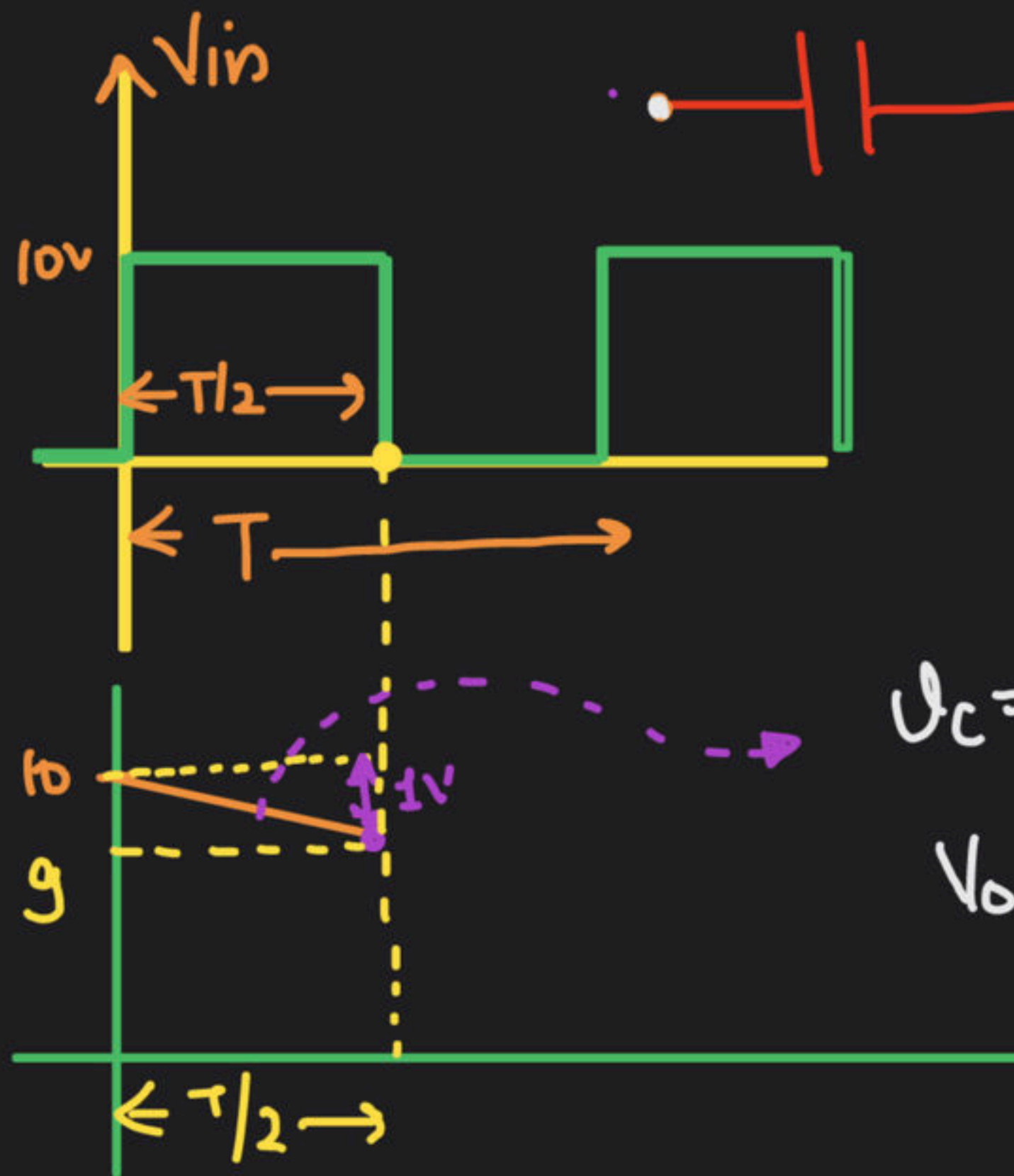

$$V_c = 10(1 - e^{-t/RC})$$

$$V_o = 10 - V_c = 10e^{-t/RC}$$

\Rightarrow

$$\omega_L = \frac{1}{RC}$$

$$10 \left[1 - \frac{t}{RC} \right]$$

$$10 \left[1 - \frac{T/2}{RC} \right] = 9$$

$$T = 2RC \times 0.1$$

$$RC = \frac{T}{2 \times 0.1} = \frac{1}{50 \times 2 \times 0.1}$$


$$RC = \frac{1}{10} = 0.1$$

$$\boxed{\omega_L = \left\{ \frac{1}{RC} = \frac{1}{0.1} = 10 \right\}}$$

 In a multi-stage RC-coupled amplifier the coupling capacitor

- (a) limits the low frequency response.
- (b) limits the high frequency response.
- (c) does not effect the frequency response.
- (d) blocks the d.c. components without effecting the frequency response.

[EC-1993 : 1 Mark]



An amplifier is assumed to have a single-pole high-frequency transfer function. The rise time of its output response to a step function input is 35 nsec. The upper -3 dB frequency (in MHz) for the amplifier to a sinusoidal input is approximately at

a) 66

b) 0.66

c) 0.066 ~~d) 9.9~~

$$t_r = 2.2RC$$

$$RC = \frac{35}{2.2} \text{ ns.}$$

$$\omega_H = \frac{1}{RC} = 62.8 \times 10^6 \text{ rad/sec}$$

$$f_H = \frac{\omega_H}{2\pi} = 9.9 \times 10^6 \text{ MHz}$$

Q.6 The f_T of a BJT is related to its g_m , C_π and C_μ as follows:

(a) $f_T = \frac{C_\pi + C_\mu}{g_m}$

(b) $f_T = \frac{2\pi(C_\pi + C_\mu)}{g_m}$

(c) $f_T = \frac{g_m}{C_\pi + C_\mu}$

~~(d)~~ $f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$

[EC-1998 : 1 Mark]

Q.7 An *npn* transistor (with $C_\pi = 0.36$ pF) has a unity gain cut-off frequency f_T of 400 MHz at a dc bias current $I_C = 1$ mA. The value of its C_μ (in pF) is approximately ($V_T = 26$ mV)

☒ (a) 15

(b) 30

(c) 50

(d) 96


[EC-1999 : 2 Marks]

$g_m = 1/26$

$C_\mu + C_\pi = 15.30$
pF

Common Data For Q. 7 and 8 :

Consider the phase shift oscillator shown in figure with parameters $R = 4 \text{ k}\Omega$ and $C = 10 \text{ nF}$.

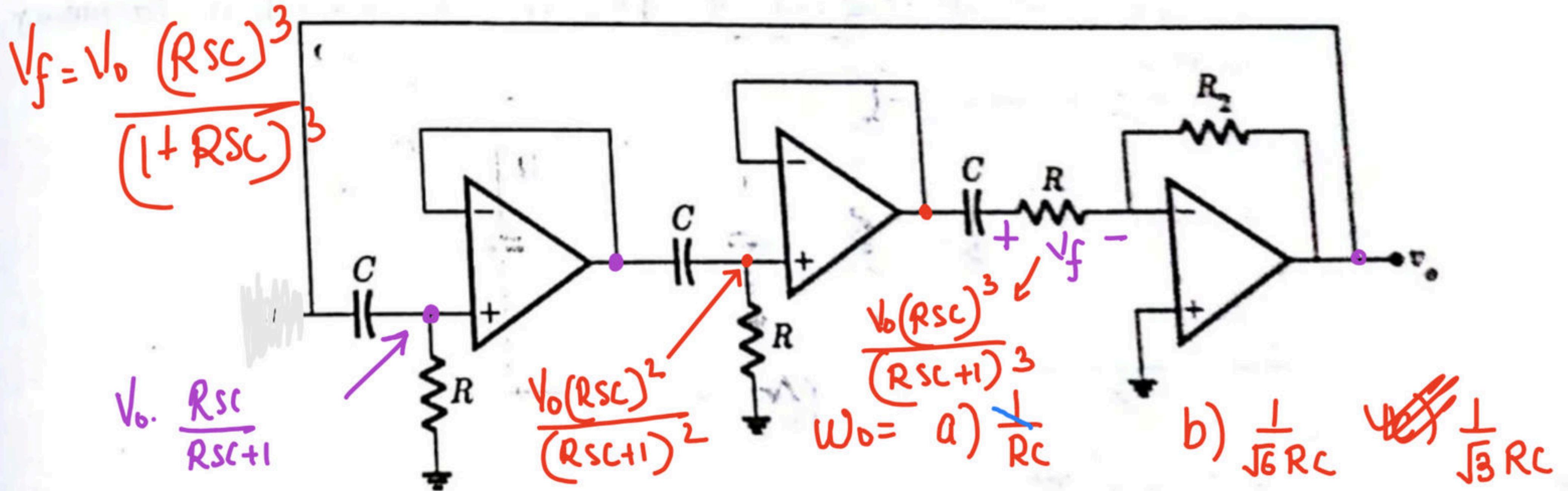

QUES 10.2.7 What is the frequency of oscillation (in kHz) ?

QUES 10.2.8 The required value of R_2 for the oscillation is _____ $\text{k}\Omega$.

a) 32 b) 16
c) 4 d) 48

$$\beta = \frac{(R_{SC})^3}{(1 + R_{SC})^3} =$$

$$A\beta = -\frac{R_2}{R} \cdot \frac{(R_{SC})^3}{1 + 3(R_{SC})^2 + 3R_{SC} + (R_{SC})^3}$$

1

$$\omega = \frac{1}{\sqrt{3}RC} \checkmark$$

$$-\frac{R_2}{R_1} \cdot \frac{-j \frac{1}{3\sqrt{3}}}{j\sqrt{3} - j \frac{1}{3\sqrt{3}}} = 1$$

$$\frac{R_2}{R_1} \cdot \left(\frac{1}{9-1}\right) = 1$$

$$R_2 = \underline{\underline{32k}}$$

Revise duode
 ~~~~~  
 Revise EDC  
 ~~~~~